

5 10 22 28 34 42 48
54 59 62 67

ELEKTOR ELECTRONICS

THE INTERNATIONAL
ELECTRONICS MAGAZINE

67 ADDRESS

29 MOTOROLA BULLETIN
BOARD

31 MOTOROLA LITERATURE ADDRESS

61 IC UK ADDRESS

April 1994
£ 2.45

DISCOUNT VOUCHER
FOR ELEKTOR BOOKS




MAINS SIGNALLING SYSTEM

RS232 speedo-
meter

Headphone
amplifier

Halogen
light dimmer

Stroboscope

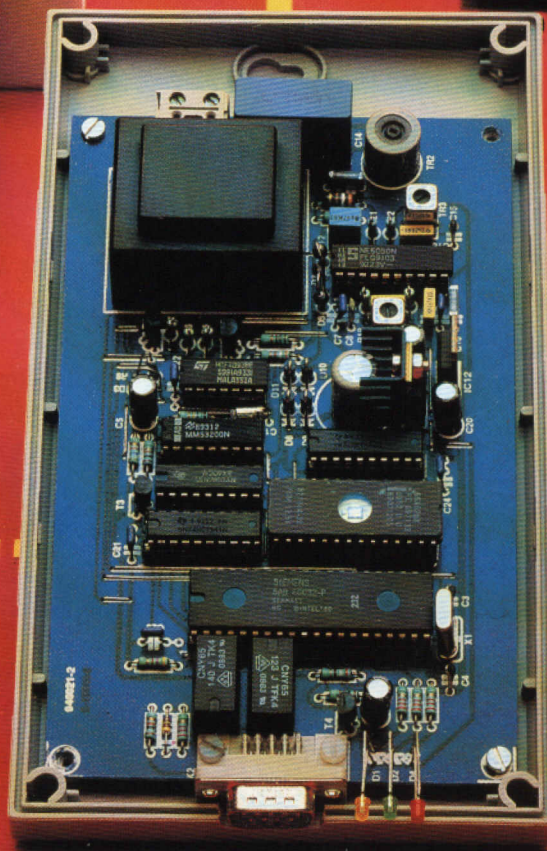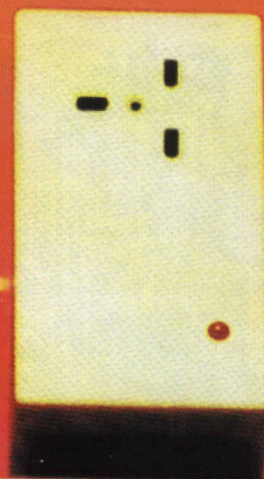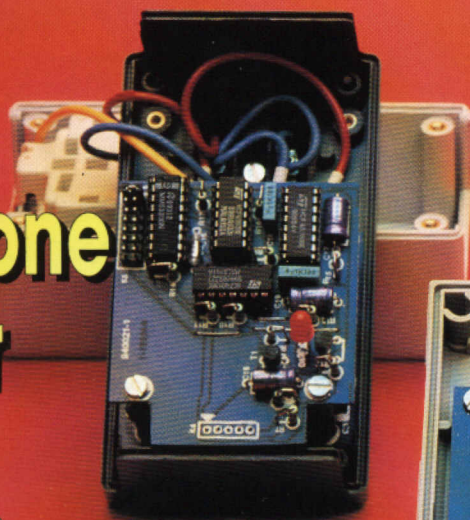

AUDIO & HI-FI • COMPUTERS & MICROPROCESSORS • DESIGN IDEAS • RADIO, TELEVISION & COMMUNICATIONS • SCIENCE & TECHNOLOGY • TEST & MEASUREMENT

In next month's issue

- Stamp BASIC computer
- General purpose sensor monitor
- Differential probe for oscilloscopes
- Morse decoder
- Using the double balanced mixer
- Figuring it out – Part 16: More about Fourier
- And others for your continued interest

Front cover

The photograph shows the receiver of a mains signalling system for home automation, of which the first part (of a two-part article) is discussed on page 42. Mains signalling is a method by which signals can be superimposed on mains wiring for the remote control of electrical equipment. The technique is well established in the USA, but in this country and Europe interest in it as a medium for communications has begun only in the late 1980s.

© 1994 Elektor BV.

ABC
AUDIT BUREAU OF CIRCULATIONS

CONSUMER PRESS

READERSHIP SURVEY. Readers are asked to spend a few minutes on answering a number of multiple choice questions on their likes and dislikes of the form and content of this magazine – page 39

BOOK CREDIT VOUCHER. In this and the next two issues we will publish a voucher that will entitle the holder to up to 30% discount on the purchase price of any Elektor Electronics book – page 51

AUDIO & HI-FI

- 22 **PROJECT:** Headphone amplifier
Design by T. Giesberts

COMPUTERS & MICROPROCESSORS

- 10 **PROJECT:** RS232 speedometer
Design by D. van de Vliet
- 28 **PROJECT:** 68HC11 processor board
Design by J. Scherer and A. Hermann
- 34 **COURSE:** 80C535 hardware/assembler – Part 2
Software by Dr. M. Ohsmann
- 59 **PROJECT:** RS232 interface for general-purpose bus
Design by A. Rietjens

GENERAL INTEREST


- 5 **PROJECT:** Halogen light dimmer
Design by T. Giesberts
- 42 **PROJECT:** Mains signalling system – Part 1
Design by W. Hackländer and S. Furchtbar
- 48 **COURSE:** Figuring it out – Part 15: Sine waves and others
By Owen Bishop
- 62 **PROJECT:** Stroboscope light
Design by T. Giesberts

RADIO, TELEVISION & COMMUNICATIONS


- 16 **PROJECT:** A lower frequency receiving system
By Richard Q. Marriss, G2BZQ
- 54 Direct conversion receivers – Part 2
By Joseph J. Carr, BSc, MSEE

MISCELLANEOUS INFORMATION

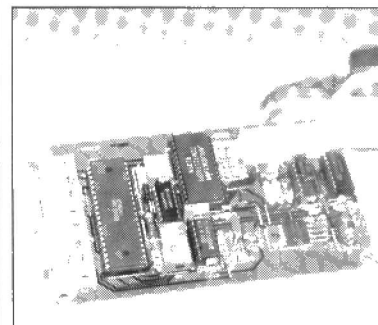
- 74 Buyers' guide
- 67 Component ratings
- 68 Credits
- 74 Index of advertisers
- 68 Letters
- 70 Readers' services
- 69 Switchboard




RS232 speedometer - p. 10

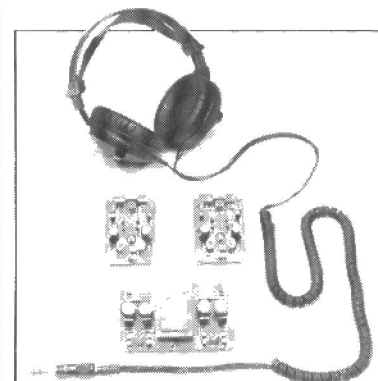

Headphone amplifier - p. 22

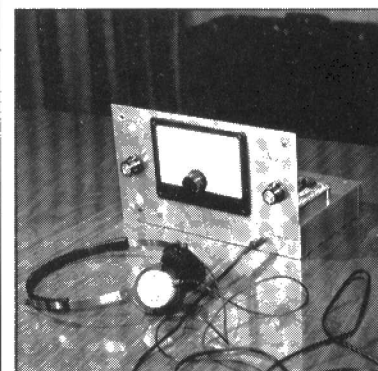


Direct conversion receivers - p. 54

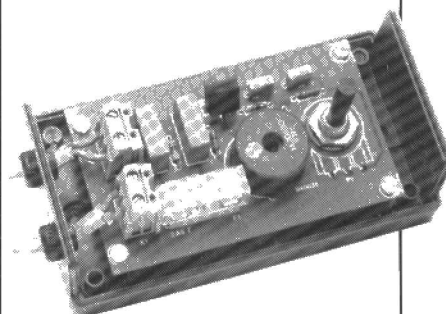

Halogen light dimmer - p. 5

Elektor Electronics is published monthly, except in August, by Elektor Electronics (Publishing), P.O. Box 1414, Dorchester, Dorset DT2 8YH, England. The magazine is available from newsagents, bookshops, and electronics retail outlets, or on subscription at an annual (1994) post paid price of £27.00 in the United Kingdom; air speeded: £34.00 in Europe; £43.00 in Africa, the Middle East and South America; £45.00 in Australia, New Zealand and the Far East; and \$57.00 in the USA and Canada. Second Class Postage paid at Rahway N.J. Postmaster: please send address corrections to Elektor Electronics, c/o Mercury Airfreight International Ltd Inc., 2323 Randolph Avenue, Avenel, New Jersey, N.J. 07001.

HALOGEN LIGHT DIMMER

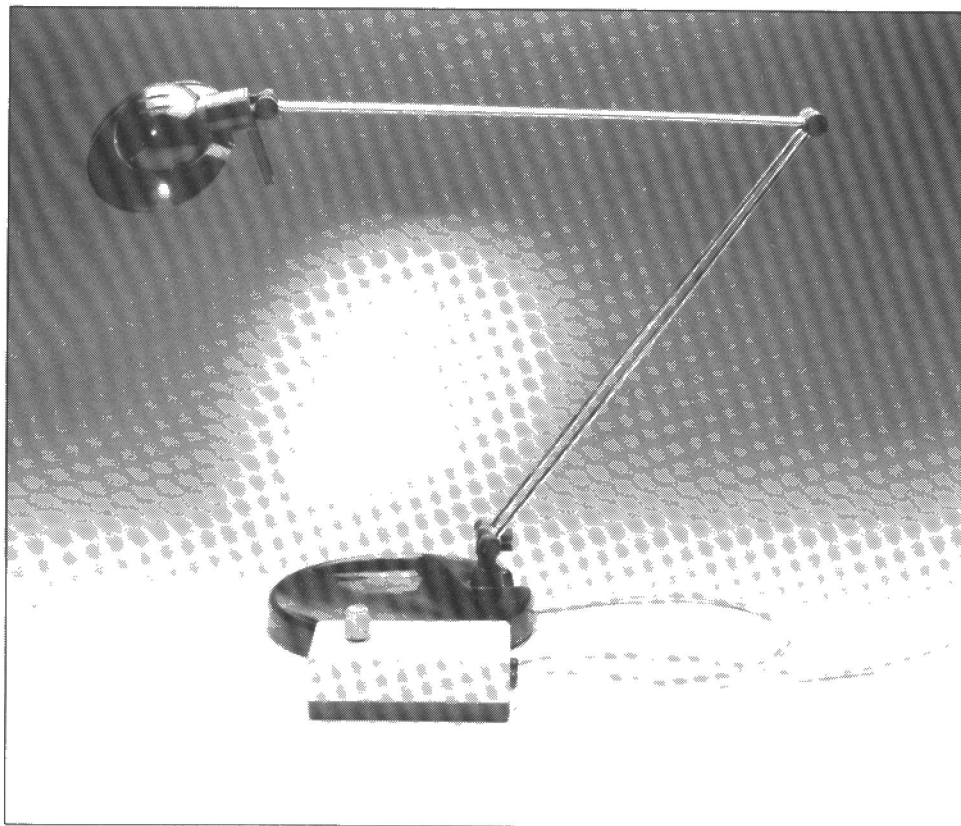

The popularity of halogen light is still increasing, and rightly so because of some distinct advantages: the colour temperature is agreeable and excellent to work by, the efficiency is relatively high, and the lamps are powered by a low voltage. One disadvantage of halogen lights is rarely mentioned, however, although it is pretty obvious: conventional light dimmers can not be used. In this article an ingenious circuit is described to overcome that disadvantage.

Design by T. Giesberts

THERE are several ways of controlling the intensity of a lamp. The simplest and most obvious of these is to insert a high-power adjustable resistor in the supply line to the lamp. Theoretically, there is no objection against this solution. In practice, however, the power lost (in the form of heat) via the resistor increases as the lamp intensity is reduced. Again, this is no problem in theory, but most of you will balk at the energy waste caused by a red-glowing resistor and a lamp lighting at, say, a quarter of its nominal intensity. Fortunately, the series resistor method has never made it to large scale use with halogen lights, and it is easy to see why.

A much more elegant alternative is the adjustable transformer, or auto-

transformer, which held a very strong position for quite some time as a light dimmer in theatres and cinemas. With the arrival of thyristors and triacs, the autotransformer soon disappeared, and the principle of voltage control was replaced by phase control.

Phase control

Although an autotransformer is an interesting piece of technology, it is a fairly costly and cumbersome device. These disadvantages do not apply to the competitive technique, phase reduction, also known as phase control or phase cutting. Light dimmers operating on this principle are just as compact and inexpensive as the previously mentioned adjustable resistors, but

that is as far as the comparison goes because they are virtually free from the 'energy waste' disadvantage.

Phase control is achieved with the aid of a fast electronic switch (usually a triac), which is driven in such a way that it is closed during a section of the each period of the alternating supply voltage. In this way, pieces are 'cut out' of the phase. During the time the switch is open, no current flows, so no energy is wasted in the regulating device. The operation of the phase control is illustrated in **Fig. 1**. As soon as the alternating voltage is past the zero crossover point, and about to increase in the positive or negative direction, a capacitor is charged via an RC network. Almost instantly, the triac is fired (triggered) by a pulse generated by the charged capacitor. The triac starts to conduct, and switches on the lamp. The lamp lights only briefly, however, because the triac stops to conduct as soon as the current which flows through the device drops below the so-called 'hold' level. That happens, obviously, when the alternating voltage reaches the next zero crossover point, which causes the triac to be switched off, and wait for the next trigger pulse.

By comparing the left-hand and right-hand section of **Fig. 1**, it becomes clear how the intensity of the lamp can be made adjustable. By including a potentiometer in the previously mentioned RC network, the instant at which the capacitor is sufficiently charged to furnish the trigger pulse, becomes variable. If an 'early' instant is set (left-hand part of **Fig. 1**), the triac will conduct the largest part of each half period. Consequently, the lamp will light at an intensity just below its maximum. By increasing the RC time (right-hand drawing), the triac is fired much later, so that the lamp lights much shorter. If the firing pulse arrives just before the next zero crossing, the lamp will hardly light because it is on for a very small part of each half period.

Phase control with halogen lights

Unfortunately the transformer used with halogen lights makes it impossible to apply the above principle of phase cutting straight away to achieve intensity control. While a normal incandescent lamp forms a fairly 'neat' non-reactive load, the transformer used to step down the mains voltage to the halogen lamp supply voltage of 12 V or 24 V is a highly inductive load.

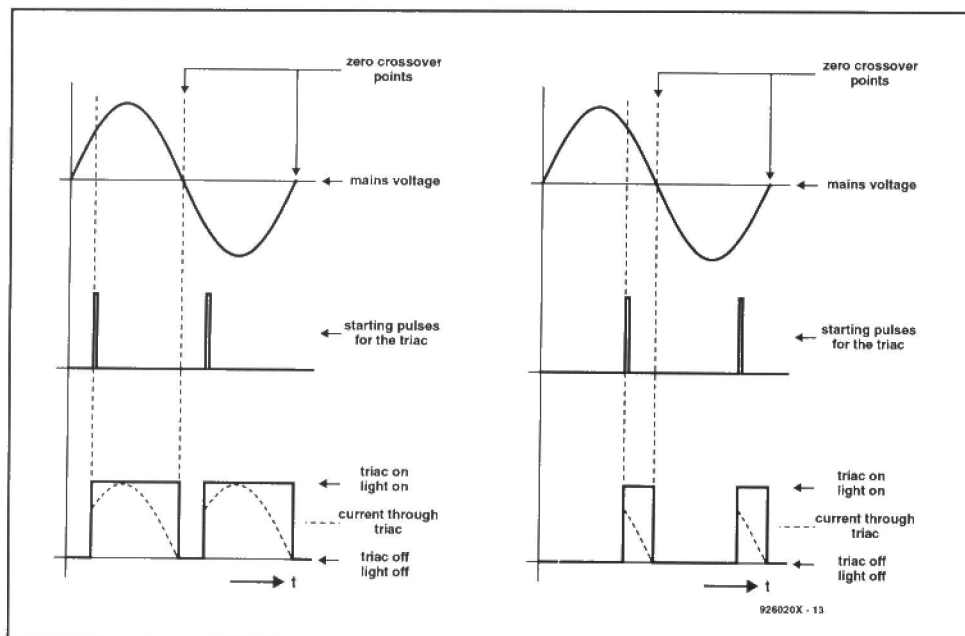


Fig. 1. In a phase reduction dimmer circuit, the lamp is only on for an (adjustable) part of each half period of the alternating supply voltage. This is achieved with the aid of a triac, which is triggered by an RC circuit, and switched off again (automatically) on each zero crossover point of the alternating voltage.

Consequently, current and voltage are not in phase, causing a lot of trouble. Assuming that a phase control circuit is used to 'dim' a transformer, it will often happen that a firing pulse arrives at the triac gate when the current, instead of the voltage, passes a zero crossover point. If that happens, the triac can not possibly start to conduct because it passes a current which is

below the hold level. The result of the reactive component presented by the transformer primary is erratic behaviour of the control.

Can we do something about that? The first solution would appear to use a triac with a very low hold current, because that reduces the risk of faulty triggering considerably. However, this is considered 'cheap' by many, and

goes round the actual problem. The real solution obviously lies in conditioning the trigger pulse. Two options are available: (1) the firing pulse may be made wider so that it lasts beyond zero crossings of the current, should these occur, or (2) each pulse is repeated a couple of times at very short intervals.

The second option is adopted for the present circuit, and a glance at the circuit diagram in Fig. 2 shows the practical implementation.

The triac control proper is shown in the right-hand part of the diagram. Forgetting about C_3 for a moment, i.e., assuming P_1 and R_3 to shunt R_4 , leaves you with an ordinary dimmer circuit. Capacitor C_4 is charged via resistors R_3 , R_4 , P_1 and R_5 . After a certain time, which is adjustable with P_1 , the charge contained in C_4 is large enough for diac D_1 to start conducting, so that a firing pulse is applied to the gate of triac Tri_1 . Consequently, the triac conducts, and so forms a connection between K_1 and K_2 , i.e., the input and the output of the dimmer circuit. So far, nothing new.

The operation of the circuit is made special by the capacitor we 'forgot about' in the above description. In fact, C_3 is charged virtually simultaneously with C_4 , and functions as a reservoir device for the latter. Immediately after D_1 starts to conduct, and a part of the charge of C_4 has 'disappeared' in the gate of Tri_1 , the capacitor is almost instantly recharged by C_3 via R_3 , causing another trigger pulse at the triac gate. This happens a couple of times, so that the triac gate is fed with bursts of three or four trigger pulses. The triac trigger burst is shown in the oscillogram in Fig. 3.

The remainder of the circuit is all plain sailing, and requires hardly any further explanation, since the components used are found in nearly every dimmer circuit. Briefly, network R_1 - C_1 prevents voltage surges caused by the inductive load from 'killing' the triac. The combination of inductor L_1 and capacitor C_2 keeps the spurious signals caused by the trigger circuit away from the mains lines, where they would give rise to interference in other equipment. Resistor R_2 , finally, acts as a 'bleeder' across capacitor C_2 , preventing dangerous voltages on the circuit output when the load is disconnected.

The triac used in the dimmer, finally, is just the thing for the present application: it has a hold current of only 50 mA, and is capable of withstanding short pulses of up to 63 A!

Building the dimmer

For ease of construction as well as for safety's sake, the dimmer is best built on the printed circuit board shown in

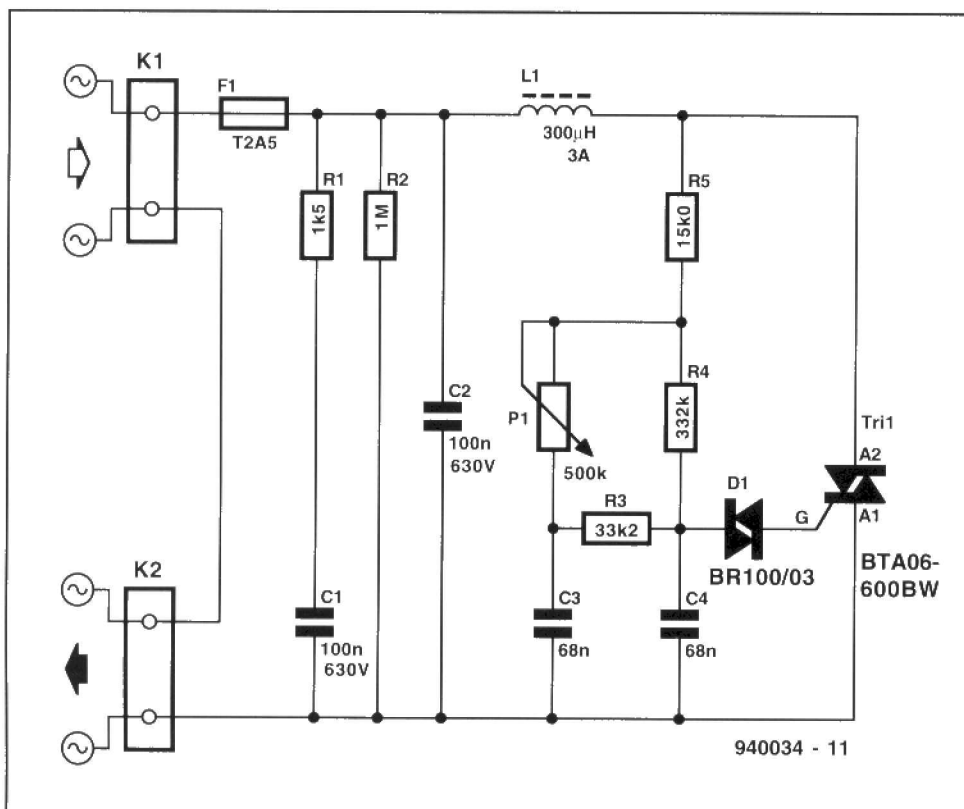


Fig. 2. To make sure that the dimmer operates reliably with the inductive load presented by the transformer primary, the RC network is extended with a capacitor to provide a burst of trigger pulses, rather than a single pulse.

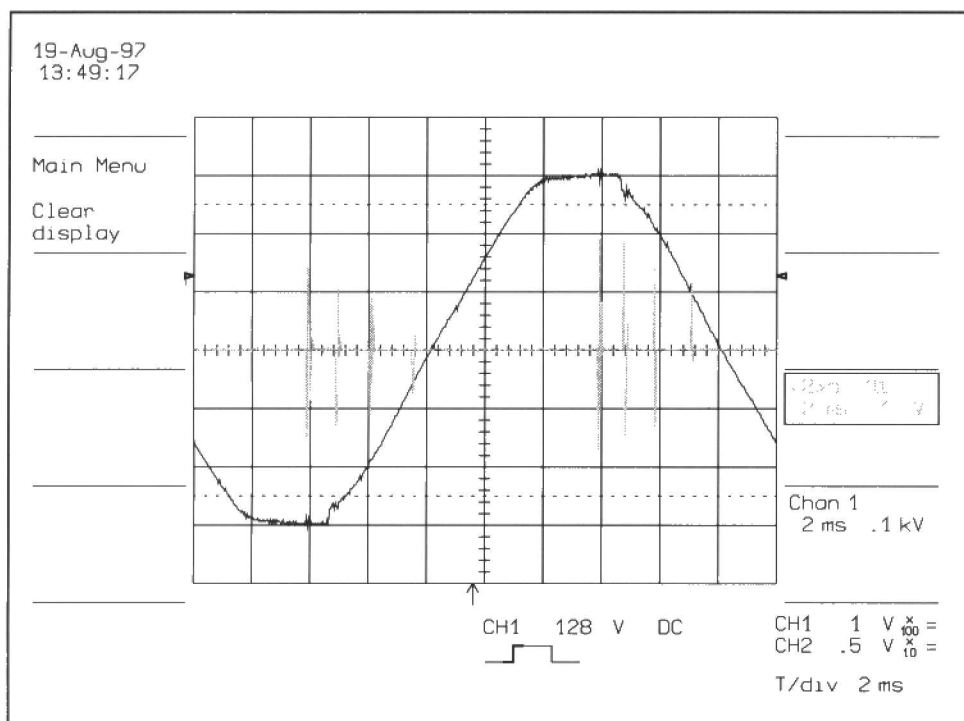


Fig. 3. LeCroy 9410 oscilloscope screendump showing the trigger burst and the alternating supply voltage. If one of the pulses in the burst happens to coincide with the zero crossover point, there is always another to trigger the triac.

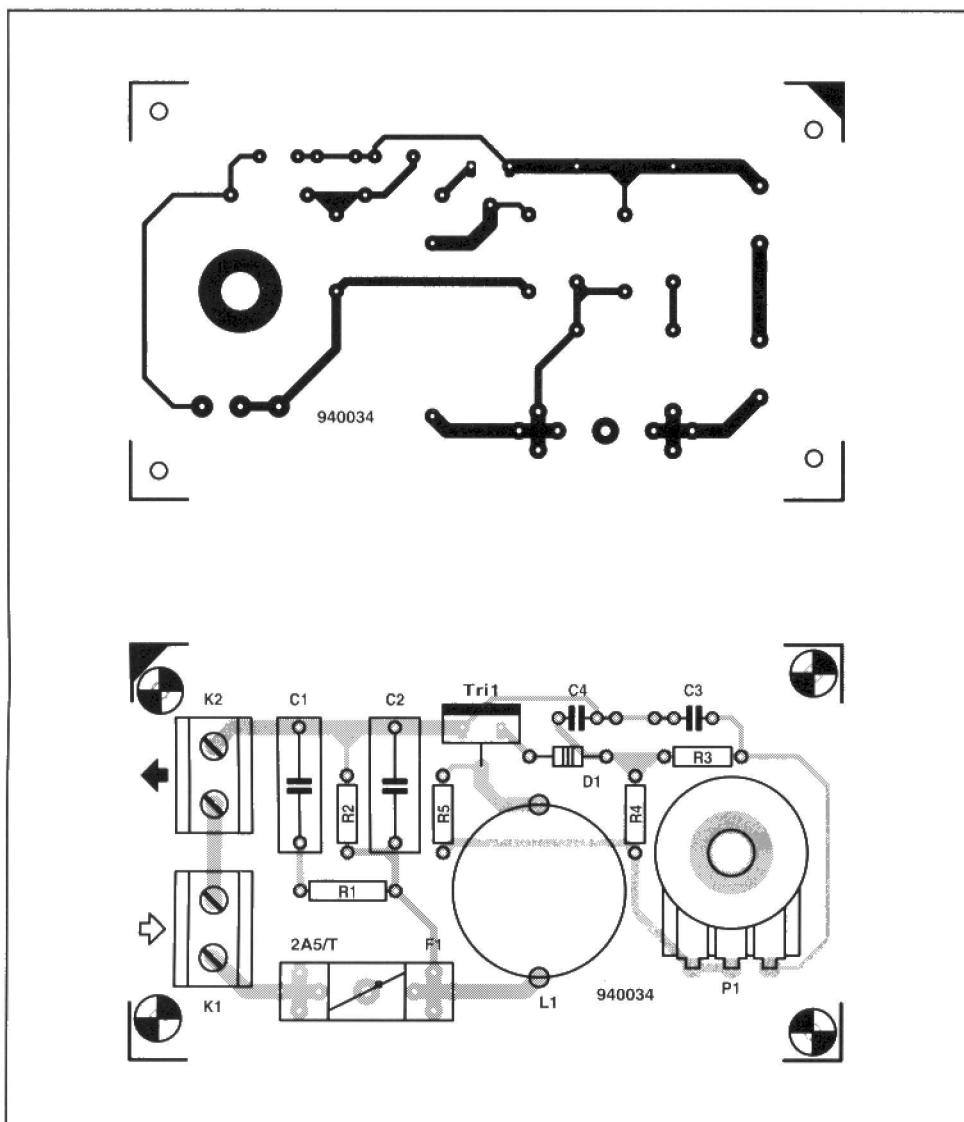


Fig. 4. Populating this printed circuit board should not take you more than half an hour or so (PCB not available ready-made through the Readers Services).

Fig. 4. Unfortunately this PCB is not available ready-made through our Readers Services, so you have to etch and drill it yourself.

Construction should be easy for the 'average' home constructor. Be sure, however, to pay attention to the specifications of the components used. Capacitors C_1 and C_2 must be rated at 630 VDC, and potentiometer P_1 must be a type with a plastic spindle. Do not use an ordinary choke for L_1 , but a real suppressor choke capable of handling up to 3 A. The triac can make do without a heat-sink if the load current does not exceed about 1 A (P approx. 200 W). If you intend to use the dimmer for higher currents (for instance, for a 300-W ceiling uplight), the triac must be fitted with a small heatsink. The maximum current the circuit is capable of supplying is about 2.5 A (approx. 500 W).

Since a dimmer is invariably connected directly to the mains, every precaution should be taken to ensure electrical safety. **Most parts in the circuit are at mains potential, and are, therefore, extremely dangerous to touch. Never touch any part while the circuit is connected to the mains. Always disconnect the circuit from the mains before doing any measurement or adjustment.** Mount the dimmer in an all-ABS enclosure, and provide sturdy grommets and strain reliefs on the mains cables connected to K_1 and K_2 . ■

COMPONENTS LIST

Resistors:

- $R_1 = 1k\Omega$ 1%
- $R_2 = 1M\Omega$ 1%
- $R_3 = 33k\Omega$ 1%
- $R_4 = 332k\Omega$ 1%
- $R_5 = 15k\Omega$ 1%
- $P_1 = 500k\Omega$ linear w. plastic spindle

Capacitors:

- $C_1, C_2 = 100nF$ 630VDC
- $C_3, C_4 = 68nF$

Semiconductors:


- $D_1 = BR100/03$ diac
- $Tri1 = BTA06-600BW$ (SGS-Thomson)

Miscellaneous:

- $L_1 = 300\mu H$ 3A suppressor coil, e.g., Newport 1430430
- $K_1, K_2 = 2$ -way PCB terminal block, pitch 7.5mm
- $F_1 =$ fuse 2A5 slow, w. PCB mount holder
- Enclosure: e.g. OKW A 90 20 087 (65x20x40mm)
- 2 strain relief clamps

RS232 SPEEDOMETER

Serial ports are frequently used for long-distance communication between computer equipment. The speed at which data is conveyed on such a link is called the baud rate, a figure indicating the number of bits transmitted per second. Unfortunately, in practice there are often gross differences between the programmed and the actually achieved data speed. The circuit described here measures the actual speed of RS232 data.

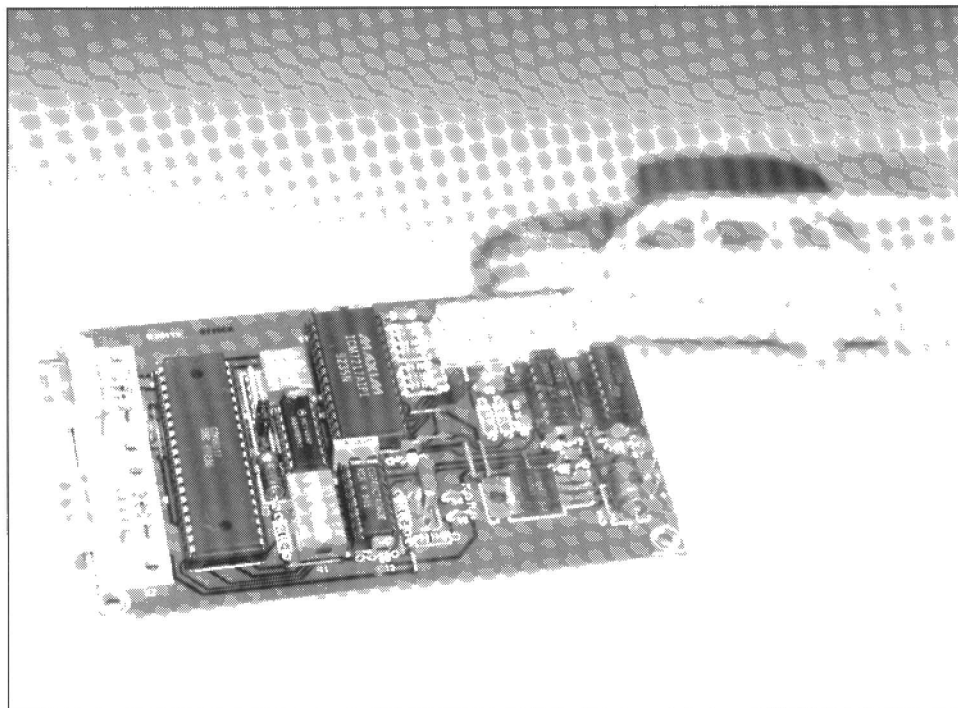

Design by D. van de Vliet

TWO interfaces may be found on virtually any computer: the parallel Centronics interface, and the serial RS232 interface. These two communication ports allow the computer to exchange data with peripheral devices and/or other computers. The big advantage of the parallel port is the relatively high speed at which data may be transmitted. A single write command

to this port is sufficient to transmit eight databits at a time. On the down side, the parallel port requires a large number of wires. Apart from the eight data lines there are at least two control lines, and a ground line. That is 11 lines for a minimum configuration. When the parallel link is relatively long, crosstalk between the individual lines increases, but may be suppressed

to some extent by adding a screen around every signal line. All in all, a lot of copper wires are required to set up a reliably operating parallel connection. The parallel port is, therefore, less suitable for long-distance communication.

The second interface is the serial RS232 port, which transmits one bit at a time. In principle, two wires, a signal wire and a ground wire, are sufficient to set up a fast and reliable data connection. A disadvantage of the serial port is that quite a few control signals are required to prevent data being lost. Essentially, two solutions are available to implement handshaking between the sending and the receiving device: hardware (RTS/CTS) and software (XON/XOFF, EOT/ACK, and others). Hardware handshaking is fast but needs a minimum of two extra wires. The software solution does not need extra wires, but slows down the communication because control commands are inserted between the data signals. Fortunately, a serial link with hardware handshaking has fewer wires than a parallel link.

Serial it will be


Once it has been decided to use serial communication between two computer devices, it is necessary to agree on a number of transmission parameters which apply to the transmitter and the receiver. Apart from the transmission speed (baud rate), the error checking method (parity bit) and the number of stop bits have to be made identical at both ends of the serial link. Normally, a start and a stop bit are appended to the eight databits, so that a serial word consists of 10 bits. The parity bit is rarely used these days. In the exceptional case of two stop bits and a parity bit being added, the serial word consists of 12 bits.

Figure 1 shows the structure of 10-bit and 12-bit serial words. The numbers 10 and 12 are essential when determining the effective speed of a serial link. At a baud rate of 1,200, the maximum number of 10-bit words that can be transmitted per second is 120, or 100 if 12-bit words are used.

The baud rate selection depends on a number of factors. If the computer communicates with a peripheral which is located nearby, a high baudrate, for instance, 19.2 kbit/s, may be used. If, on the other hand, a very long cable is used, a lower speed has to be chosen to enable the negative effects of stray capacitance introduced by the cable to be

MAIN SPECIFICATIONS

Baudrate:	300 to 19,200 bits per second
Compatible:	with any RS232 interface
Connection:	inserted into link between equipment
Signal line:	RxD or TxD; selection via jumper
Measurement:	exact data speed
Display:	four 7-segment LED displays
Readout:	datawords per second
Data format:	all existing formats supported

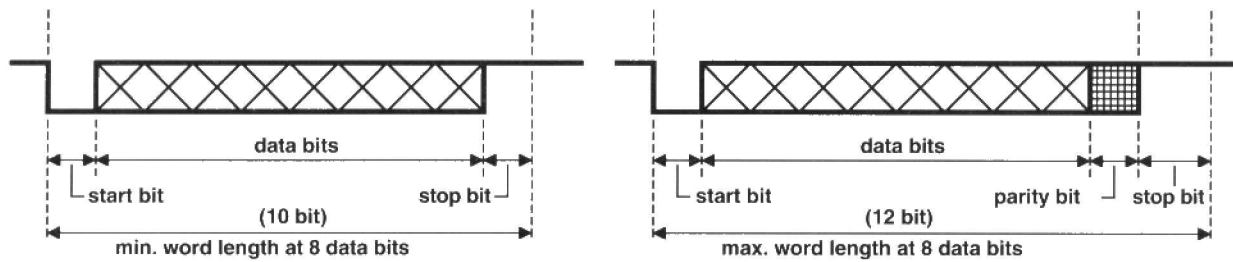

930119 - 11

Fig. 1. Structure of 10-bit (left) and 12-bit (right) serial words. Words consist of databits, a start bit, a parity bit, and one or two stop bits.

suppressed.

Note that so far we have only been discussing the actual speed of the interface. By using data compression algorithms, the effective speed of a serial link can be boosted considerably. As a result of compression techniques, each bit conveyed via the cable is given a certain 'added value'.

The exact speed

As already noted, the speed at which a serial link is to operate is determined to a large extent by the baudrate. There are, however, other factors that determine the communication speed. Both at the transmitter and the receiver end


of the cable, a microprocessor often needs time to do a lot of calculations before it is able to transmit or receive a byte. Obviously, this is a slowing-down factor, particularly if the calculations are complex, and no buffering is implemented. The delay is caused by the handshaking protocol, which halts the communication for the time needed by the microprocessor to do its number crunching. Consequently, the serial link is much slower than one would expect from the baud rate set on the transmitter and the receiver.

Equipment fitted with data buffers is less affected by delays because the data flow can be maintained while the processor is busy calculating. Unfor-

tunately it is not always evident if such a buffer is present inside a certain peripheral, so that the actual data speed achieved on a data link can only be measured by a special instrument. Such an instrument is described here.

The circuit

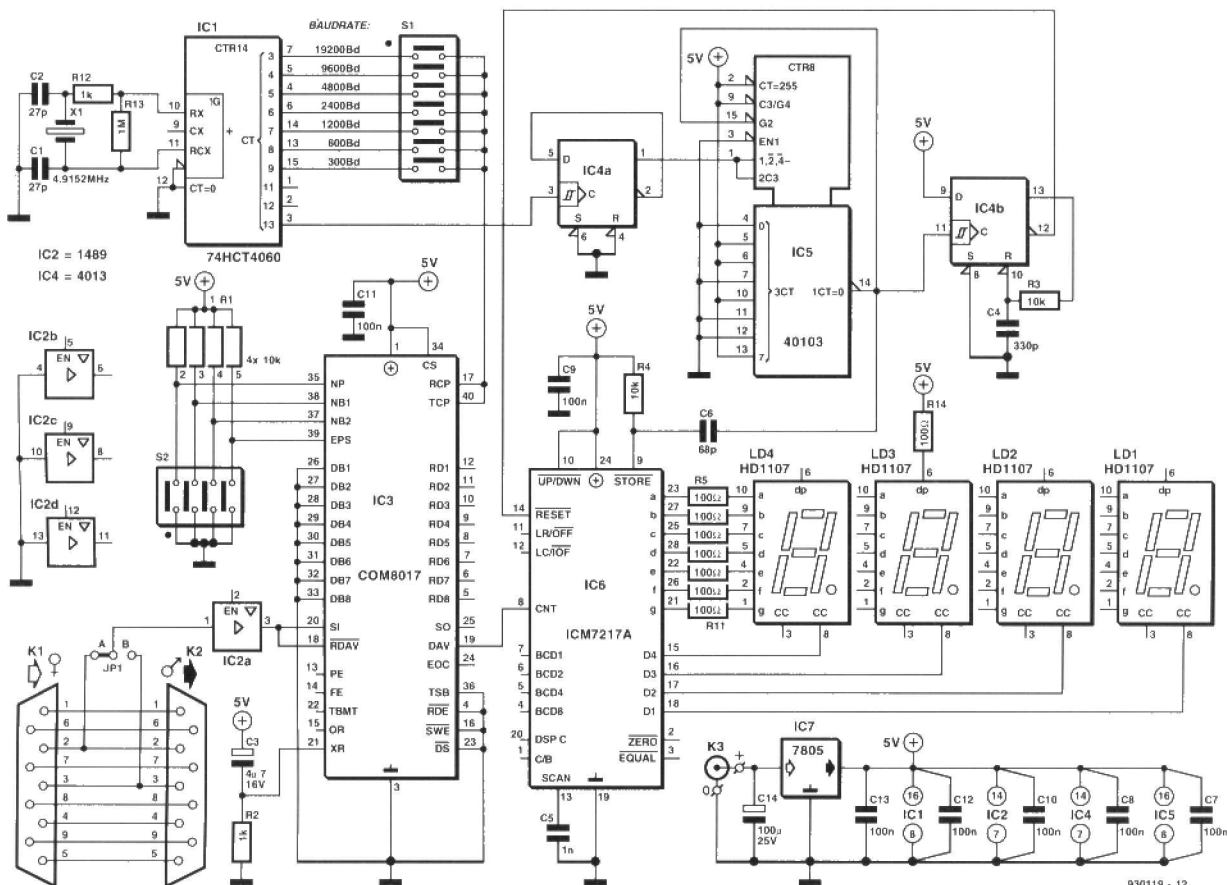The circuit diagram of the RS232 speedometer is given in **Fig. 2**. The heart of the circuit is formed by a UART (universal asynchronous receiver/transmitter), IC₃, a type COM8017 or AY3-1015. This IC is capable of converting parallel data into serial, and vice versa. To be able to do this, the UART only requires a clock



930119 - 12

Fig. 2. Circuit diagram of the RS232 speedometer. Most of the work is done by a UART type COM8017.

signal which determines the bit speed. Only a small section of the UART is used in the present circuit. None the less, the approach is economical, since a discrete circuit capable of doing serial-to-parallel conversion with checks on stop bits and parity would be more expensive. The non-used inputs of the UART have been made inactive.

The UART is reset by network R_2 - C_3 . Behind it sits a display circuit built with a Harris Semiconductor type ICM7217A, IC₆, and four Siemens LED displays type HD1107. Every time the UART receives a valid word, its DAV (data available) output supplies a positive pulse transition (rising edge) which causes the contents of the counter contained in IC₆ to be increased by one. What remains to be done at this

stage is to set up a time slot within which the number of DAV pulses is counted. Fortunately, that is not a problem because the circuit contains a baudrate generator which can also be used to create a suitable timing signal for the counter.

The oscillator built around quartz crystal X_1 operates at a frequency of 4.91 MHz. To obtain the desired clock signals, the 4.91-MHz clock is fed to the cascade of divide-by-two ripple counters contained in IC₁.

The desired baudrate is selected with the aid of switches contained in S_1 . The UART expects a clock frequency which equals 16 times the baudrate on the serial link. Hence, output Q13 of IC₁ (pin 3) supplies a signal with a frequency of 300 Hz

($4.9152 \text{ MHz}/2^{14}$). The 300-Hz signal is divided by 300 with the aid of a bistable wired as a divide-by-two scaler (IC_{4a}), and a presetable counter (IC₅). The result is a 1-Hz signal at pin 14 of IC₅.

The combination of the counter, the display, and the 1-Hz reference signal allows the number of DAV pulses that occur within one second to be readily measured, so that the exact number of data words conveyed via the serial link in one second is accurately known.

The circuit uses two steps to store the counter information. First, the negative-going edge of the STORE signal (IC₅ pin 14) is used to copy the counter contents into an output register, and from there to the display. Next, a reset signal (IC_{4b}, pin 12) resets the counter in IC₆. Bistable IC_{4b} is wired to operate as a monostable multivibrator (MMV). It generates a reset signal on the positive-going signal edge that appears at the output of IC₅ every second. The mono time of the MMV is determined by network R_3 - C_4 .

Four bright displays indicate how many bytes (not bits!) reached the receiver during the last second. Usually,

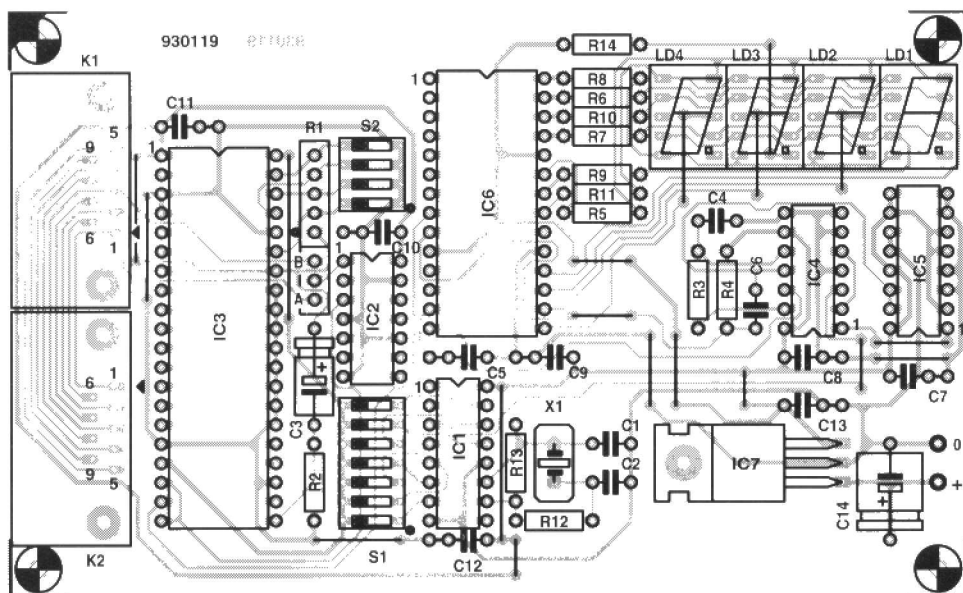
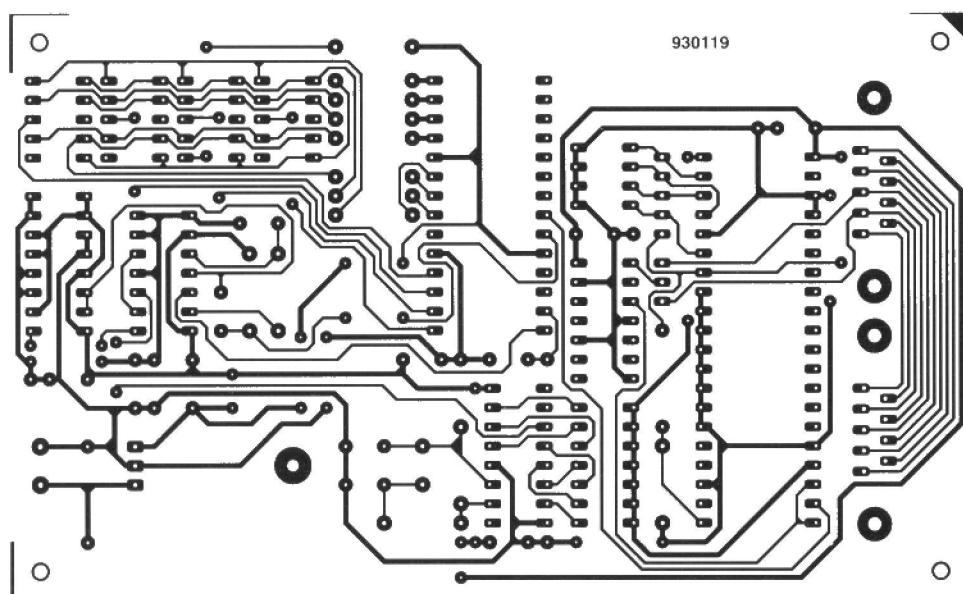


Fig. 3. Artwork of the printed circuit board designed for the RS232 speedometer (PCB not available through the Readers Services).

COMPONENTS LIST

Resistors:

R1 = 4-way SIL array 10k Ω
 R2, R12 = 1k Ω
 R3, R4 = 10k Ω
 R5-R11, R14 = 100 Ω
 R13 = 1M Ω

Capacitors:

C1, C2 = 27pF
 C3 = 4 μ F 16V
 C4 = 330pF
 C5 = 1nF
 C6 = 68pF
 C7-C13 = 100nF
 C14 = 100 μ F 25V

Semiconductors:

IC1 = 74HCT4060
 IC2 = 1489
 IC3 = AY-3-1015 or COM 8017
 IC4 = 4013
 IC5 = 40103
 IC6 = ICM7217A
 IC7 = 7805
 LD1-LD4 = HD1107

Miscellaneous:

K1 = 9-way sub-D socket, angled.
 K2 = 9-way sub-D plug, angled.
 K3 = mains adaptor socket.
 S1 = 7-way DIP-switch.
 S2 = 4-way DIP-switch.
 X1 = 4.9152MHz crystal.
 JP1 = 3-way SIL-header w. jumper.

the readout will indicate a value which is at least 10 times smaller than the set baud rate (remember, 10 bits are needed for every word). The advantage of the byte-speed readout is that the user has a clear indication of the amount of information conveyed. The decimal point in LD₃ is on continuously to make the displayed value easily readable.

It is important to note that the speed measurement works correctly only if hardware (RTS/CTS, etc.) handshaking is used. Software handshaking uses start and stop commands which are also conveyed via the data lines. Obviously, these commands are recognized as valid databytes by the speedometer, while they are not data proper. Since software handshaking is hardly used any more, you probably need not worry about this deficiency of the speedometer.

The rest of the circuit is really straightforward stuff. The serial input signal is buffered by IC_{2a}, a type LM1489. As already mentioned, switch S₁ is used to select the desired data speed, while S₂ allows you to select the number of stop bits, the parity check, and the number of databits contained in a byte. The function of the two switches is summarized in **Table 1**.

Construction: no problems!

A printed circuit board has been designed to make the construction of the RS232 speedometer as easy as possible. Unfortunately, this printed circuit board is not available ready-made through the Readers Services, so you have to etch it yourself.


It is best to start by fitting the 18 wire links on the board. In this way, the links can not be forgotten later. Also, four wire links are located underneath displays, so they have to be fitted first in any case. It is recommended to use IC sockets since that enables faulty ICs to be replaced more easily.

Fit jumper JP₁. Position A means that the speed of the Tx/D signal is measured, while in position B the speed of the Rx/D signal is measured. Set the baudrate and the transmission format with the aid of the DIP switches, and the circuit is ready for use.

Connect the supply input to the output of a 9V/200 mA mains adapter, and insert the speedometer into the serial link. Next, switch on the speedometer, and start the transmission. The measured value should appear almost instantly on the displays.

EVERYTHING UNDER CONTROL?

Wherever data is exchanged via a serial link, it is essential for the transmitter and the receiver to have matching transmission parameters, laid down in the handshaking protocol. The RS232 link supports hardware and software protocols. Software handshaking makes use of extra characters which are added to the data proper. Effectively, one device controls the other by means of the data transmitted. In this way, a computer is capable of sending text line-by-line by adding the 'end-of-text' (EOT) marker at the end of each line. EOT being an ASCII character, the printer is able to interpret this message as a command to print the received data. When it is finished with printing, and ready to receive new data, it transmits an acknowledge message in the form of an ACK code. Like EOT, ACK is a standard ASCII sign. The advantage of software handshaking is the small number of signal lines that make up the serial link (see **Fig. A**).

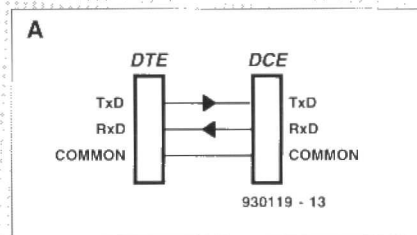


Hardware handshaking is a different kettle of fish, and based on different combinations of handshaking lines. For example, a computer (transmitter or DTE, data terminal equipment) is connected to a modem (receiver or DCE). As soon as the computer is switched on, its DTR (data terminal ready) line (pin 20) becomes active. This is a signal for the modem to become active. In this type of link, the


DTR output on the computer is connected to the DTR input on the modem. Hence, the DTR connection on the transmitter is different from that on the receiver.

The modem signals that is ready for use by actuating its DSR (data set ready) output (pin 6) on the RS232 port. This signal is detected by the computer on its DSR input. In other words, the modem acts as a transmitter, and the computer as a receiver.

Next, the computer actuates the RTS (request to send) line, pin 4. Via the CTS (clear to send) line, the modem informs the computer whether or not it is ready to accept data. If so, the transmission may commence. One handshaking line that has not been mentioned so far is called DCD (data carrier detect). It is actuated by the modem, and indicates that a stable connection has been established with another modem via, for instance, the telephone line. By monitoring the status of this line, the computer is able to detect when the carrier disappears from the telephone line.

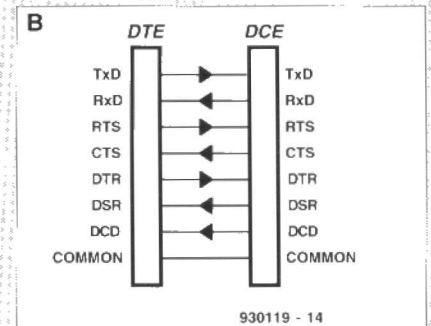

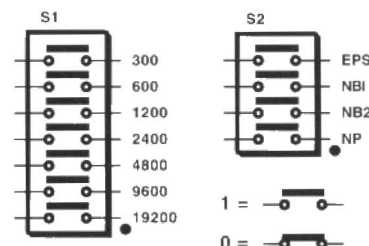Evidently, the disadvantage of the hardware handshaking option is the larger number of wires, as shown in **Fig. B**.



settings S2	
EPS = 1	parity = even
EPS = 0	parity = odd
NP = 1	parity = none
NP = 0	parity

NB2	NB1	bit/character
0	0	5
0	1	6
1	0	7
1	1	8

930119 - T1

Table 1. Overview of DIP switch functions.

A LOWER FREQUENCY RECEIVING SYSTEM

The lower frequency regions of the radio spectrum are probably the most unknown, and neglected by the more recent generations of radio listening enthusiasts. Yet, signals, often mysterious, abound, provided one has a good receiver and antenna system. Such a system is described in this article.

By Richard G. Marris G2BZQ

FOR convenience, the lower frequency spectrum has been lumped together to include the VLF (very low frequency) bands (2 kHz to 30 kHz, or 150,000 m to 10,000 m), plus part of the MF (medium frequency) band (300 to 500 kHz, or 1,000 m to 600 m). This range does, of course, encompass the European long-wave broadcast band, which is a comparatively small part of the spectrum under consideration.

Those who use the HF bands tend to use the half-wave dipole antenna as a reference. Well, a half-wave dipole at, say, 100 kHz (3,000 m) would be just under 1,500 m (approx. 3,000 ft) long! This gives some idea of the antenna problems at LF.

A suitable receiver must cover the range 2 kHz to 500 kHz (150,000 m to 600 m), and be accurately calibrated at 10 kHz intervals. It must be capable of receiving AM and CW transmissions, and preferably LSB and USB (upper/lower sideband) at the higher frequency end. An AVC (automatic volume control) on/off switch is an advantage, and an adjustable noise limiter is a distinct asset. A tape recorder gives the facility of replaying, and studying, the more mysterious signals; and anyone with RTTY receiving facilities may well be able to use them on occasion.

The receiver

The receiving system used consists of an amateur HF bands communications receiver switched to the 3,500-4,000 kHz band, as a tuneable IF (intermediate frequency) and demodulator, plus a wideband LF converter with a 3,500 kHz crystal oscillator. These units are shown schematically in Fig. 1. Any existing amateur band 3,500-4,000 kHz receiver can be used, whether a 'solid state' or older all-tube instrument.

In this particular case, a near perfect 1960's all-tube Heathkit amateur band type RA-1 receiver is used. The LF converter is a tiny circuit board

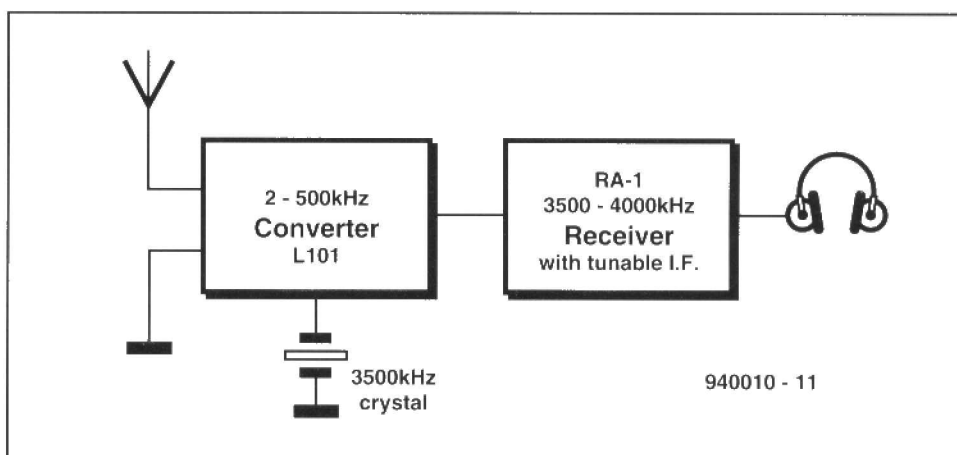


Fig. 1. Block diagram of the VLF receiving system.

type L-101/80D/PCB purchased from L.F. Engineering Co. Inc. in the USA (Ref. 1). At a price of \$39 plus \$4 postage, it was just not worth constructing such a unit, as originally intended. The converter is supplied complete with a 3,500 kHz quartz crystal, and came fitted with an on/off switch, a red LED indicator and a battery connector. The circuit uses a PP3 9-V battery, and has a current drain of

only 3 mA.

The LF converter uses a high-impedance end-fed antenna input matched to a J-FET mixer type 2N5457, and requires at least a 30-m (100-ft) long end-fed antenna. The result of the arrangement is a wide dynamic range, and higher gain than the more usual low-impedance coaxial feedline input. The output impedance into the main receiver is 50 Ω .

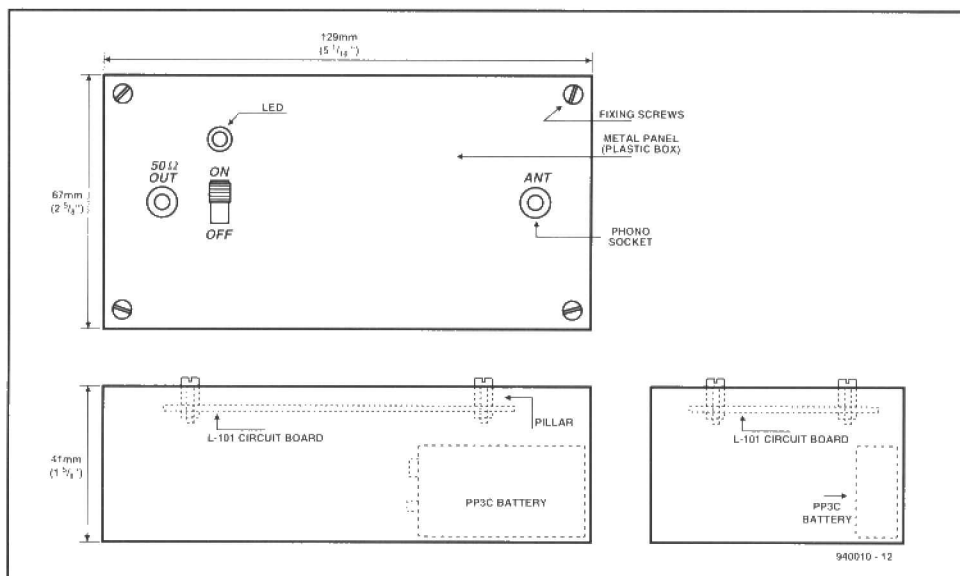


Fig. 2. The VLF converter is built into a small plastic box.

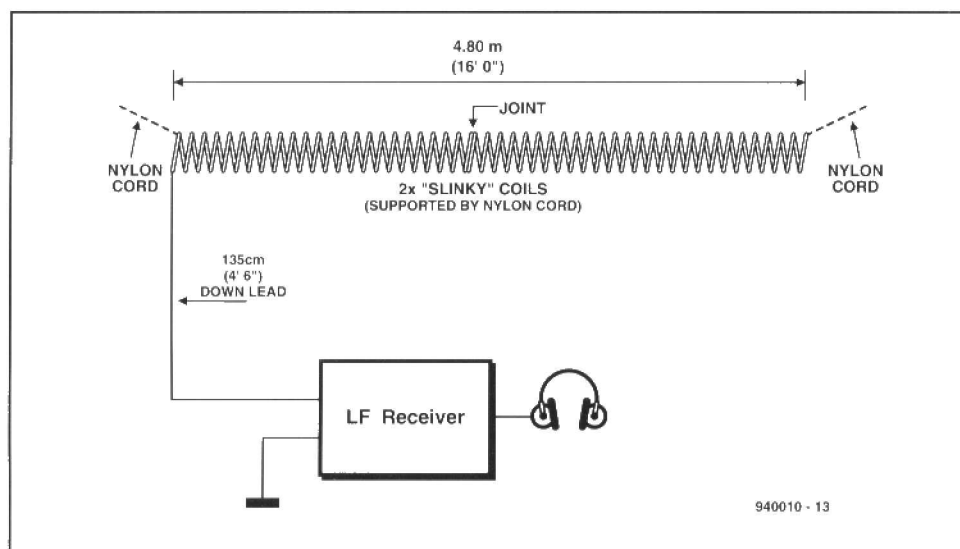


Fig. 3. The 'double-Slinky' end-fed antenna for 2-500 kHz.

The little circuit could be incorporated into the main receiver, or separately boxed. The latter option was adopted, see **Fig. 2**. The converter board is mounted, with battery, in a small plastic box with a metal lid. Throughout the whole system, phono jack sockets and plugs are used for the interconnections.

The LF converter and main receiver are interconnected with RG58 coax cable with a maximum length of about 1.2 m (4 ft). A good ground/earth should be connected to the LF converter.

With a crystal-controlled local oscillator, and crystal calibration in 100-kHz steps on the main receiver used as a variable IF, a high degree of frequency accuracy is achieved. The station frequency is measured by deducting 3,500 kHz from the tuning scale on the main receiver — see **Fig. 6**. Further frequency checks are the various time/frequency standard stations — see later.

Installing a well-elevated 30+ m antenna wire is not achievable by many, especially in built-up areas, where there may be space problems, rules and regulation, and planning permission refusals to contend with.

A number of specialized, compressed, LF antennas have been designed, built and tested. The most suitable are described below.

Antennas for VLF

1. 'Double-Slinky' end-fed antenna (2-500 kHz)

This antenna is shown in **Fig. 3**. It can be mounted indoors or outdoors, taking up an overall physical length of 4.8 m (16 ft) plus a 1.35-m download.

The antenna consists of two 'Slinky' coils connected in series. A Slinky coil is a 90-turn 7-cm diameter flexible steel spring, weighing just over 1 kg.

Each coil contains 20 m (67 ft) of conductor. When compressed, the Slinky is only about 6 cm long, but can be extended, in a helical configuration, up to about 5 m. Slinky is available from Antenna West in the USA (Ref. 2).

For the double Slinky antenna, two Slinky coils are connected in series, end to end, with a 1.35-m PVC covered flex download (which is not a critical length) — see **Fig. 3**. To connect the two coils in series, the end of each coil should have the end turns flow-soldered together.

The 'double Slinky' is supported at either end, on site, by threading white nylon cordage through the coil centre — see **Fig. 3**.

Indoors, the double Slinky may be hung up diagonally across the room,

with the download dropping down to the LF receiver in the corner of the room. Outdoors the antenna is hung from a window, with the download indoors to the receiver, and the whole supported by a nylon cordage to a suitable pole, building or tree.

If used outdoors, it will be necessary to varnish the double Slinky turns to eliminate the possibility of corrosion. The simplest way of varnishing is to suspend the stretched antenna, horizontally, outdoors, at about chest level, and thoroughly spray with varnish. To be absolutely effective, it is recommended to apply three separate coats of varnish.

The double Slinky end-fed antenna is most effective between 2 kHz and 500 kHz, and, in fact, throughout the MW AM broadcast band with other receivers.

2. The end-fed ferrite antenna (95-500 kHz)

This small space-saving antenna consists of a tuned coil wound around a ferrite rod, and end-fed with a 1.2-m lead — see **Fig. 4**. The antenna is very effective, with sharp directional properties, and a sharp 'null'.

The ferrite coil assembly is shown in **Fig. 5**. It consists of a standard 20-cm long \times 9.5 mm diameter (8/16 in) ferrite rod as used in LW/MW AM broadcast receivers. These rods are available from a number of suppliers, on the surplus market, or can be salvaged from an old broadcast receiver.

The coil winding consists of 12.7 cm (5 in) of close wound turns of 24 SWG (23 AWG) DCC (double cotton covered)

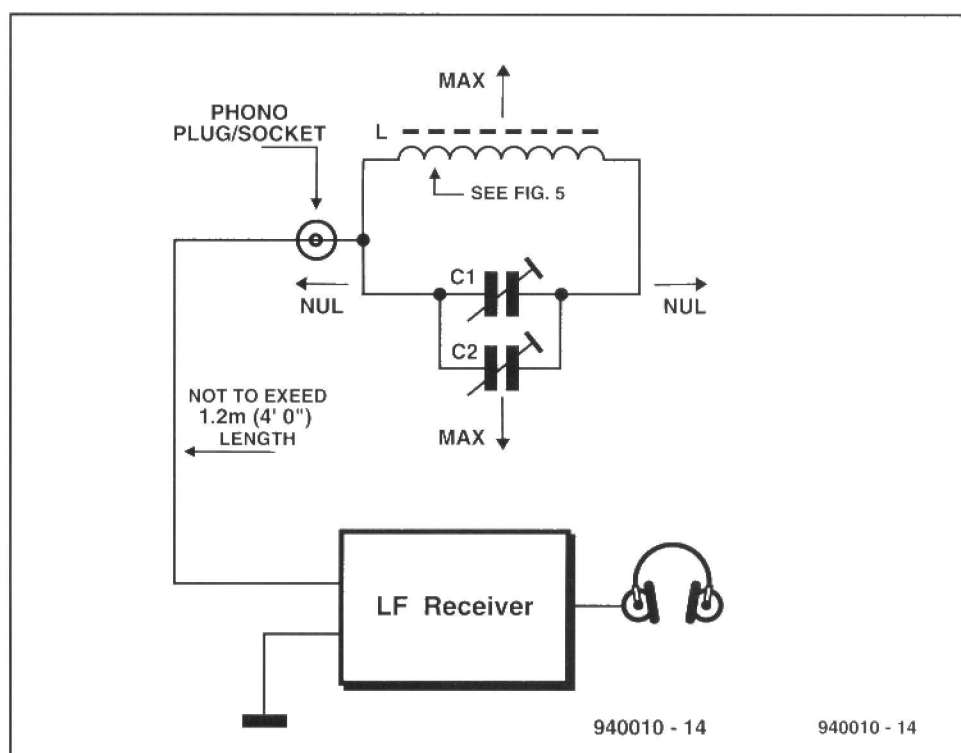


Fig. 4. The end-fed ferrite antenna (95-500 kHz).

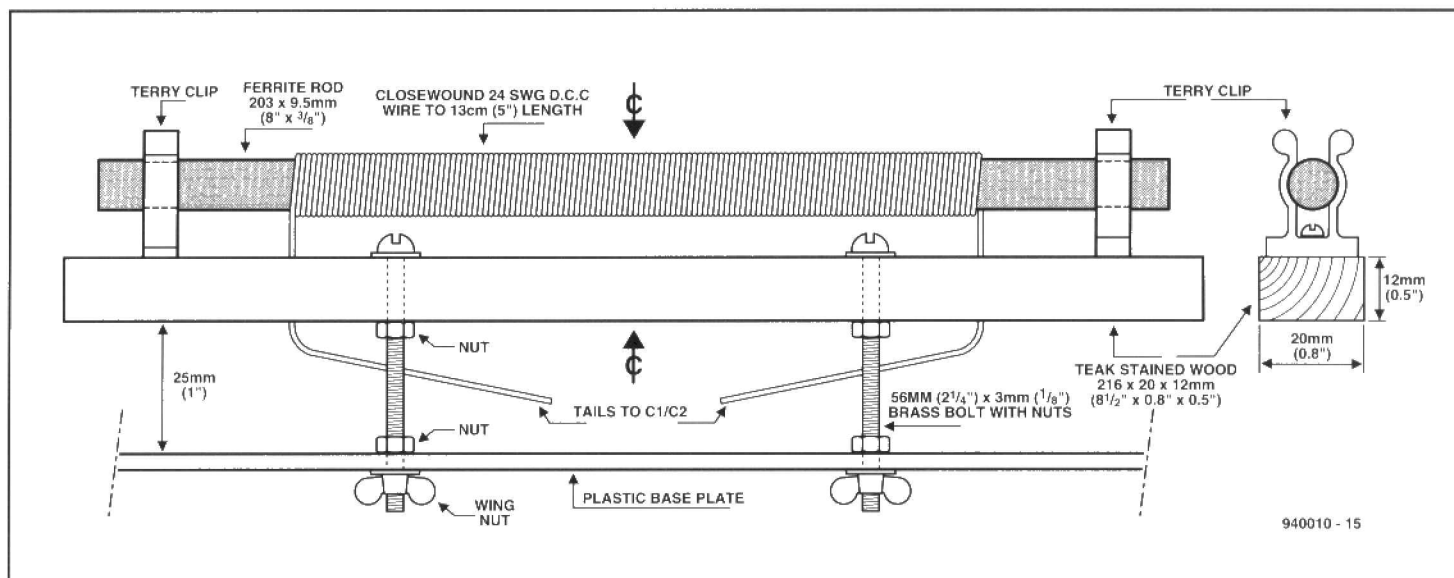


Fig. 5. Construction of the rod/coil for the end-fed antenna.

copper wire. The winding is centred either side of the middle of the rod. It is much easier to wind a 12.7-cm length than try to count 225 turns of wire. The wire ends are secured with two turns of masking tape, and the whole winding is varnished after initial testing.

The ferrite rod/coil assembly is supported by two plastic coated Terry clips screwed to a strip of teak-stained wood. As shown, the whole assembly is fastened to, and stood-off from, the antenna base plate with two brass bolts. Two nuts and a wingnut are required for each bolt, as shown.

The 1,000-pF variable capacitor (C1+C2) is a standard robust two-gang 500 pF + 500 pF tuning capacitor wired in parallel. Any adjustable trimmers/padders should be removed, and the capacitor should be fitted with an insulated extension spindle.

The simple final antenna assembly is shown in **Fig. 7**. The base plate used was an inverted coloured rigid 22 cm (8.5 in) diameter plastic picnic plate. Alternatively, a plastic or plywood base (22x22 cm), mounted on a 6x6 mm wood framework could be used.

Actual layout positions are not critical, and will depend on the physical

size of the two-gang variable capacitor, which is bolted to the base plate as shown in **Fig. 7**.

When in use, the antenna is actually placed on a small turntable to take advantage of its sharp directional effect, which assists in interference elimination.

This end-fed tuned ferrite antenna covers the frequency range from 95 kHz to 500 kHz (3,185 m to 600 m).

Listening around the spectrum

Lower frequencies listening is a completely different ball-game to HF listening. Also, wide differences can be expected between the LF and HF ends of this LF spectrum.

In general, long-distance reception is best during the hours of darkness, especially during the long winter nights. Exceptions do occur. Below about 30 kHz, however, long-distance reception is possible around the clock. Unfortunately, there is not a lot to hear down there. The receiver's CW mode should be used. However, we do have the standard frequency/time signal station GBR (Rugby) at 16 kHz, which has a wavelength of around

19 km — imagine a dipole just under 10 km long! There is also the US Navy submarine communications system which uses frequencies up to about 70 kHz. Very occasionally, high-speed CW stations have been heard, but origins not established. Listening below 30 kHz can be interesting, even if not very enlightening.

As we tune upwards in frequency, activity increases from 30 kHz to 500 kHz. Atmospheric static is often a nuisance — it is minimum around noon, and maximum during the hours of darkness. Much of it appears to be directional, and here the end-fed ferrite antenna helps. It has been noticed that as one tunes lower in frequency, from about 500 kHz, the incidence of fading signals appears to decrease.

Probably the most important step for the listener is to establish the location, on the receiver dial, of the various standard frequency and time signal stations that operate around the world. A useful publication is the low-cost *Standard frequency and time signal stations of the world* (Ref. 3), which lists frequencies, callsigns and station locations of 17 such stations between 16 kHz and 500 kHz. It also indicates the various time codes used. A readily available signal is the Loran C navigation aid on 100 kHz, among other navigational systems, to be heard below 150 kHz along with CW signals.

On the average domestic receiver, in Europe, the long-wave AM broadcast band is shown on the dial as from 2,000 m (150 kHz) to 1,100 or 1,000 kHz. It is peculiar to Europe and surrounding countries. Most European countries have an LW broadcasting station, as do several North African countries, such as Algeria and Morocco, and further East, Turkey. LW AM stations also appear to spread through Asiatic Russia.

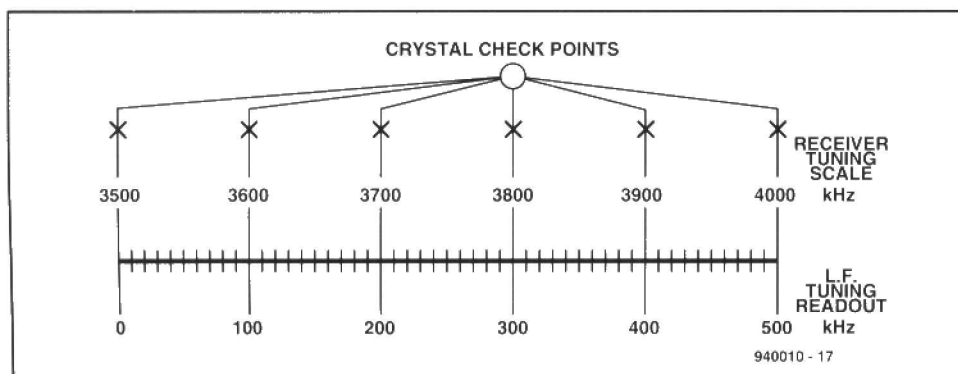


Fig. 6. LF tuning readout.

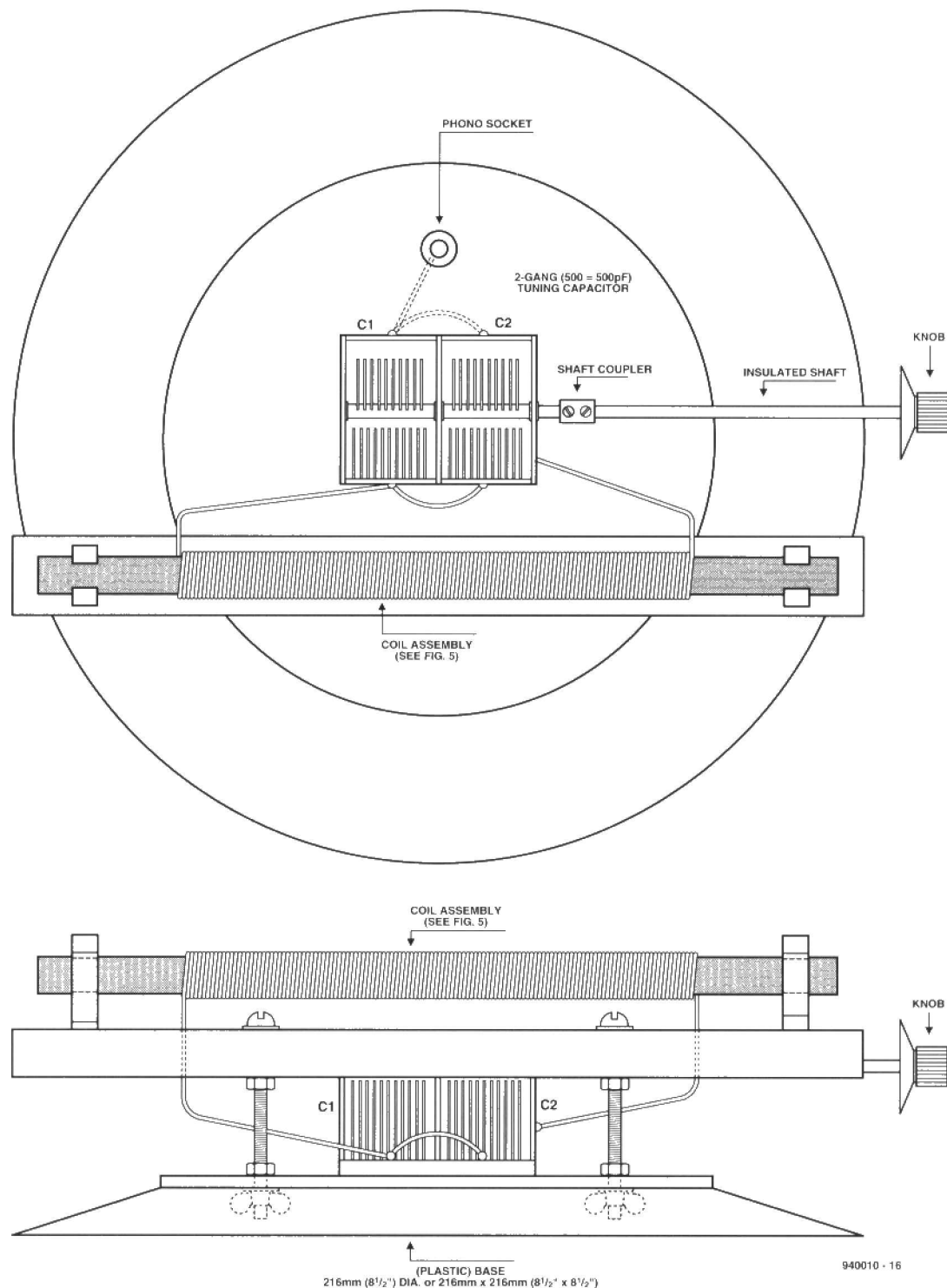


Fig. 7. Construction of the end-fed ferrite antenna assembly, which is mounted on a turntable.

Another relatively unknown fact, in Europe, is the existence of the 1,750-m Amateur Experimental Band which is available in the USA, Canada and in some Pacific areas. This band covers the frequency range from 160 kHz to 190 kHz, and there is the Long Wave Club of America (Ref. 4) which publishes a monthly magazine called *Lowdown*. Recently it has been read that Australian (and possibly New Zealand) amateurs are using 196 kHz for transmission and reception. Additionally, there is a multitude of

worldwide air/marine navigational beacons, weather and information stations, etc. These can be heard readily throughout the LW band, except in Europe, where they may be blanketed by the LW broadcast stations. Some of them may still be heard, however, between 270 kHz and 500 kHz. Also between 300 kHz and 500 kHz the odd AM and SSB station may be heard, plus CW and occasional RTTY. There is much which is not readily identifiable, and a tape recorder is an asset to study these signals later. ■

References and addresses:

1. L.F. Engineering Co. Inc., 17 Jeffry Road, East Haven CT06513, USA.
2. Antenna West, 1500 North 150 West, Provo UT84604, USA.
3. *Standard frequency and time signal stations in the world*, published by the International Short Wave League, and obtainable from the Hon. Secretary, 10 Clyde Crescent, Wharton, Winsford, Cheshire CW7 3LA, England.
4. The Long Wave Club of America, 45 Wildflower Road, Levittown PA 19057, USA.

HEADPHONE AMPLIFIER

Design by T. Giesberts

Music should be heard and enjoyed as if the orchestra were right in front of you. Unfortunately, neighbours, children and other members of the family may not be as keen as you on the particular piece of music you are enjoying. The answer to this is, of course, the use of headphones. These also have the advantage of offering a quality of reproduction that only loudspeakers costing at least ten, and probably twenty, times as much as the headphones would be able to equal.

A first-class electroacoustic transducer, whether this is a headset or a loudspeaker, can only perform to its true specification if the amplifier driving it is also first class. It is, of course, not necessary to connect a headset to a power amplifier; after all, it needs only little energy. Yet, in practice, the headphone output is often taken from the power amplifier output via a potential divider. It is, however, far better to connect it to the output of the preamplifier via a dedicated headphone amplifier as described in this article.

A headphone amplifier is, strictly speaking, a sort of line amplifier with a power output. Its amplification need not be high, since the sensitivity of most headsets is usually fairly good. If we assume that the output of the preamplifier is 1 V r.m.s., an amplification of a few times is quite sufficient: some tens of milliwatts is fine.

Average good-quality headphones provide a sound pressure of 90–100 dB for an input of about 1 mW. It should be borne in mind that modern headphones have a fairly high impedance. Until not so long ago, this impedance was 8 Ω or so, but nowadays good-quality headphones have an impedance of hundreds of ohms (typically 600 Ω). The present amplifier can deliver up to 40 mW into 600 Ω . Never use this full power for listening long; it may permanently and irreversibly damage your hearing. **Too many young people are going deaf prematurely because they listen to headphones at too high a volume!**

Note that the amplifier is not suitable for use with electrostatic headphones. These need far more energy and are, therefore, normally driven straight from the power output amplifier.

The circuit

The design—see Fig. 2—is a pure symmetric one which can be split into an amplifier that works from a positive supply and one that operates with a negative supply. This design, used in the past in preamplifiers for moving-coil pick-ups, is known for its excellent performance at low drive levels. However, it appears to do

well also at higher signal levels. Its only drawback is the requirement for two input capacitors: one for the n-p-n stage and one for the p-n-p stage. But, since in a headphone amplifier the input impedance may be fairly high (here about 20 k Ω), these 2.2 μ F capacitors can be kept fairly small so that good-quality ones (poly-

ethylene or polypropylene) can be used.

The signal from the preamplifier is applied to R₁. This resistor and C₁ form a low-pass filter that limits the bandwidth of the incoming signal to about 400 kHz for a preamplifier output impedance of 600 Ω . The signal is then applied to amplifiers T₁ and T₂ via capacitors C₂ and

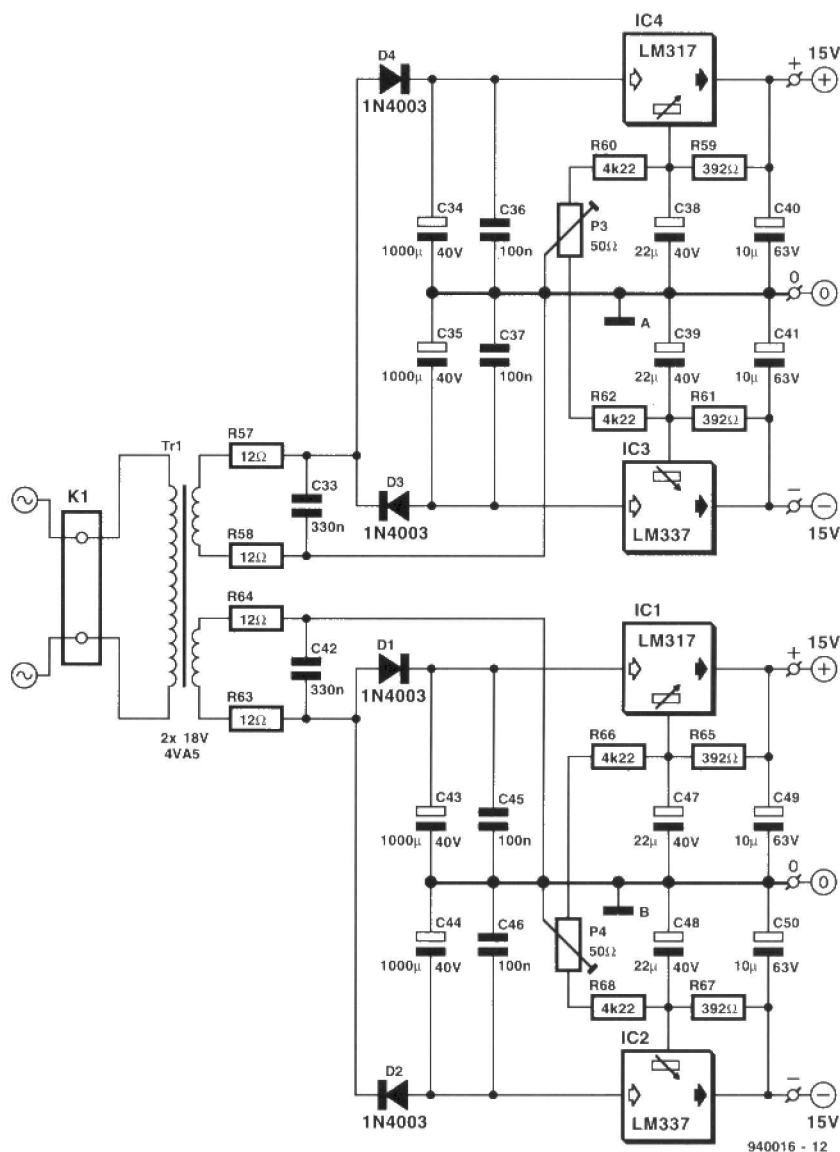


Fig. 1. Circuit diagram of the double power supply for the headphone amplifier.

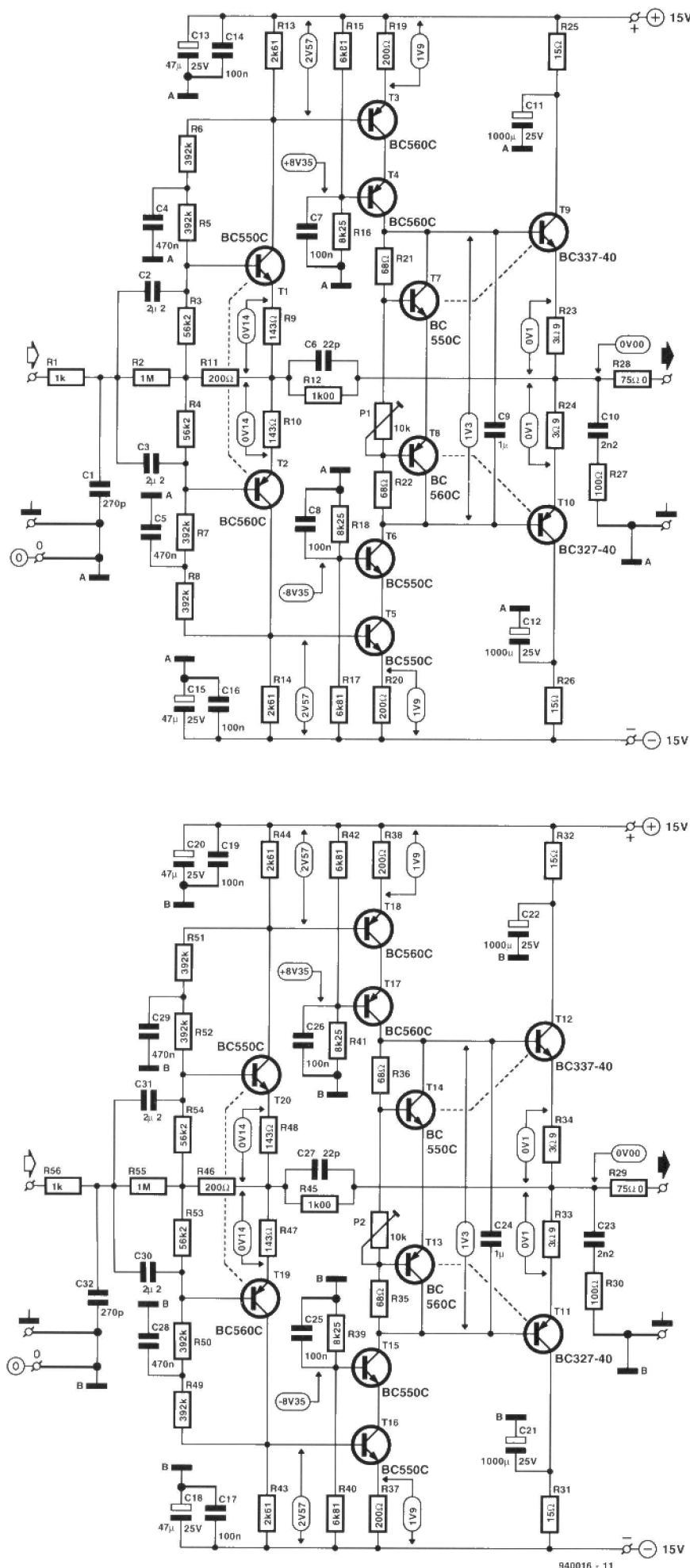


Fig. 2. Circuit diagram of the stereo headphone amplifier.

C₃. The amplification of these stages depends on the values of R₉, R₁₁, R₁₃ (in the case of T₁) and R₁₀, R₁₁, R₁₄ (in the case of T₂). Resistor R₁₁ is also part of the feedback loop of both transistors. The d.c. operating point is set by R₃-R₅-R₆ (T₁) and R₄-R₇-R₈ (T₂). These resistors also provide some local feedback.

The signals at the collector of T₁ and T₂ are fed to two cascode stages, T₃-T₄ and T₅-T₆ respectively. These stages provide wide-band amplification and impedance matching between the input transistors and the 'output' stage. A drawback of this arrangement is that output transistors can not be driven up to the supply voltage level, but that is not so important in the case of a headphone amplifier. The output transistors are driven by the collector signals of T₄ and T₆.

Transistors T₇ and T₈ form an adjustable 'zener' stage that sets the quiescent current. They are thermally coupled with T₉ and T₁₀ to ensure that the quiescent current remains reasonably stable during temperature variations in the output transistors.

The current through T₉ and T₁₀ is relatively high (25 mA), which is typical of Class A operation. The transistors are connected to the power supply via 15 Ω resistors, buffered by electrolytic capacitors C₁₁ and C₁₂.

Overall feedback is provided by R₁₂. Together with R₁₁, this resistor determines the amplification of the complete amplifier.

Network R₂₇-C₁₀ ensures a constant load at high frequencies.

The output impedance is 75 Ω (R₂₈). Power amplifiers normally have a low output impedance, but headphone amplifiers need a higher one. On the one hand, a low impedance ensures that the varying impedance of the headphones does not influence the output characteristic, and on the other hand, a resistor is necessary to protect the output stage against short circuits that occur every time the jack plug of the headphones is inserted into the socket. The specified value of R₂₈ was found to be a good compromise.

Since a stereo amplifier draws a fairly high current, the amplifier is given a dedicated power supply—see Fig. 1. To ensure strict separation of the channels, the mains transformer uses two secondary windings, each of which provides a symmetrical voltage of ±15 V. In this way, only two windings are needed for two isolated symmetrical voltages. Deriving symmetrical voltages from a single winding is possible with half-wave rectification: one diode uses the positive half-periods to charge an electrolytic capacitor, and another diode rectifies the negative half-periods. The use of relatively large electrolytic smoothing capacitors ensures that the ripple is kept small in spite of the half-wave rectification. Resistors R₅₇, R₅₈, R₆₃ and R₆₄ limit peak currents.

Integrated circuits IC₁–IC₄ regulate the output voltages, which are held at ± 15 V with the aid of resistance networks. Presets P₃ and P₄ enable setting exactly symmetrical voltages and setting the output of each output stage to exactly zero.

Construction

The complete amplifier is best built on the printed-circuit board in **Fig. 4**. This board consists of three parts: left-hand channel amplifier, right-hand channel amplifier and power supply. It is advisable to cut the board into three parts, so that the power supply can be fitted some distance from the amplifiers.

Population of the boards is straightforward, but make sure that the flat sides of transistor pairs T₁–T₂, T₇–T₉, T₈–T₁₀, T₁₉–T₂₀, T₁₂–T₁₄ and T₁₁–T₁₃ fit snugly together. Make two small rings of copper or aluminium and use these to clamp T₁ and T₂, and T₁₉ and T₂₉, securely together for good thermal contact. Fit lobe-finned heatsinks as used for TO-39 transistors around the other four pairs. These heatsinks should be slightly flattened before fitting them—see **Fig. 3**.

Interwiring is minimal: six wires for the supply voltages.

It is advisable to build the amplifier in a dedicated case, since most preamplifier will not have the space to house it. Fit the mains entry at the back of the case and the audio input sockets and the (6.3 mm) jack socket at the front. **Figure 5** shows how this must be wired.

When the construction is completed, set P₃ and P₄ to the centre of their travel. Connect a multimeter (200 mV direct voltage range) across R₂₃. Adjust P₁ until the voltage across R₂₃ is 100 mV. Do the same

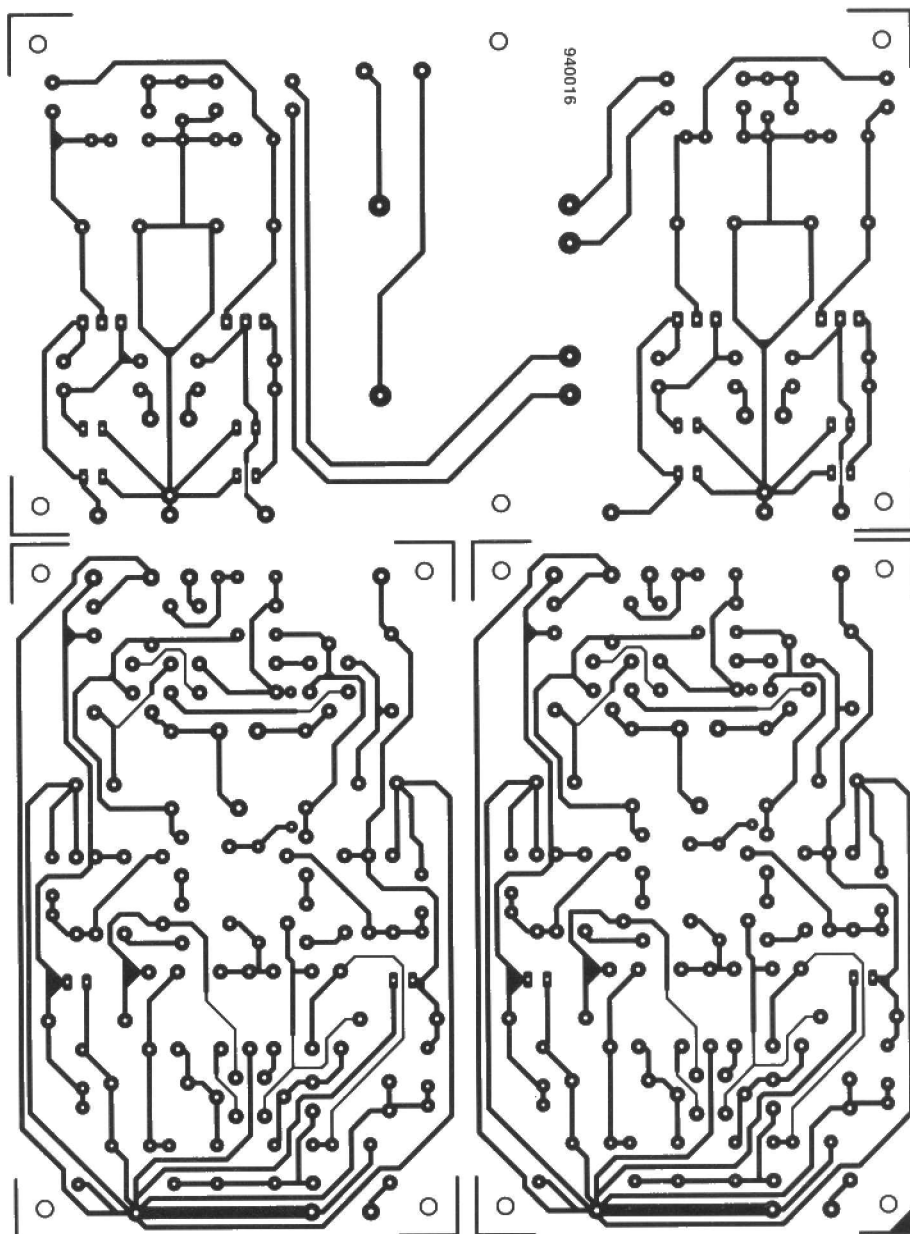


Fig. 4. The printed circuit board for the headphone

in the other channel with P₂ and R₃₄.

Connect the multimeter to the output of each amplifier in turn and adjust P₃ and P₄ respectively for zero reading of the meter (50 mV range).

Parts list

Resistors:

R₁, R₅₆ = 1 k Ω

R₂, R₅₅ = 1 M Ω

R₃, R₄, R₅₃, R₅₄ = 56.2 k Ω , 1%

Main parameters

Supply voltage	± 15 V
Current drain (each output stage)	about 30 mA
Quiescent current (each output stage)	25 mA
Output power	40 mW into 600 Ω
THD + noise (at 1 mW into 600 Ω)	<0.0015% (20 Hz–20 kHz)
THD at 1 kHz/1 mW	<0.0005%
Signal-to-noise ratio	>112 dB (A-weighted)
Input impedance	about 20 k Ω
Output impedance	75 Ω
Bandwidth	400 kHz
Slew rate (without R ₁ –C ₁)	350 V μ s ⁻¹
Allowable loads	33–600 Ω

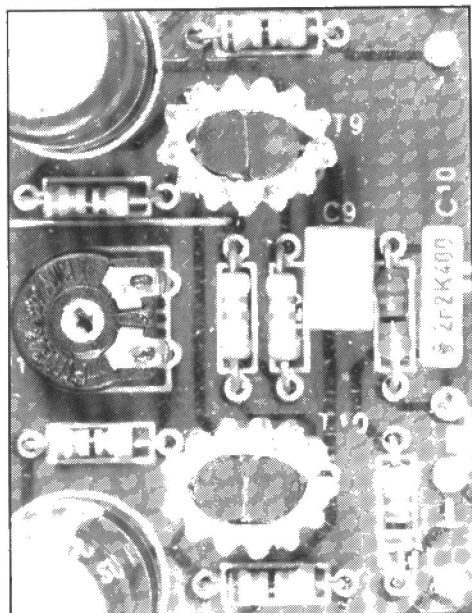
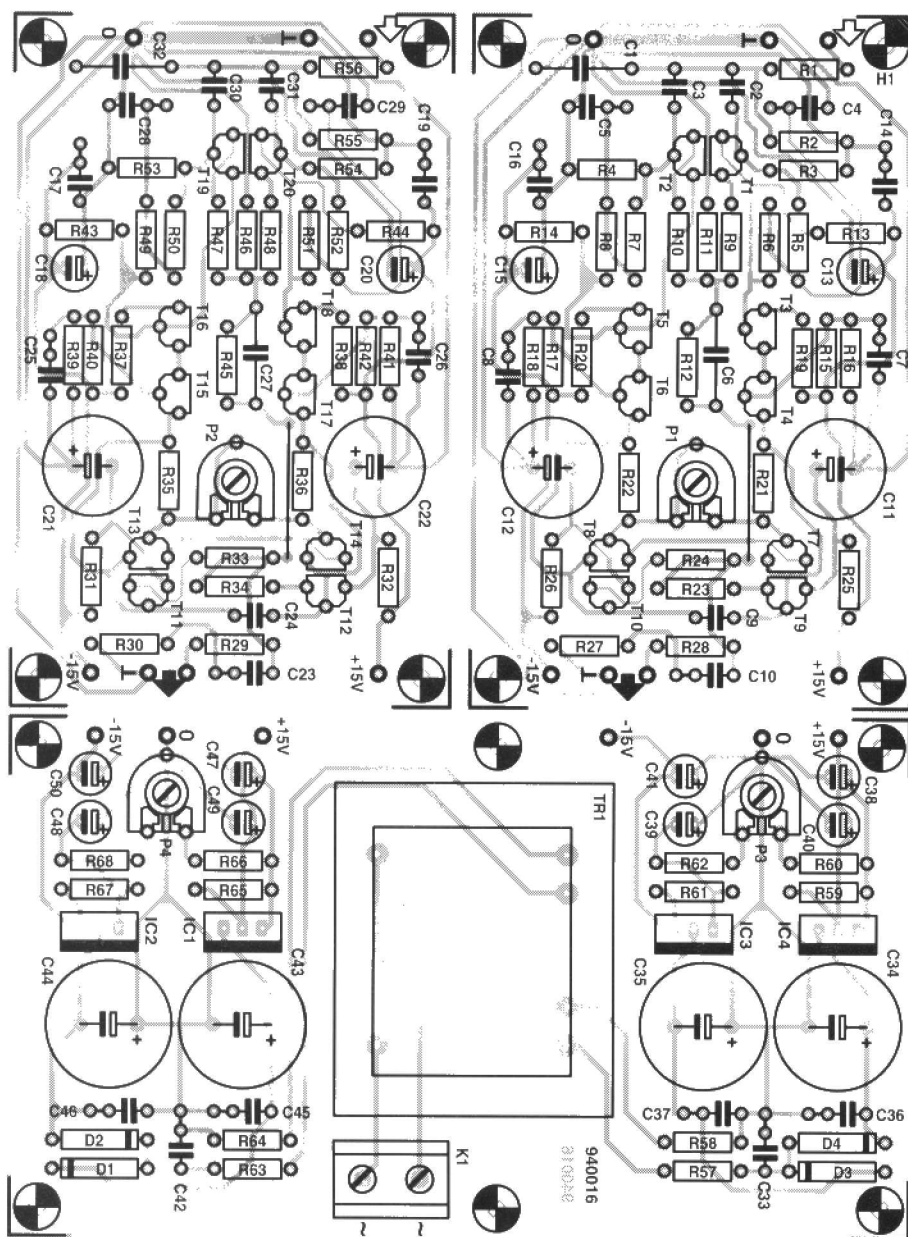


Fig. 3. This photograph shows how the pairs of transistors should be thermally coupled with the aid of a slightly flattened lobe-finned heatsink (TO39 size).

**Capacitors:**

$C_1, C_{32} = 270 \text{ pF}$, polystyrene
 $C_2, C_3, C_{30}, C_{31} = 2.2 \mu\text{F}$, 50 V, polythene or polypropylene, pitch 5 mm
 $C_4, C_5, C_{28}, C_{29} = 470 \text{ nF}$
 $C_6, C_{27} = 22 \text{ pF}$, polystyrene
 $C_7, C_8, C_{14}, C_{16}, C_{17}, C_{19}, C_{25}, C_{26}, C_{36}, C_{37}, C_{45}, C_{46} = 100 \text{ nF}$
 $C_9, C_{24} = 1 \mu\text{F}$, pitch 5 mm
 $C_{10}, C_{23} = 2.2 \text{ nF}$
 $C_{11}, C_{12}, C_{21}, C_{22} = 1000 \mu\text{F}$, 25 V, radial
 $C_{13}, C_{15}, C_{18}, C_{20} = 47 \mu\text{F}$, 25 V, radial
 $C_{33}, C_{42} = 330 \text{ nF}$
 $C_{34}, C_{35}, C_{43}, C_{44} = 1000 \mu\text{F}$, 40 V, radial
 $C_{38}, C_{39}, C_{47}, C_{48} = 22 \mu\text{F}$, 40 V, radial
 $C_{40}, C_{41}, C_{49}, C_{50} = 10 \mu\text{F}$, 63 V, radial

Semiconductors:

D_1 – $D_4 = 1\text{N}4003$
 T_1, T_5 – T_7, T_{14} – $T_{16}, T_{20} = \text{BC}550\text{C}$
 T_2 – T_4, T_8, T_{13}, T_{17} – $T_{19} = \text{BC}560\text{C}$
 $T_9, T_{12} = \text{BC}337$ –40
 $T_{10}, T_{11} = \text{BC}327$ –40

Integrated circuits:

$\text{IC}_1, \text{IC}_4 = \text{LM}317$
 $\text{IC}_2, \text{IC}_3 = \text{LM}337$

Miscellaneous:

$K_1 = 3$ –way terminal block, pitch 7.5 mm
 $\text{Tr}_1 = \text{mains transformer}$, secondary $2 \times 18 \text{ V}$, 4.5 VA
 PCB Ref. 940016 (see page 70)

amplifier should preferably be cut into three.

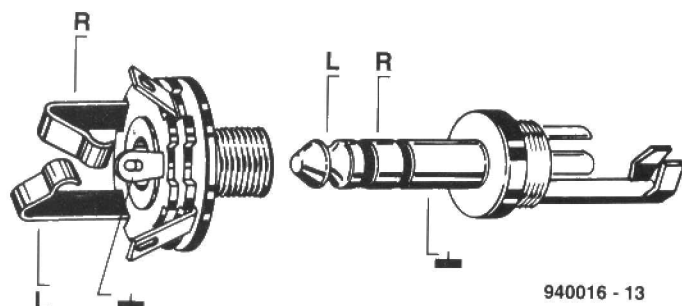



Fig. 5. Wiring details of a 6.3 mm jack plug and socket.

R_5 – R_8, R_{49} – $R_{52} = 392 \text{ k}\Omega$, 1%
 $R_9, R_{10}, R_{47}, R_{48} = 143 \Omega$, 1%
 $R_{11}, R_{19}, R_{20}, R_{37}, R_{38}, R_{46} = 200 \Omega$, 1%
 $R_{12}, R_{45} = 1.00 \text{ k}\Omega$, 1%
 $R_{13}, R_{14}, R_{43}, R_{44} = 2.61 \text{ k}\Omega$, 1%
 $R_{15}, R_{17}, R_{40}, R_{42} = 6.81 \text{ k}\Omega$, 1%
 $R_{16}, R_{18}, R_{39}, R_{41} = 8.25 \text{ k}\Omega$, 1%
 $R_{21}, R_{22}, R_{35}, R_{36} = 68 \Omega$
 $R_{23}, R_{24}, R_{33}, R_{34} = 3.9 \Omega$

$R_{25}, R_{26}, R_{31}, R_{32} = 15 \Omega$
 $R_{27}, R_{30} = 100 \Omega$
 $R_{28}, R_{29} = 75.0 \Omega$, 1%
 $R_{57}, R_{58}, R_{63}, R_{64} = 12 \Omega$
 $R_{59}, R_{61}, R_{65}, R_{67} = 392 \Omega$, 1%
 $R_{60}, R_{62}, R_{66}, R_{68} = 4.22 \text{ k}\Omega$, 1%
 $P_1, P_2 = 10 \text{ k}\Omega$ preset
 $P_3, P_4 = 50 \Omega$ preset

68HC11 PROCESSOR BOARD

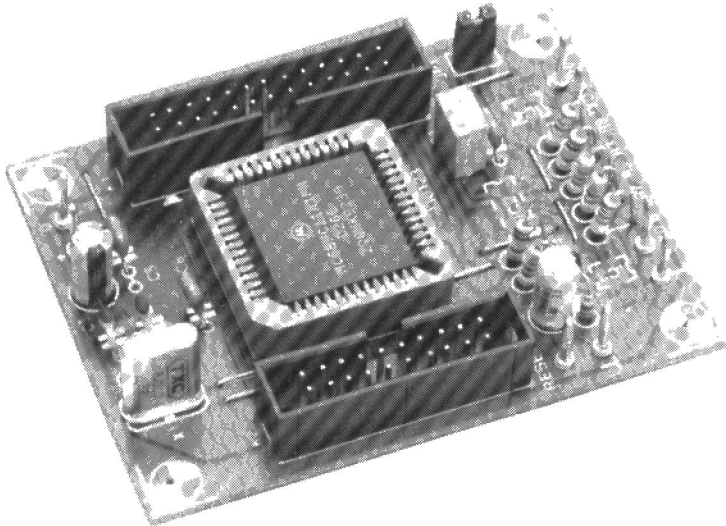The processor board discussed in this article is remarkably easy to program thanks to an EEPROM contained in the 68HC11 microcontroller. Expensive programmers or complex protocols are not required — all you need is a serial link with a PC. What's more, development software is available free of charge on two Motorola bulletin boards.



(actual size)

Design by J. Scherer and A. Hermann

MOTOROLA'S microcontroller product range is very extensive, offering processors which contain ROM, EPROM, or EEPROM as a standard feature. Also available on these ICs is a host of I/O ports. For the present project, the 68HC11 was chosen. The block diagram of this processor is given in **Fig. 1**. The CPU operates at a nominal bus frequency of 2 MHz, which equals the oscillator frequency divided by four. The processor is a 'fully static' type, which means that it can work at very low clock frequencies, even lower than 1 Hz.

The main sub-circuits of the controller are: a powerful 16-bit timer with internal prescaler; energy-saving halt and wait modes; a serial interface geared to driving I/O components; a serial communication bus; an 8-bit counter and a real-time interrupt circuit. Additionally, the 68HC11 used for the present project has an EEPROM memory of 256 bytes, and an 8-channel, 8-bit A-D (analogue-to-digital) converter. The structure of the processor will be reverted to in greater detail below.

The circuit

The power of the concept is immediately apparent from the sheer simplicity

of the circuit diagram shown in **Fig. 2**. Apart from a clock oscillator based around an 8-MHz quartz crystal (R_1 , C_1 , C_2 and X_1), a reset circuit (R_2 , C_3) and two opto-isolators (IC_3 and IC_4), there is only a handful of other components which couple the sub-circuits. Since only internal program memory is used, most of the 52 pins of the processor are available for control applications. This also brings out the main disadvantage of the concept: your program may not be larger than 512 bytes!

The processor's serial interface arranges the communication between the development system and the control computer. Via this interface, software is exchanged between the control computer and the controller board. If jumper JP_1 is not fitted, the processor automatically starts a small internal program after a reset. This routine waits for information to appear on the serial channel. Depending on the first byte transmitted on this channel (the byte must be FF_{11} in this application), the serial port is initialized at 1200 baud. The next 256 bytes transmitted are stored in the controller's RAM (random access memory). At the same time, they are returned to the computer via the TxD (transmit data) link. As soon as the 256th byte is re-

MAIN SPECIFICATIONS


Processor:	68HC11A1T
RAM:	256 bytes
EEPROM:	512 bytes
Clock frequency:	8 MHz
Software:	freeware on bulletin board
Communication:	via RS232 port
PCB:	single-sided
I/O:	22 lines available

ceived (i.e., the 257th including the FF_{11} header byte), the serial routine is automatically interrupted, and the processor starts to execute the program it has just finished storing in RAM. This 'bootstrap' method is very useful for testing small programs. There is, however, another application for this very special feature of the 68HC11. If the RAM is loaded with a program which arranges for received data to be stored into the 512-byte EEPROM, the controller can be programmed automatically. The program copied into the EEPROM in this way remains intact until it is overwritten by a new program.

After using the downloader to copy a user program into EEPROM, you obviously must be able to start this program. The following option has been provided by Motorola to achieve this: when the first byte which appears at the serial input is 00_{11} , the CPU starts to execute the program contained in EEPROM. This requires fitting jumper JP_1 . After a power-up reset, a positive going pulse transition appears automatically at the TxD output. This pulse is fed to the RxD input via electronic switches IC_{2a} and IC_{2b} (4066), and the closed jumper. Since electronic switch IC_{2b} blocks the serial connection if it is closed (RxD and TxD are then interconnected), the reset circuit breaks this connection after 15 ms, whereupon the serial interface is available again for 'normal' work.


Building the processor board

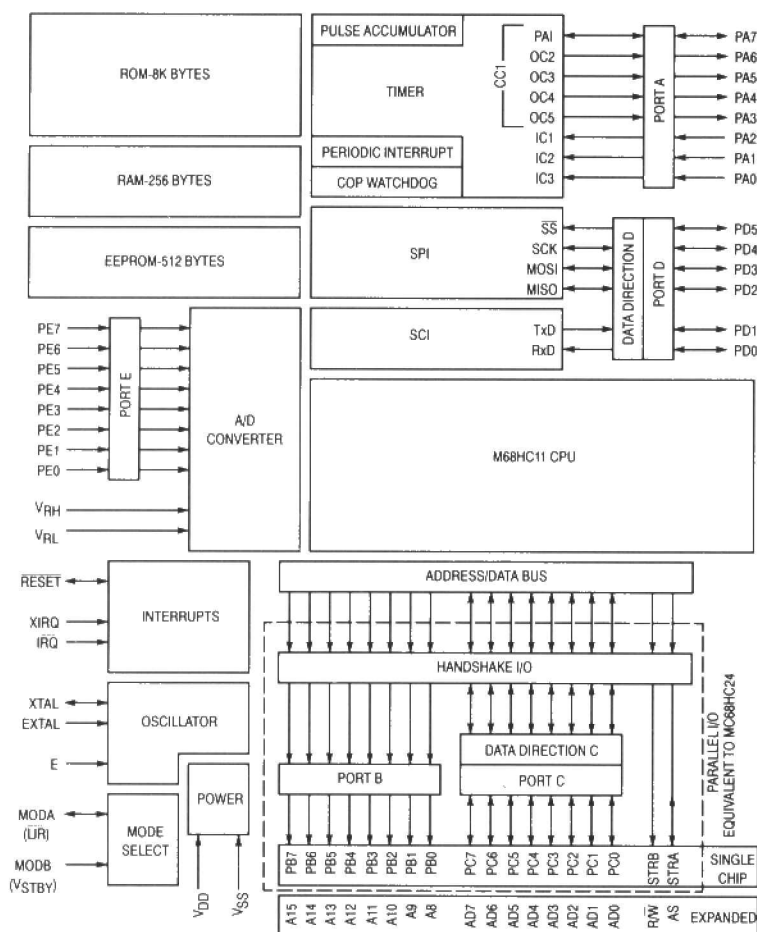As shown in **Fig. 3**, the printed circuit board designed for the 68HC11 processor board is compact and single-sided. The component mounting plan indicates that components are fitted at both sides of the board. Integrated circuits IC_2 , IC_3 and IC_4 are surface-



930123 - 11

Fig. 1. Block diagram of the 68HC11A8 processor. This IC is the 'generic' HC11 processor, from which the A1 version (used in the present project) is a smaller derivative.

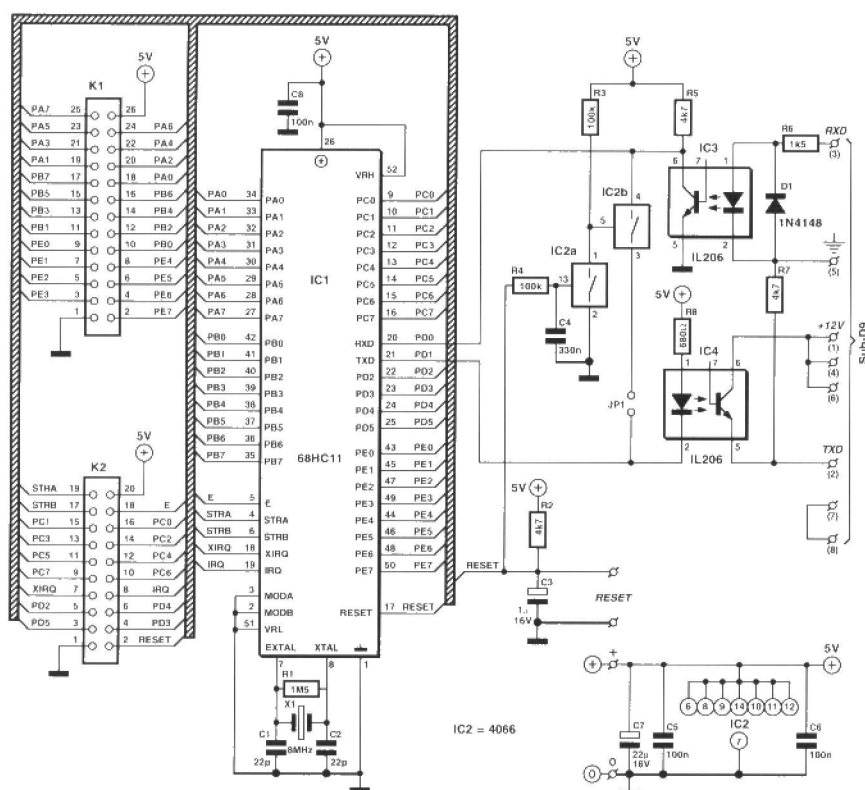

930123 - 12

Fig. 2. Circuit diagram of the 68HC11 processor board.

mount devices (SMDs), which are fitted at the track (copper) side of the board. Use thin solder wire, and a low-power (8 W) solder iron with a fine tip to mount these SMDs. Great care and precision should be exercised when fitting the 52-pin socket for the controller. Remember, a short-circuit is easily made, but difficult to trace later. After fitting the nine wire links, six solder pins, the jumper socket and connectors K₁ and K₂, the remaining components may be fitted on to the board. Keep an eye on the polarity of the electrolytic capacitors.

If difficult to obtain, the SMD versions of the opto-isolators may be replaced by normal size equivalents like the IL201, IL202 or the TIL111. A few short wires may be used to connect these parts to the respective solder spots originally provided for the SMD parts.

Software, the key to success

A vast collection of programs written for the 68HC11 is available free of charge from Motorola's bulletin boards in Munich, Germany, telephone (+49) 8992 103111, and in Austin, Texas, in the U.S.A., telephone (+1) 512 8913733. Fortunately for readers in the UK, the German bulletin board communicates in English. The following programs are needed for the present board:

for the downloader:
EEPROMIX.ASC
EEPROMIX.BOO
EEPROMIX.REC
E9CONFIG.BAS

for the assembler:
ASMHC11.COM
ASMHC11.HLP
CODES.ASC
OFFSET.ASC
RECBIN.COM
RECBOOT.COM
REG HC11.ASC

for the mini-debugger:
CONFIG.ASC
CONFIG.BAT
CONFIG.BOO
MINIBUG.ASC
MINIBUG.BOO
MINIBUG1.BAT
MINIBUG2.BAT

Downloading these programs from the bulletin boards is fairly easy. Dial up using a PC, a modem and a communications program, for instance, Procomm. Use the following line settings: 2400 baud, no parity, 8 databits, 1 stop bit. As soon as you are connected, press the ENTER key, where-

INTRODUCING THE 68HC11 FAMILY

Motorola's 68HC11 family of microcontrollers consists of a range of 8-bit processors marked by a number of powerful I/O functions. The family essentially consists of four members: 68HC11A0, 68HC11A1, 68HC11A7 and 68HC11A8. These processors are manufactured in high-speed CMOS technology, which guarantees fast operation in combination with low power. Depending on the exact IC type, the on-chip memory is an 8-KByte ROM, a 512-byte EEPROM, a 256-byte static RAM, or a combination of these.

The instruction set used to program these processors is an extended version of the one known for the 'older' 6800 or 6801. This enables software written for the 6800, 6801 or 6805 to be run on the 68HC11 without problems.

The family is 'built' around the 68HC11A8, a processor with an on-chip 512-byte EEPROM, and a 256-byte RAM. A number of other ICs were developed on this basis, as shown by the following table.

Type	EPROM	RAM (bytes)	EEPROM (bytes)	I/O lines	A-D channels
68HC11A0	-	256	-	22	8
68HC11A1	-	256	512	22	8
68HC11A7	8K	256	-	38	8
68HC11A8	8K	256	512	38	8

Depending on the programmer's selection, the CPU has either two 8-bit wide accumulators, or a single 16-bit accumulator. Furthermore, there are two 16-bit wide index registers. Up to six addressing methods are available, including direct, indirect and immediate. STOP and WAIT modes are available to reduce the power consumption of the processor when it is not active.

The chip also contains a 16-bit timer, which is fed by a software controlled prescaler. The addressing range of the external address bus is 64 KByte.

Memory

The largest option comprises the use of memory. The processor is capable of working with RAM, ROM, EPROM or EEPROM memory. The size of the ROM memory varies between 0 K and 32 KByte. The ROMs are mask-programmed with the application program during the production process. This is done by Motorola. Another important memory area is the RAM, whose size varies between 192 bytes and 1.25 Kbyte. The processor's RAM is static, and may be made non-volatile by backing up the supply voltage with the aid of a battery.

The size of the EPROM area varies between 4 and 32 KByte. This section of the memory is particularly valuable when developing prototypes, or producing low-volume series. For this purpose, Motorola also supplies an OTP (one-time programmable) version of the processor.

The last memory option is the EEPROM, whose size can vary between 0 and 2 KByte. The EEPROM memory area may be used to store calibration information, data logging data, security codes, etc. This makes the EEPROM eminently suitable for quasi-permanent storage of important data. Each 68HC11 with an on-board EEPROM also contains the hardware necessary to program this memory. External hardware is not required!

I/O options

The processor contains an 8-channel A-D converter. All processors feature a Serial Peripheral Interface (SPI), which allows special I/O components having the same interface to be connected in a simple manner. Furthermore, there is a Serial Communications Interface (SCI). The operation and layout of these interfaces is so 'clever' that they hardly load the CPU.

The SCI is a full-duplex UART (universal asynchronous receiver/transmitter) suitable for asynchronous communication. An internal baudrate generator supplies the UART clock frequency, which is derived from the microcontroller's clock signal. Both the transmitter and the receiver feature double buffering.

The SPI is a four-wire synchronous interface designed to enable high-speed communication between the processor and I/O components, or for inter-processor traffic. Only components having an SPI interface may be connected to this bus. Data may be transmitted and received simultaneously. The baudrate on the SPI is programmable.

The processors have a wide variety of I/O lines available for different control functions. These lines may be set up as inputs or outputs by programming the Data Direction Register contained in the processor. Most I/O ports have a buffer. A built-in watchdog timer alerts the processor if something goes wrong during the execution of a program. All processors may be used at a supply voltage of 3 V.

upon the Motorola bulletin board menu appears. Every screen tells you which key you should press to be able to continue. First, you are prompted to enter your name, personal password, and the transmission protocol used. After a few entries (which include questions regarding the bulletin boards you wish to see — answer 'N' most of the time), the welcome menu appears, followed by the main menu. Type 'D' to select downloading. The program will ask you for a file name, and then tells you whether or not that file is available on the system. Use a protected protocol such as XMODEM or YMODEM to do the actual downloading. This is necessary to make sure that transmission errors are detected and corrected.

Procomm starts downloading using the XMODEM protocol after pressing the 'page-down' key, and entering the name of the file you wish to receive. Files can be downloaded one after another. By contrast, in YMODEM mode, you make a list of all files you wish to download. If you are a frequent bulletin board user, will have no problems in getting what you want from the Motorola databanks. None the less, a few alternative possibilities: in the main menu, you may change the download protocol (if necessary) by pressing 'Y'. In the file menu, pressing 'L' allows you to call up the names of the available files. Next, you can select an 'area' by pressing '?', in this case, 'B' for HC11 freeware. The latter option is certainly worth trying, because a lot of interesting files are available.

Assuming that you have successfully downloaded the above programs, a couple of small modifications have to be made in E9CONFIG.BAS. Line 170 of this program contains a reference to EEPROGE9.BOO. This must be changed to read EEPROGIX.BOO. This program is the first to be copied into the RAM memory of the 68HC11 by the BASIC routine. Once started, EEPROGIX.BOO ensures that data which reaches the processor via the serial interface is stored into EEPROM. In this way, the processor is programmed with the application program.

Line 180 should contain a '1' or a '2' to point to the respective serial port on the PC, COM1: or COM2:. Line 200 enables the user to select between internal or external programming. The available options are 'I' for internal, 'X' for external, and 'V' for verify.

Line 210 should contain the name of the program to be sent to the controller. The extension for the program file name must be .REC, and the file should have the Motorola S19 format. The assembler which forms part of this development environment turns a source (.ASC) text file into S19 format (.REC).

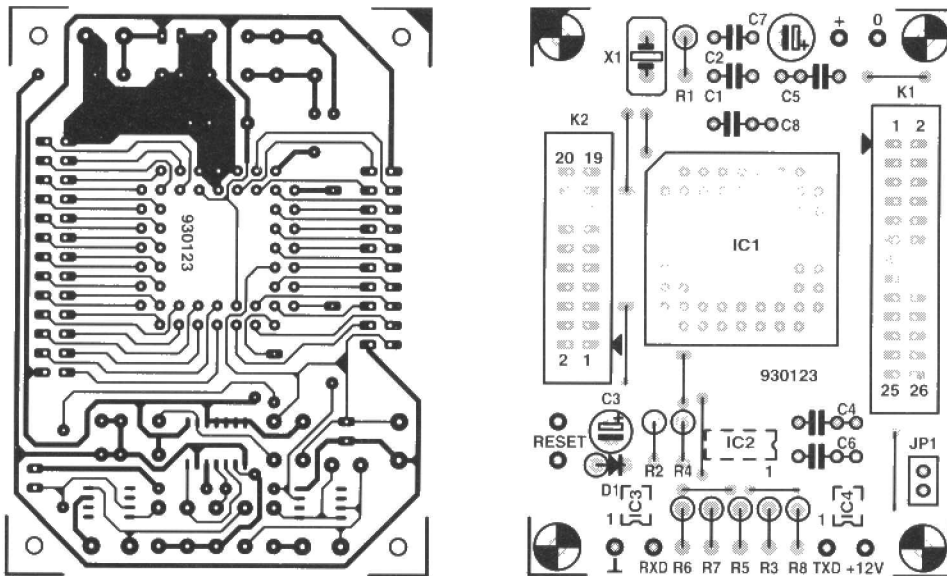


Fig. 3. Track layout (direct reading) and component mounting plan of the printed circuit board designed for the development system (PCB available ready-made through the Readers Services).

COMPONENTS LIST

Resistors:

R1 = 1M Ω
 R2; R5; R7 = 4k Ω
 R3; R4 = 100k Ω
 R6 = 1k Ω

Capacitors:

C1; C2 = 22pF
 C3 = 1 μ F 16V radial
 C4 = 330nF
 C5; C6; C8 = 100nF
 C7 = 22 μ F 16V radial

Semiconductors:

D1 = 1N4148
 IC1 = 68HC11A1 (Motorola)
 IC2 = 74HCT4066 (SMD)
 IC3; IC4 = IL206 or IL207 (SMD)

Miscellaneous:

JP1 = 2-way pin header
 K1 = 26-way boxheader
 K2 = 20-way boxheader
 X1 = 8MHz crystal
 1 52-pin PLCC socket
 8 PCB terminal pins
 1 Printed circuit board 930123 (see page 70)

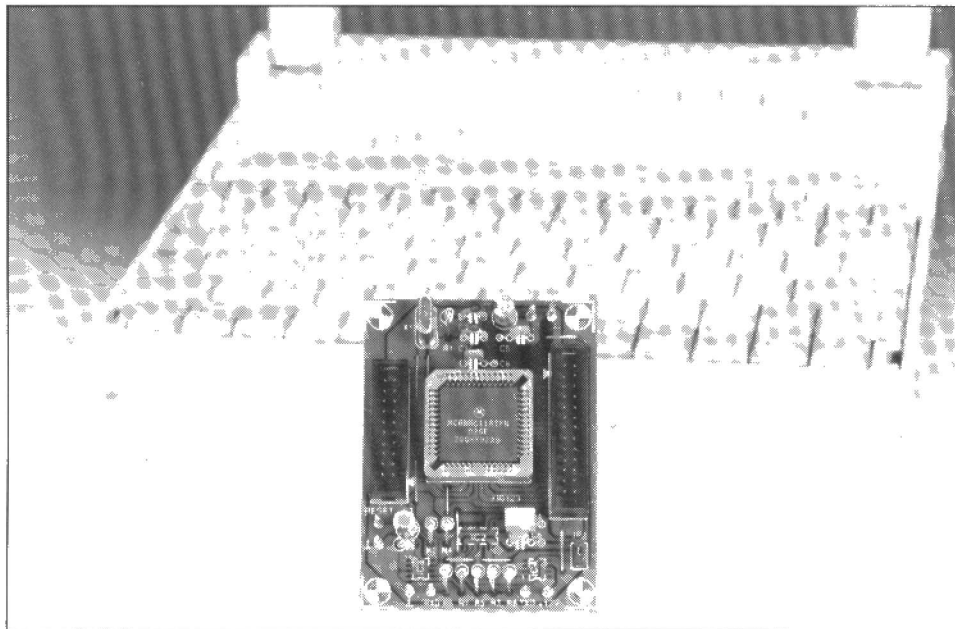


Fig. 4. Prototype of the processor board photographed in front of a portable MS-DOS PC used to download development software from Motorola's bulletin board, and to communicate with the 68HC11 board.

Lines 220 and 230 allow you to enter the desired baud rate, in this case, 1200. The last line which needs to be 'customized' is 1100. Replace the statement reading "T0% >100" with "T0% >5000".

If, after starting a program, an error report appears telling you that a WEND has been encountered without an associated WHILE, the WEND instruction in line 1100 must be moved to a new line.

Program development

If you have the hardware and the above utility programs, you can start developing programs for the 68HC11. Source code must be written in ASCII format, and comply with the rules given in the file ASMHC11.HLP. Connect the 68HC11 system to your PC's serial port via three wires, RxD, TxD and ground (note: in some cases, RxD and TxD must be swapped). Run

E9CONFIG.BAS under QBASIC to set up the file exchange and EEPROM programming. If required, the mini debugger may be copied into the controller's RAM. Thanks to the bidirectional connection between the PC and the processor board, you get a very good idea of the operation of the application program, and the type of errors it may contain.

For further reading:

HC11 MC68HC11A8 databook.
 AN1060 (application note) MC68HC11 Bootstrap Mode.
 MC68HC11 programmer's reference manual.

The above publications are available from the Motorola European Literature Centre, 88 Tanners Drive, Blakelands, Milton Keynes MK14 5BP.

80C535 HARDWARE/ASSEMBLER COURSE

PART 2: A-D CONVERTER AND WATCHDOG

Software by Dr. M. Ohsmann

Analogue-to-digital (A-D) converter

The analogue-to-digital converter contained in the 80C535 microcontroller is a complex unit. The structure is given in **Fig. 4**. The operation of the ADC is controlled via two special registers. The primary control register is located at address 0D8H, and is called ADCON. Bits 0, 1 and 2 in this register control the multiplexer connected ahead of the A-D converter proper. These bits determine which input line on port P6 is connected to the ADC input for the next conversion cycle. The ADC mode is controlled by bit 3 in the ADCON register. If the bit is set to 0, the ADC stops after each conversion. If the bit is set to 1, the ADC operates continuously.

Bit 4 in the ADCON register is a BUSY flag, which can only be read. When at 1, this bit indicates that a conversion is in progress. Shortly afterwards, it returns to 0. An A-D conversion lasts 14 machine cycles, or 14 μ s at a CPU clock frequency of 12 MHz. Once the BUSY flag is at 0, the result of the A-D conversion may be read from an SFR called ADDAT at address 09DH.

The ADC has a resolution of 8 bits. A special feature of the 80C535 is the reference voltage selection, which makes the ADC a very flexible unit. The 80C535 requires an external reference voltage of 5 V, which is connected via pin 12 (VAGND, reference voltage ground terminal) and pin 11 (VAREF, reference voltage positive terminal). For the maximum values of the reference voltage, please refer to the description of the 80C535 single-board computer, and the SAB80C535 datasheets.

For the experiments discussed in the present course, the SBC supply voltage (5 V) is used (as determined by jumpers JP3 and JP4), which means that no additional parts or external supplies are required. The internal reference voltage used by the ADC is derived from the external reference with the aid of a programmable voltage di-

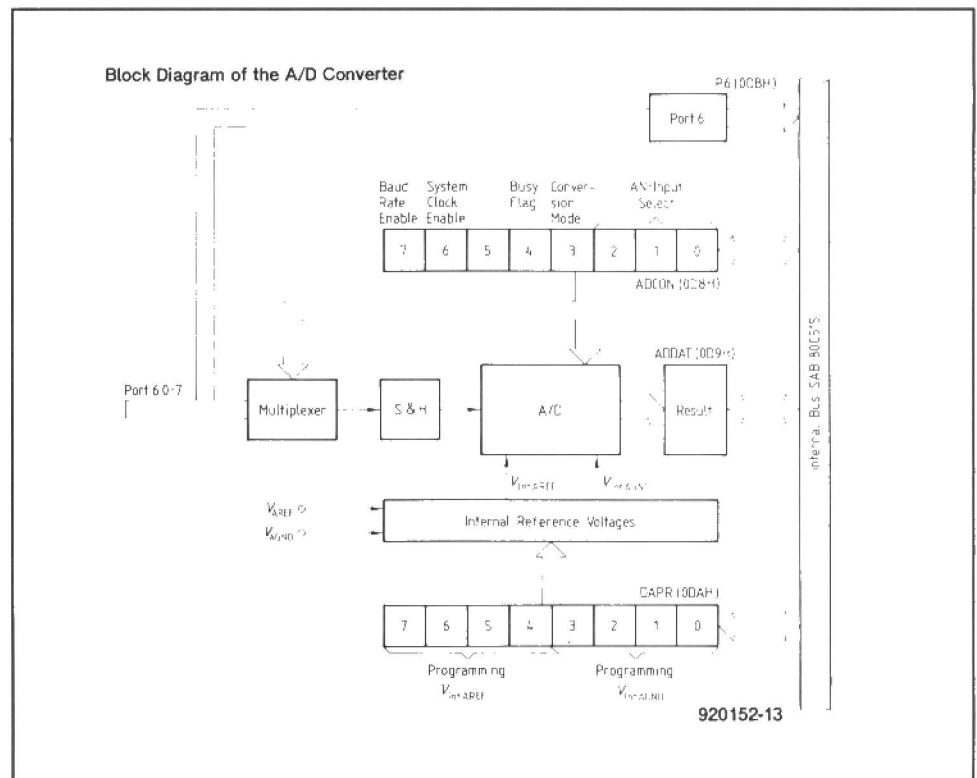


Fig. 3. Structure of the analogue-to-digital converter (ADC) contained in the 80C535.

vider, which is controlled via an SFR called DAPR at address 0DAH. The lower nibble of DAPR (bits 0 through 3) allow the lower limit, IVAGND, of the voltage converter window to be programmed, while the higher nibble (bits 4 through 7) programs the upper limit, IVAREF, of the window in steps of (VAREF/VAGND)/16. The values listed in **Table 3** are obtained at VAGND=0 V and VAREF=5 V.

The conversion window must have a minimum 'size' of 1 V. A window size of 0-5 V is obtained by loading DAPR with the value 0000 0000B. Similarly, a value of 1000 0100B results in a window size of 1.25-2.5 V. The 8-bit ADC uses the window so created, and divides it into 256 parts. Assuming a window size of 0-5 V, a voltage of 2.5 V at the A-D converter produces an output value of 128, or 080H, in the ADDAT register. The same input voltage would produce a value 255, or 0FFH, if a window size of 1.25-2.5 V

IVAGND IVAREF	Bits 3 to 0 (IVAGND)	Bits 7 to 4 (IVAREF)
0	0000	—
0.3125	0001	—
0.625	0010	—
0.9375	0011	—
1.25	0100	0100
1.5625	0101	0101
1.875	0110	0110
2.1875	0111	0111
2.5	1000	1000
2.8125	1001	1001
3.125	1010	1010
3.4375	1011	1011
3.75	1100	1100
4.0625	—	1101
4.375	—	1110
4.6875	—	1111
5.0	—	0000

Table 3. ADC window size depending on IVAREF and IVAGND programming.

were defined. Interestingly, a 10-bit converter may be realized by setting up four windows with a size of 1.25-V each. This will be reverted to below.

An A-D conversion operation is started as follows. First, write the desired window size into DAPR. Next, the ADC converts the voltage level on the channel selected via ADCON. Meanwhile, the BUSY flag is set. The result of the conversion is available for reading as soon as the BUSY flag has returned to 0. Incidentally, it is possible to convert alternating voltages (of up to 5 kHz according to the datasheets), but only if the source impedance of the voltage source driving the ADC input is smaller than 5 kΩ. This is necessary to enable the charge contained in the internal capacitance of the ADC to be reversed within the so-called LOAD time of three machine cycles. The lines of port P6 (analogue input lines) may also be interrogated directly at address 0DBH (not bit-addressable). For example, if you need only two analogue inputs, you have six

digital input lines left on P6.

Armed with the above knowledge, you should be able to understand the operation of the example program given at the end of the article on the 80C535 computer. A further example covering the use of the ADC in the 80C535 is discussed below.

A 10-bit A-D converter in software

The flow-chart of a program that turns the 8-bit ADC contained in the 80C535 into a 10-bit converter is given in Fig. 5, while the assembly language listing is shown in Fig. 6. The main program starts at the MAIN label. It switches the system clock on to port line P1.6 (this is done for test purposes), and sets variable Channel to 0. This variable contains the channel to be converted later by AD10BIT, the A-D converter subroutine proper. Next, the main program calls subroutine AD10BIT, which does the actual conversion, and stores the result into a

80C535 PROGRAMMING

You need the following to be able to follow the 80C535 hardware/assembler course:

Hardware:

- An 80C535 single-board computer as described in *Elektor Electronics* February 1994.
- An IBM PC or compatible with a serial port on COM1: or COM2:

Software:

- Courseware disk (5.25 inch, 360K MSDOS format).
- EMON52 system EPROM, fitted on 80C535 SBC.

The courseware disk and EPROM are available as a set under order code 6221. The disk is also available separately under order code 1811. For prices and ordering information, see page 70.

JOIN THE COURSE!

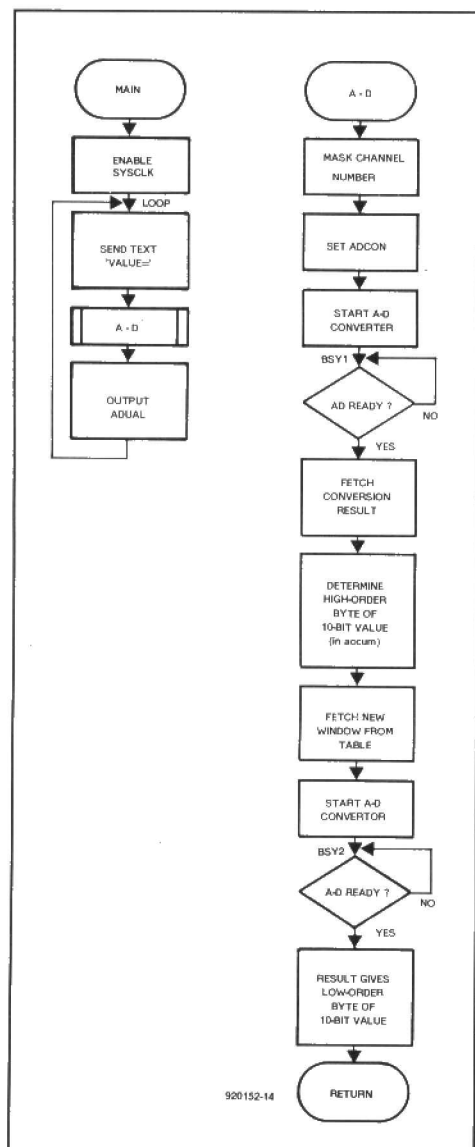


Fig. 5. Flow chart of 10-bit analogue-to-digital converter program.

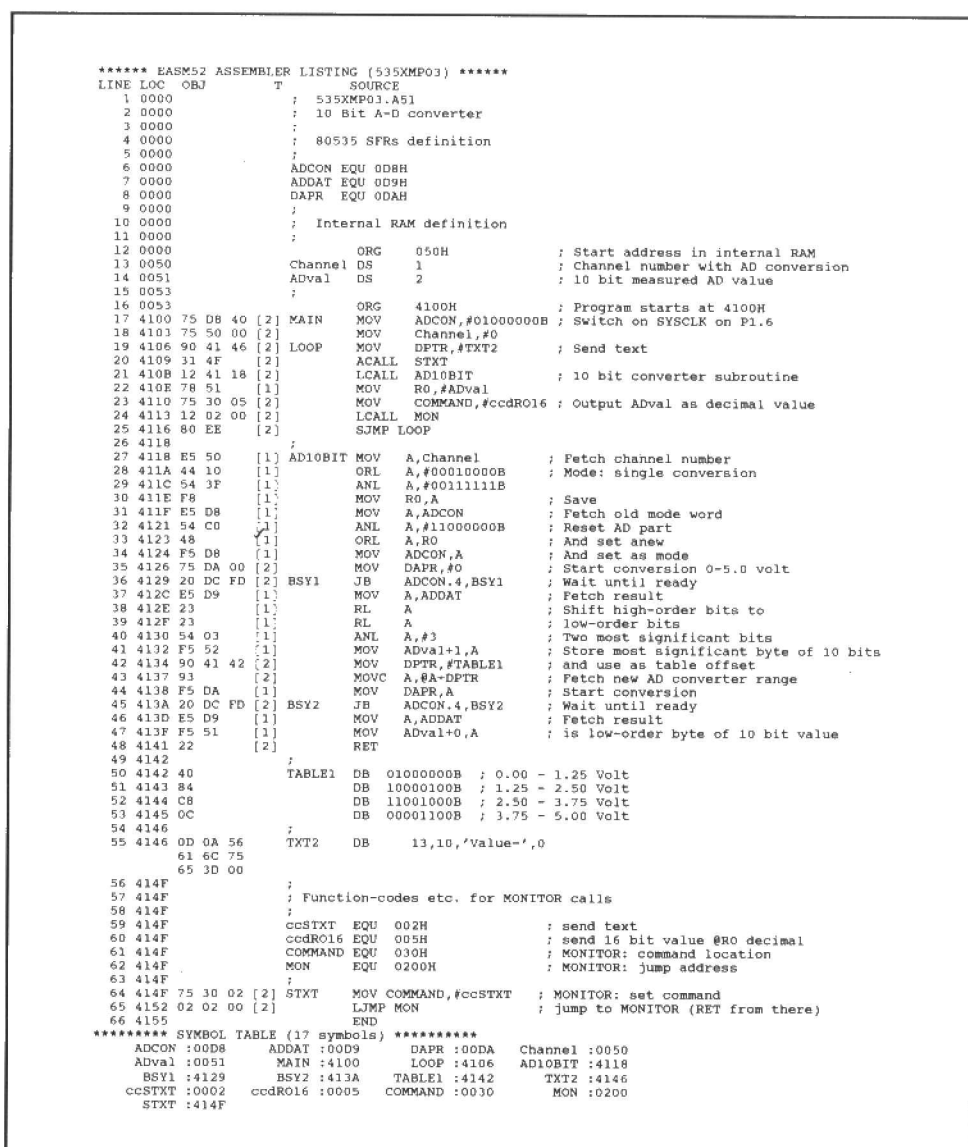


Fig. 6. By means of a clever division of the internal reference voltage into four sub-ranges, this program implements a 10-bit A-D converter (535XMP03 on course diskette).

16-bit variable called Adval, located in the internal RAM of the 80C535. The conversion result is output in decimal notation by the main program via the 16-bit decimal output subroutine in the EMON52 monitor. Once that is done, the main program starts again (at LOOP), and continues infinitely.

In subroutine AD10BIT, the ADC is first switched to single conversion mode, and to the channel indicated by the respective variable. When programming the ADC mode and channel number, care should be taken to mask bits 6 and 7 which control the baudrate generator and the system clock output. This is achieved by first fetching the contents of ADCON (line 31), and then changing the desired bits only with the aid of ORL and AND instructions. Next, the ADC (with a window size of 0-5 V) is started by the instruction in line 35. The loop in line 36 waits for the conversion operation to finish by constantly monitoring the BUSY bit. Once the conversion is done, the result is fetched. Bits 6 and 7 of the result indicate one of four ranges in which the input voltage lies. The four ranges are 0-1.25 V, 1.25-2.5 V, 2.5-3.75 V and 3.75-5 V. Two rotate instructions move these two bits to positions 0 and 1 in the accumulator. The word so created forms the higher order byte of the total result, and is stored at address ADval+1. Next, the A-D conversion is started using the relevant window. The control words to be loaded into DAPR for this purpose are contained in a look-up table (label: TABLE1). The two bits already established are used as indices for access to the table (lines 42 and 43). The second, 'fine', A-D conversion is started in line 44, and BUSY is monitored as before to wait for the conversion to finish. The result yields the lower-order byte of the total result, and is stored at address ADval+0. That completes the full 10-bit conversion.

The program processes the voltage at analogue input 0 (K6 pin 3), and outputs the voltage level as a decimal value via the V24 serial channel to the PC. Clearly, the A-D converter described is only suitable for very slowly varying voltages, since two conversions are performed, during which the input voltage must remain the same. Tests on several 80C535 controllers have shown that the internal ADC is subject to fairly large tolerances. For example, even a direct connection of the analogue input to VAREF failed to produce the full-scale value of 1023. Instead, a lower value was obtained, which also appeared to vary between the chips tested. For applications demanding high accuracy, it is, therefore, better to use an external converter.

```
***** EASM52 ASSEMBLER LISTING (535XMP04) *****
LINE LOC OBJ T SOURCE
1 0000 ;
2 0000 ; 535XMP04.A51
3 0000 ; Watchdog test
4 0000 ;
5 0000 ; 80C535 Special Function Registers
6 0000 ;
7 0000 IEN0 EQU 0A8H
8 0000 IEN1 EQU 0B8H
9 0000 ;
10 0000 ; Functions codes for MONITOR calls
11 0000 ;
12 0000 ccSTXT EQU 002H ; Send text
13 0000 COMMAND EQU 030H ; MONITOR: command location
14 0000 MON EQU 0200H ; MONITOR: jump address
15 0000 ;
16 0000 ; ORG 4100H ; First program starts at 4100H
17 4100 MAIN EQU $
18 4100 D2 BE [1] SETB IEN1.6
19 4102 51 0A [2] LOP ACALL SNDOK ; Send text OK
20 4104 80 FC [2] SJMP LOP ; and do again
21 4106 ;
22 4106 ; ORG 4200H ; Second program starts at 4200H
23 4200 MAIN2 EQU $
24 4200 D2 BE [1] SETB IEN1.6
25 4202 51 0A [2] LOP2 ACALL SNDOK ; Send text OK
26 4204 D2 AE [1] SETB IEN1.6 ; Reset watchdog
27 4206 D2 BE [1] SETB IEN1.6
28 4208 80 F8 [2] SJMP LOP2
29 420A ;
30 420A 90 42 13 [2] SNDOK MOV DPTR,#TXT0 ; Send report OK
31 420D 75 30 02 [2] MOV COMMAND,#ccSTXT ; MONITOR: set command
32 4210 02 02 00 [2] LJMP MON ; jump to MONITOR (RET from there)
33 4213 4F 4B 20 TXT0 DB 'OK',0
34 4217 00 END
***** SYMBOL TABLE (11 symbols) *****
IEN0:00A8 IEN1:00B8 ccSTXT:0002 COMMAND:0030
MON:0200 MAIN:4100 LOP:4102 MAIN2:4200
LOP2:4202 SNDOK:420A TXT0:4213
```

Fig. 4. Program 535XMP04 on your course disk teaches you the basics of the 80C535's watchdog.

Watchdog

To enable uninterruptable systems (also called no-break systems) to be realized more comfortably, the 80C535 features an on-board watchdog timer. This is basically a 16-bit counter which generates a processor reset if an overflow occurs. The watchdog is started by setting bit 6 in the IEN1 SFR at address 0B8H. Once started by software, the watchdog can not be halted. At a clock frequency of 12 MHz, a CPU reset is generated after 65,536 μ s. Obviously, that can only be prevented by the program resetting the watchdog timer to 0 in time. This is achieved by setting bit 6 in IEN0 and bit 6 in IEN1 by two successive (!) instructions.

A correctly operating program must always ensure that the watchdog is reset in time. Once the program crashes, it is likely that the watchdog is no longer reset. The result is that the entire CPU is reset by the watchdog, and the program is automatically restarted. It is possible to use software to determine whether or not a reset was triggered by the watchdog by examining bit 6 in the IPO register (address 09AH, not bit-addressable). If this bit is at 1, the CPU was reset by the watchdog.

The use of the watchdog in 80C535 assembly language is illustrated by the listing in Fig. 7. This program, 535XMP04.A51 (found on your course disk), shows a 'faulty' subprogram which does not reset the watchdog, and starts at address 4100H. A correctly working program starts at ad-

dress 4200H.

What happens if the program at 4100H is started after a reset caused by the watchdog? Care should be taken not to reset the watchdog by a periodically actuated interrupt routine. That is because the correctness of the interrupt routine is no guarantee that the main program is still running correctly. Implementing a truly 'no-break' system is quite taxing to the programmer!

What happens when the quartz crystal oscillator fails? No provision has been made in the 80C535 to detect this, and for the highest possible reliability it is, therefore, recommended to employ an external watchdog. The 80C537 has a few interesting features in this respect.

Next time: The 80C535's timers and their use in time measurement and pulsewidth modulation. Also a brief introduction into the use of interrupts.

Note: in response to readers' enquiries we would suggest the following suppliers of the SAB80C535 microcontroller:

• Electrovalue, Unit 3, Central Trading Estate, Staines TW18 4UX, England. Tel. (0784) 442253, fax (0784) 460320.

• C-I Electronics, P.O. Box 22089, 6360-AB Nuth, Holland. Fax: (+31) 45 241877 (IC supplied incl. free datasheet).

C-I Electronics also supply kits of the 80C535 computer. *tech. ed.*

MAINS SIGNALLING SYSTEM

PART 1: RECEIVER

Design by W. Hackländer & S. Furchtbar

Mains signalling is a method by which signals can be superimposed on mains wiring for the remote control of electrical equipment. It was first proposed by two Swiss inventors, Routin and Brown, who patented the method to control street lighting in 1896. The technique is well established and accepted in the USA, but in this country and Europe interest in it as a medium for communication has begun only in the late 1980s. This article deals with a system for use in home automation. The main advantages of the system are ease of installation, flexibility and relatively low cost (because it uses existing mains wiring).

The mains signalling system, which is controlled by a computer (**not** part of the system), may be used for switching or dimming lights, random switching of lights to give the house a 'lived-in' look while the occupant is away, switching all lights simultaneously in the event of danger, providing programmed or remote switching of electrical appliances, and many others. It is particularly helpful to disabled or handicapped people.

The system uses radio frequency (r.f.) signals superimposed on the very low frequency (v.l.f.) mains voltage. The r.f. signals are too high in frequency to interfere with the power supply and too low to affect radio and TV reception. They are, however, easily detected by a suitable receiver as described in this first part of the article. The modulation used is amplitude shift keying (ASK) which is facilitated by an IC specially developed for mains signalling systems.

The equipment complies with European Standard EN 50 065-1, which was approved by CENELEC (Comité Européen de Normalisation Electrotechnique—European Committee for Electrotechnical Standardization), of which the United Kingdom is a member.*

The system forms a link between a computer and mains-operated equipment—see **Fig. 1**. It consists of a transmitter (sometimes called controller) and one or more receivers. Each apparatus to be controlled via the system needs its own receiver, which switches it on and off. Up to 127 receivers may be controlled by one transmitter. The status of each receiver is monitored at the transmitter. The transmitter is an intelligent unit whose microprocessor provides the commands that are transmitted via the computer. Communication between the transmitter and the computer is via a standard RS232 link.

Design considerations

The circuit diagram in **Fig. 4** is drawn in two distinct parts: that at the left per-

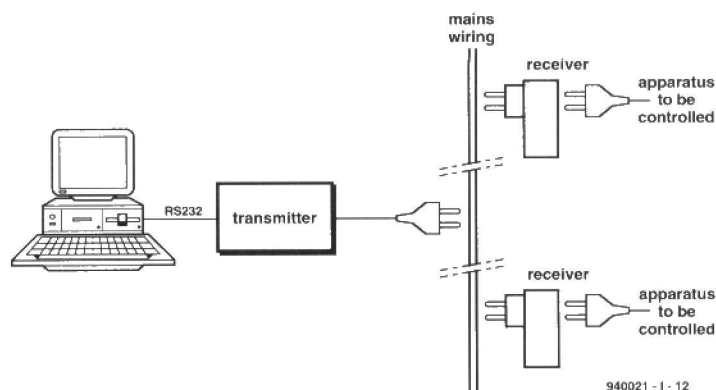


Fig. 1. Setup of a 2-receiver system. Up to 127 receivers may be accommodated.

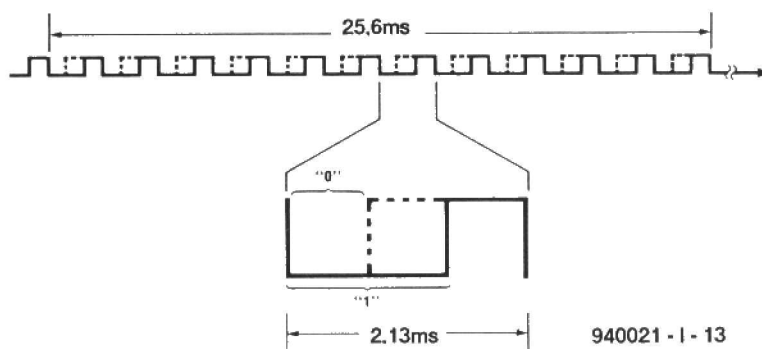


Fig. 2. Construction of the code used by the MM53200N.

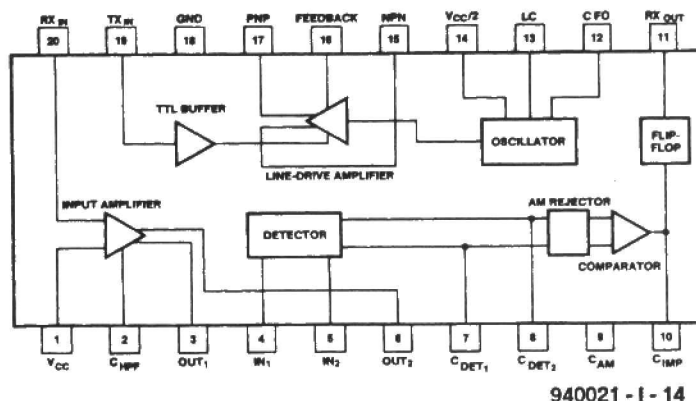


Fig. 3. Block schematic of modem IC NE5050.

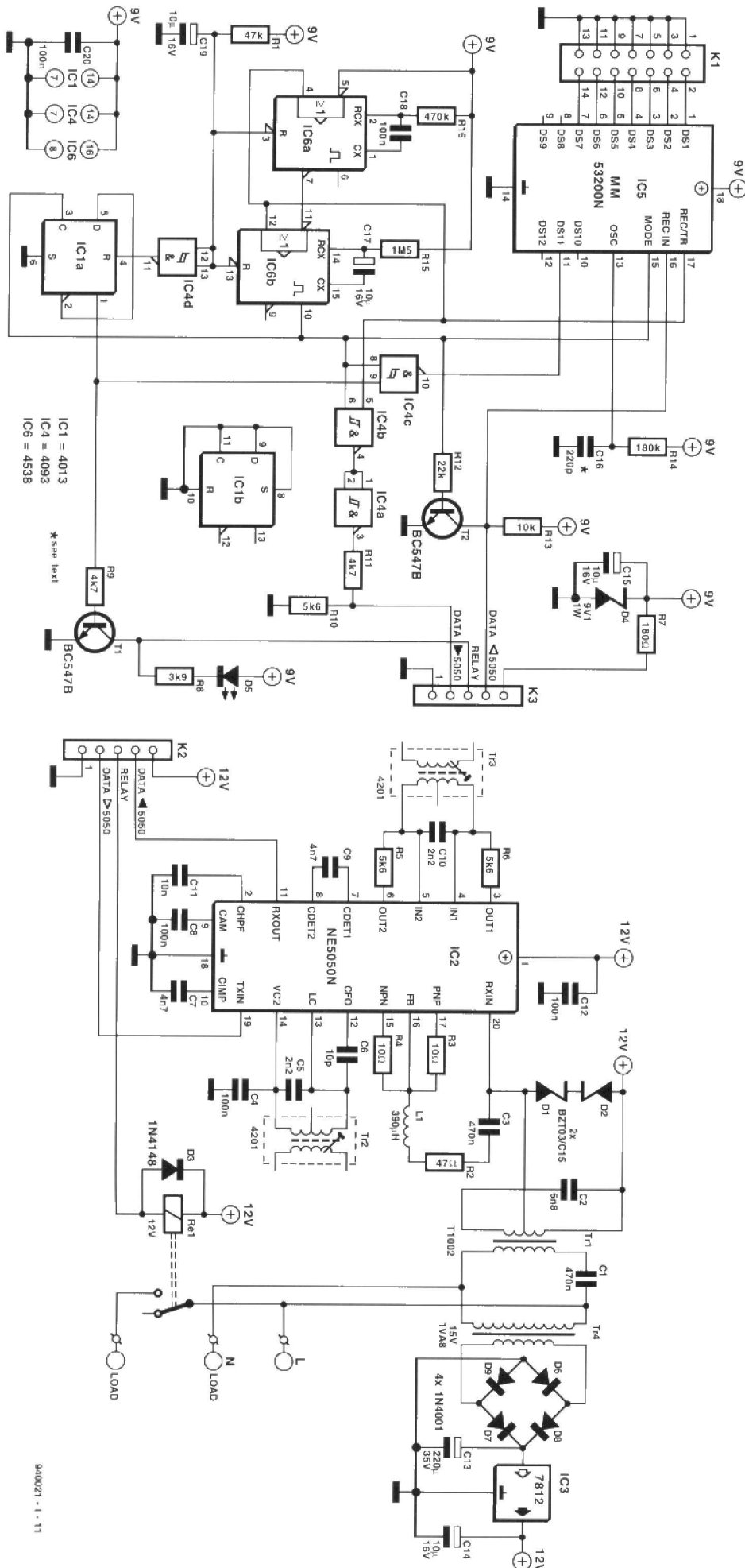


Fig. 4. Circuit diagram of the mains signalling receiver.

forms the data recognition and back reporting of data information; that at the right comprises the modulator/demodulator—modem—and the power supply.

The transmitter sends a train of 13 pulses along the mains wiring which are picked up by the receiver(s). Of the 13 pulses, eight are used for conveying the address. Each receiver compares the incoming code with its own address. If the two are identical, the relay in the receiver changes state. At the same time, the receiver sends back a pulse train containing its address and possibly having a '1' in the 11th position. This digit indicates to the transmitter that the receiver's relay is energized. This arrangement means that each receiver occupies two addresses in the system. Since eight bits are used, the total number of receivers is limited to 127, which should not present a problem in most cases.

Address recognition is performed by IC₁, a Type MM53200 from National Semiconductor. This IC contains an oscillator, an encoder and a decoder. In the transmit mode, the IC converts the 12 logic levels at its data inputs, DS₁–DS₁₂, into a train of 12 pulses (plus a start pulse). The pulse repetition rate (p.r.r.) is determined by network R₁₄–C₁₆. The width of each pulse determines the logic level—see Fig. 2. The encoding used guarantees reliable data transfer even when the signal lines are subject to interference.

In the receive mode, the incoming signal (12 data pulses plus start pulse) is compared to the local code in a sequential manner. If there is an error, the system is reset and begins its comparison on the next pulse. If all 12 bits are received correctly, a 'valid' signal is generated. This signal clears one counter and clocks another. The latter (3-stage) counter counts the 'valid' pulses. When and only when four correct pulse trains, with a maximum pulse spacing of 142 ms, have been received, does the transmit/receive output go low.

Data-select pins 1–9 of IC₁ are connected to ground via jumpers on header K₁. In the IC, the pins are connected to pull-up resistors, ensuring that each of them is automatically at high logic level if there is no jumper to earth. Consequently, the jumpers at these pins enable addresses 0–127 to be set. Address 0 corresponds to no jumpers and address 127 to seven jumpers at K₁.

The clock of IC₁ has been fixed at about 45 kHz by the time-constant R₁₄–C₁₆. At that frequency, transmitting a complete pulse train takes about 25.6 ms.

When the power is switched on, monostables IC_{6a} and IC_{6b}, as well as bistable IC_{4d}, are reset via R₁–C₁₉. The output of IC_{6b} is then low, so that IC₁ is in the receive mode (via mode input pin 15). In this situation, T₂ is cut off, so that the signals from the modem section are transferred to pin 16 of IC₁. Pin 1 of bistable IC_{1a} is low, so that T₁ is cut off and there

is no supply to the relay. Diode D_1 is off.

When four times the correct code has been received, the transmit/receive output goes low. If no more valid data are received, this output changes state, which causes IC_{6a} and IC_{6b} to be triggered. The output of IC_{6b} clocks bistable IC_{1a} , causing this stage to change state. This results in T_1 being switched on, so that the relay is energized. Also, D_1 lights. The mono period of IC_{6a} is very short. Since the inverting output of this multivibrator is linked to the trigger input of IC_{6b} , that stage will no longer react to new incoming trigger pulses (it will also not be triggered by the data which the receiver is about to send back).

At the instant IC_{1a} changes state, IC_{6b} reverses the level at pin 15 of IC_1 , which results in the IC sending its own address code. Gate (NAND) IC_{4c} provides the logic level for DS11 (pin 11). When the output of IC_{6b} is high, the output of the gate depends on the output state of IC_{1a} and thus on the status of the relay. If the gate provides a '0', the relay is energized; if a '1', the relay is not powered. In this way, the transmitter receives information as to the status of the receiver.

The pulse train from IC_1 is generated a few times until the mono time of IC_{1b} has elapsed. During this time, T_2 is on so that no transmitted signals can be sent back to pin 16 of IC_1 . After this period, IC_1 switches back to the receive mode.

Modulation/demodulation

Modulation and demodulation of the digital signals is provided by line driver IC_2 , a Type NE5050 from Philips/Sigmetics specially developed for use in mains signalling systems. The block diagram of this device is shown in **Fig. 3**. The IC uses amplitude shift keying in which the two

digital levels are transmitted at different amplitudes (strictly speaking, maximum amplitude and no amplitude).

Capacitors C_5 , C_6 and transformer Tr_2 determine the frequency of the send oscillator (here, 100 kHz). The carrier wave

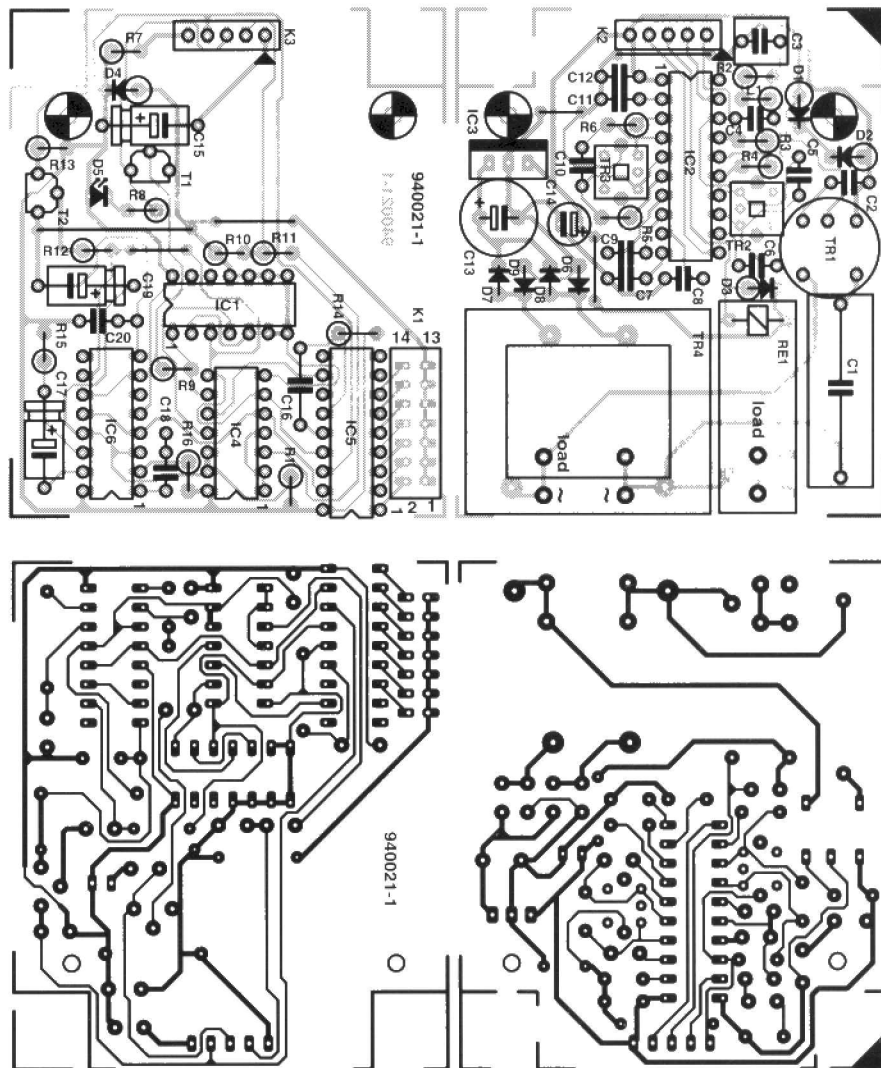


Fig. 5. Printed circuit board for the mains signalling receiver.

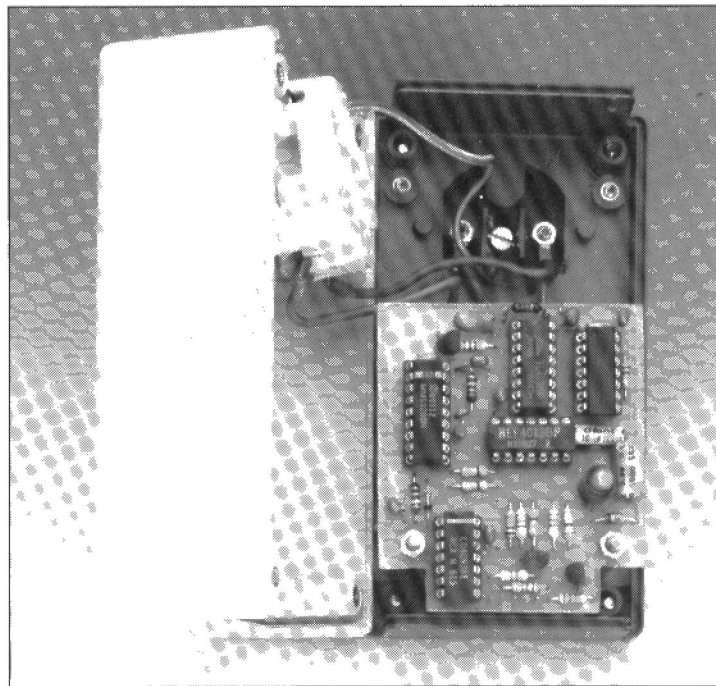
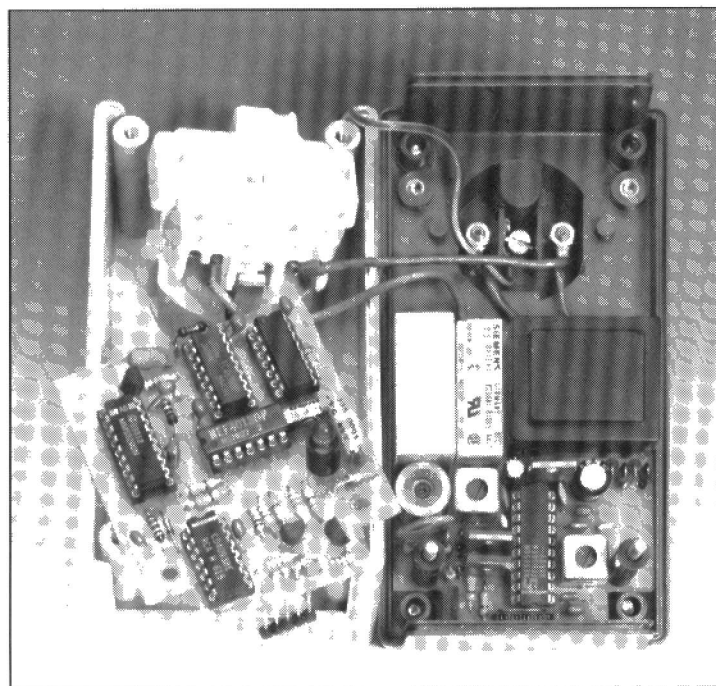


Fig. 6. Illustration of how the board should be fitted into the enclosure: first fit the modem board to the bottom of the case with threaded (or partly threaded) spacers (left-hand photo); then fit the digital board on top of the spacers (right-hand photo).

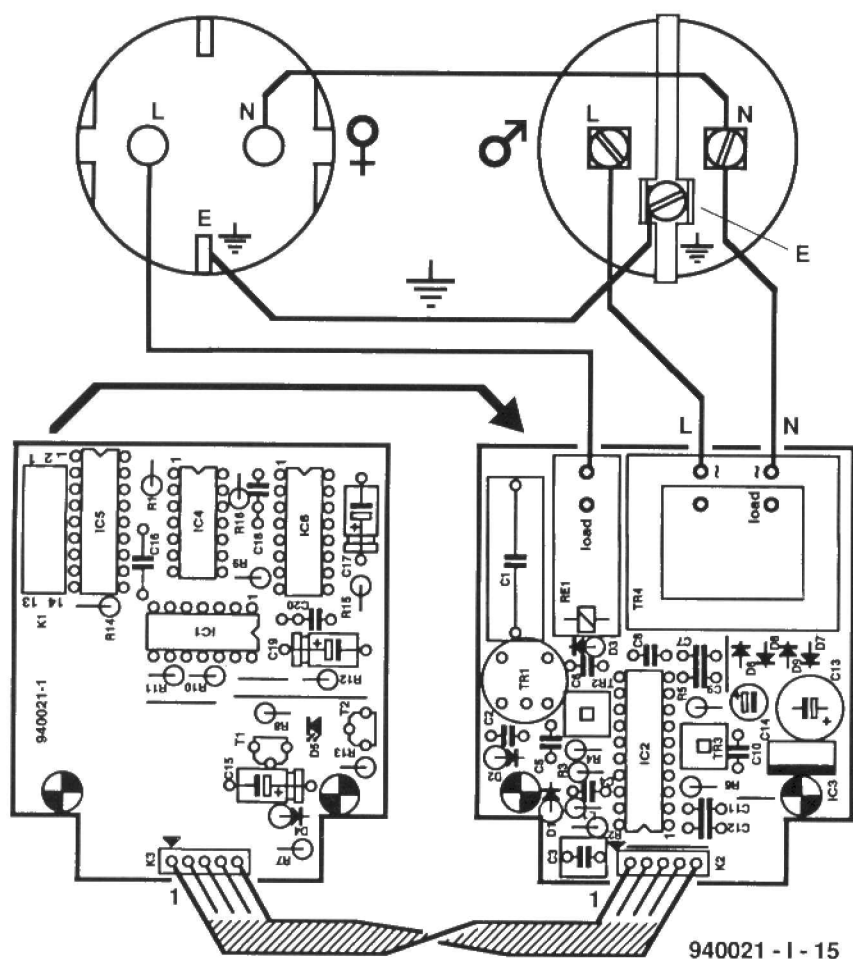


Fig. 7. Wiring diagram of the boards and plug and socket arrangement.

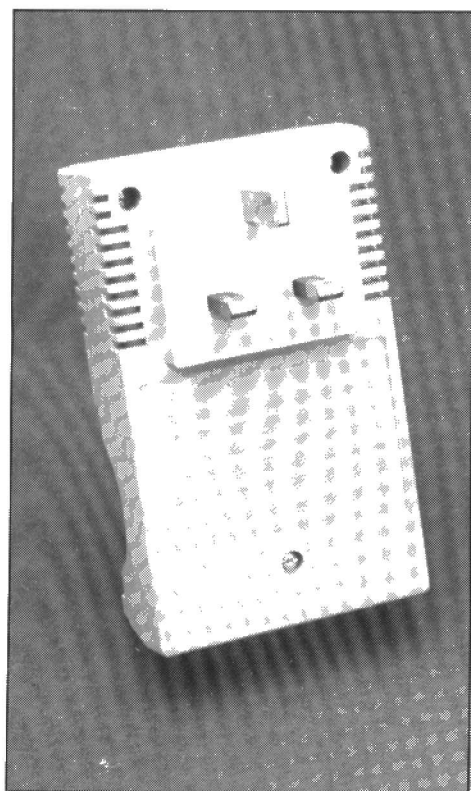


Fig. 8. Case fitted with standard UK plug and socket.

generated by the line driver is switched on and off by the digital signal applied to its pin 19. The output, pins 15 and 17, of IC₂ is applied to the mains wiring via R₃, R₄, low-pass filter L₁ (which suppresses high harmonics), impedance matching resistor R₂, coupling capacitor C₃ and isolating transformer Tr₁.

Capacitor C₂ and Tr₁ form a band-pass filter with a central frequency of about 110 kHz.

Capacitor C₁ provides severe attenuation of the 50 Hz mains signal.

Series-connected diodes D₁ and D₂ limit the received signal and suppress interfering spikes on the mains voltage. The specified types are special transient-voltage-suppression diodes that react very fast to such spikes: they should not be replaced by different types.

The received (and possibly limited) signal is applied to pin 20 and then to a band-pass filter in the IC, whose upper cut-off frequency is fixed at 300 kHz; the lower cut-off frequency is determined by the value of C₁₁.

A further band-pass filter, consisting of C₁₀ and Tr₃, is provided between the input amplifier and the detector (in IC₂).

The signal is then applied to a low-pass

filter of which C₉ is a part, and finally to an AM rejection stage, where any residual component of the 110 kHz carrier wave is removed. The average direct voltage is stored in C₈.

After passing through the comparator, the signal is enhanced by C₇ (which removes any remaining spikes) and an internal bistable (which smooths its edges). Finally, the data are sent to IC₁₁ via pin 11.

The power supply is straightforward. A 1.8 VA transformer, Tr₄ provides 15 V a.c. which, after rectification in D₆-D₉ and smoothing by C₁₃, is held at 12 V by IC₃.

Since IC₁, IC₄, and IC₆ can not tolerate a 12 V supply, network R₇-D₄ lowers the supply to these ICs to 9 V.

Construction

The receiver must be built in a special, high-impact ABS enclosure with an integral mains plug at the front and a mains socket at the back; the type of plug and socket depends on the country you live in. The photograph in Fig. 8 shows a standard UK type; American and European types are also available (see Parts List). The insulating properties of the enclosure must be first class, because transformer Tr₁ may not provide full mains isolation.

The circuitry is built on two printed circuit boards as shown in Fig. 5. One of these houses the modem IC, transformers and relay and the other the digital circuits. Remove two corners of each of the boards to ensure that the lid will still fit on the case.

Because of the limited available space, mount all resistors and zener diodes upright. Use sockets for all ICs.

Keep all connecting wires at the track side of the digital board short, otherwise the finished board will not fit in the case.


Place the LED a few millimetres above the board, so that it fits nicely in a 5 mm dia. hole drilled in the lid of the case. For safety reasons, **do not** use a 3 mm LED.

The two boards are interconnected via a length of 5-core flat-cable. Insert this cable in the holes at the track side of the upper board.

Solder three pins at the track side of the modem board for connecting the mains cable. In the prototype, flat pins with small ridges that sit securely on the board were used. However, standard round pins bent at right angles and securely soldered in place may also be used.

Interconnect the two mains connections in the case with the relevant pins underneath the mains transformer on the modem board with insulated circuit wire (5-10 cm long) terminated into appropriately sized solder tags. Connect the remaining pin underneath the relay with the L(ive) pin of the case socket. Interlink the earth terminals on the plug and socket. All these connections are shown in Fig. 7. Fit all mains connections on the boards

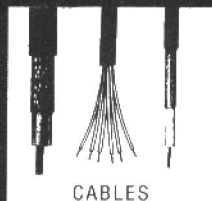Call us now! We have the widest range of components available - At competitive prices!




CABLES




CAPACITORS




VIDEO HEADS

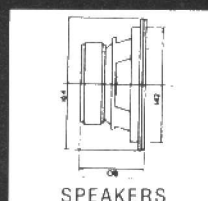

SPEAKERS

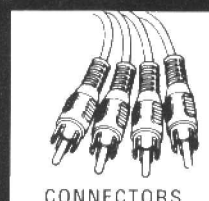

CONNECTORS

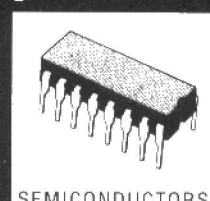

SEMICONDUCTORS

CRICKLEWOOD
ELECTRONICS

Cricklewood Electronics Ltd, 40 Cricklewood Broadway, London NW2 3ET.
Telephone: 081 452 0161 Faxsimile: 081 208 1441

All Major Credit Cards Accepted



with insulating sleeve.

When the boards are completed, install the modem board at the bottom of the case and fasten it with two 25 mm (1 in.) partly threaded spacers. Next, mount the other board on to the spacers and fix it into place with two M3 bolts. This board should be seated immediately above the relay. If necessary, fit shims on to the spacers to increase the distance between the board and relay slightly. The photographs in **Fig. 6** show how the boards are located in the case.

Parts list

Resistors:

$R_1 = 47 \text{ k}\Omega$
 $R_2 = 47 \Omega$
 $R_3, R_4 = 10 \Omega$
 $R_5, R_6, R_{10} = 5.6 \text{ k}\Omega$
 $R_7 = 180 \Omega$
 $R_8 = 3.9 \text{ k}\Omega$
 $R_9, R_{11} = 4.7 \text{ k}\Omega$
 $R_{12} = 22 \text{ k}\Omega$
 $R_{13} = 10 \text{ k}\Omega$
 $R_{14} = 180 \text{ k}\Omega$
 $R_{15} = 1.5 \text{ M}\Omega$
 $R_{16} = 470 \text{ k}\Omega$

Capacitors:

$C_1 = 470 \text{ nF}$, 250 V a.c., 630 V d.c.
 $C_2 = 6.8 \text{ nF}$, MKT, pitch 5 mm
 $C_3 = 470 \text{ nF}$, MKT, pitch 5 mm
 $C_4, C_8, C_{12}, C_{18}, C_{20} = 100 \text{ nF}$, MKT, pitch 5 mm
 $C_5, C_{10} = 2.2 \text{ nF}$, MKT, pitch 5 mm
 $C_6 = 10 \text{ pF}$
 $C_7 = 4.7 \text{ nF}$, MKT, pitch 5 mm

$C_9 = 4.7 \text{ nF}$
 $C_{11} = 10 \text{ nF}$
 $C_{13} = 220 \mu\text{F}$, 35 V, radial
 $C_{14} = 10 \mu\text{F}$, 16 V, radial
 $C_{15}, C_{17}, C_{19} = 10 \mu\text{F}$, 16 V
 $C_{16} = 220 \text{ pF}$, polystyrene

Inductors:

$L_1 = 390 \mu\text{H}$

Semiconductors:

$D_1, D_2 = \text{BZT03/C15}$ (Philips)
 $D_3 = 1\text{N}4148$
 $D_4 = \text{zener}$, 9.1 V, 1 W
 $D_5 = \text{LED}$, red, 5 mm
 $D_6\text{--}D_9 = 1\text{N}4001$
 $T_1, T_2 = \text{BC547B}$

Integrated circuits:

$\text{IC}_1 = 4013$
 $\text{IC}_2 = \text{NE5050N}$ (Philips/Signetics)

$\text{IC}_3 = 7812$
 $\text{IC}_4 = 4093$
 $\text{IC}_5 = \text{MM53200N}$ (National Semiconductor)
 $\text{IC}_6 = 4538$

Miscellaneous:

$K_1 = 14\text{-way header}$
 $K_2, K_3 = 5\text{-core flatcable}$ (5–10 cm)
 $\text{Re}_1 = \text{relay}$, 12 V, 1 make contact, for PCB mounting
 $\text{Tr}_1 = \text{T1002}$ (Toko 707VXT1002N)
 $\text{Tr}_2, \text{Tr}_3 = 4201$ (Toko LPCS4201)
 $\text{Tr}_4 = \text{mains transformer}$, 15 V, 1.8 VA for PCB mounting
 Enclosure, 120×65×60 mm (approx) with integral plug and socket (see text). Suitable cases to UK, USA and European standards are available from Bopla (in UK represented by Phoenix Mecano Ltd, Telephone (0296) 398 853.
 PCB, Ref, 940021-1 (see page 70)

*Further information on the general aspects of mains signalling may be obtained from the BEAMA Interactive and Mains Systems Association, Leicester House, 8 Leicester Street, London WC2H 7BN. Telephone 071 437 0678. Fax 071 437 4901.

In general, for domestic applications, the level of the signal applied across the mains wiring must not exceed 116 dB μV (631 mV). Measured across the line or neutral terminal and ground, the level must not exceed 316 mV (110 dB μV). The specified impedance must be 50 Ω .

Third harmonic spurious radiations must not exceed 57 dB μV (0.7 mV).

EN 50 065-1 specifies a frequency range of 95–125 kHz.

In practice, these requirements mean that only small energy levels may be applied across the mains wiring. This in turn means that the receiver must be fairly sensitive and that spurious signals and the 50 Hz mains hum must be suppressed adequately. Moreover, as extra precautions, switching instructions must be sent several times, while at the receiver, received codes are compared several times.

FIGURING IT OUT

PART 15 – SINE WAVES AND OTHERS

By Owen Bishop

This series is intended to help you with the quantitative aspects of electronic design: predicting currents, voltage, waveforms, and other aspects of the behaviour of circuits.

Our aim is to provide more than just a collection of rule-of-thumb formulas.

We will explain the underlying electronic theory and, whenever appropriate, render some insights into the mathematics involved.

In all the discussions in this series up to the present, the only periodic inputs that we have considered have been sinusoidal waves. We now have to consider circuit behaviour when the input is periodic but is not sinusoidal. For example, in what way does a given circuit respond to a square wave, a rectified sine wave, or a sawtooth wave?

The situation seems fraught with complications because there are so many possible forms that waves may have. Fortunately, we are rescued by the work of Baron Jean Baptiste Joseph de Fourier (1768–1830) whose Fourier Series provides a way of expressing complicated but periodic functions in terms of sines and cosines. When a waveform has been analysed into a number of sine and cosine waves of different amplitudes, we calculate the behaviour of the circuit for each component, considered separately. Then we make use of the principle of superposition (Part 3) to find the response of the circuit to the complete waveform. The equation for the Fourier Series is described in detail later, but we look at some simple examples first.

Summing sines

The waveform of Fig. 122 is clearly not sinusoidal, but it is easy to see that it is the sum of two sine wave of different amplitude, one having a frequency twice that of the other. These two components are shown separately in Fig. 123. In musical terms, the one with the lower frequency is termed the **fundamental**, and the one with double the frequency is the **first harmonic**. Between $t = 0$ and $t = \pi/2$, the waves reinforce each other, so that the resultant (Fig. 122) peaks in that

region. Between $t = \pi/2$ and $t = 3\pi/2$, the waves partly cancel out, causing the resultant to be flattened toward the x-axis. From $t = 3\pi/2$ to $t = 2\pi$, the waves reinforce again. We could add a constant term to the equation for Fig. 122, for example:

$$y = 6 + 4 \sin t + 2 \sin 2t \quad [\text{Eq. 120}]$$

The effect of this is simply to shift the curve up the page. In electronic terms, the periodic signal is superimposed on a constant direct voltage, assuming that y refers to a voltage. In the discussions which follow, this variable might equally well represent a current or any other quantity which varies periodically.

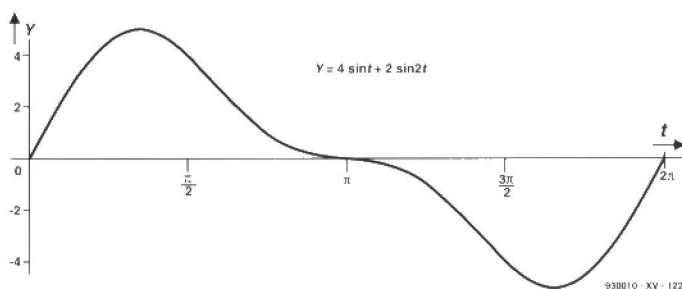


Fig. 122

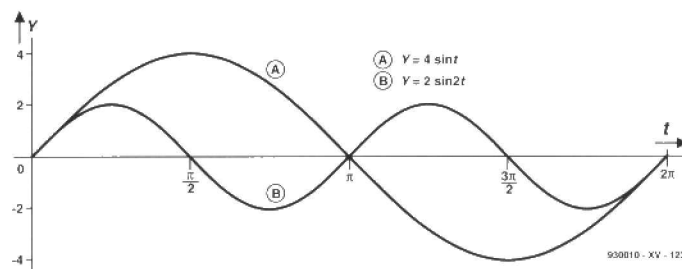


Fig. 123

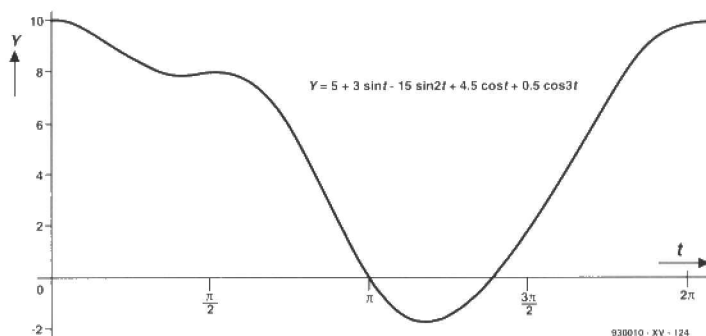


Fig. 124

Figure 124 shows a signal that has five components:

$$y = 5 + 3 \sin t - 1.5 \sin 2t + 4.5 \cos t + 0.5 \cos 3t$$

[Eq. 121]

This might be taken to be the trace of an audio signal from a musical instrument as seen on the screen of an oscilloscope. As we shall later, although a Fourier Series has (in theory) an infinite number of terms, quite often only the first few terms need to be evaluated in practice.

So far, we have **synthesized** waveforms by writing out a series comprising a constant and one or more sine or cosine terms. Now we have to find out how to work in the opposite direction. Given a waveform such as the triangular wave of Fig. 125, we **analyse** it in to its components. But, before we leave the simple examples above, note these features of the series:

- a constant (d.c.) term;
- terms in $\sin t$, $\sin 2t$ (in general, $\sin nt$, where n is an integer);
- terms in $\cos t$, $\cos 2t \dots \cos nt$;
- the terms have different coefficients, which may be positive or negative;
- the fundamental frequency is such that one cycle takes 2π seconds (we will explain how to deal with other fundamental frequencies later);
- all frequencies are multiples of the fundamental.

In practice, the series may be simplified if, for example, the constant term is zero, or the coefficients of all the sine terms or all the cosine terms are zero. Equation 120 is an example of a series in which the cosine terms all have a zero coefficient.

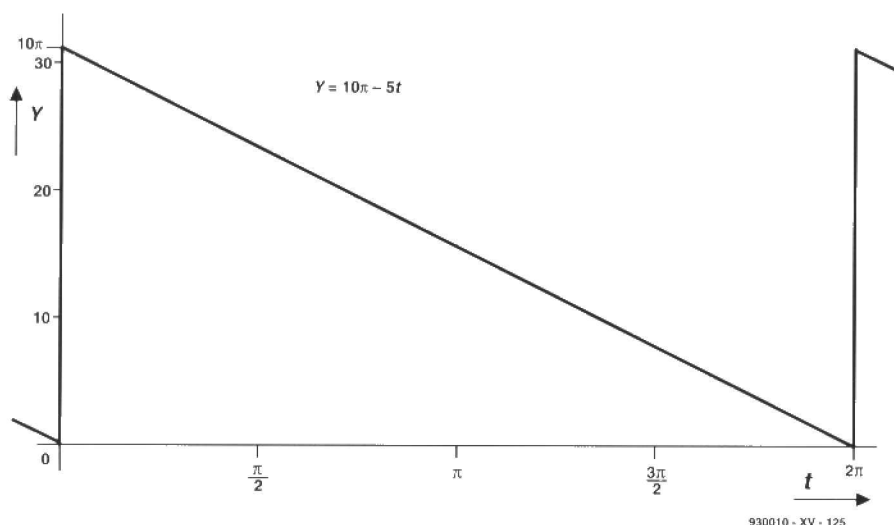


Fig. 125

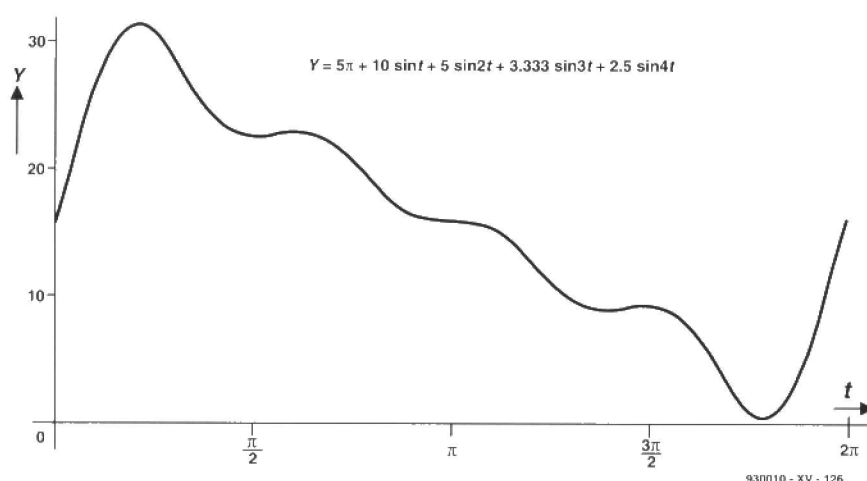


Fig. 126

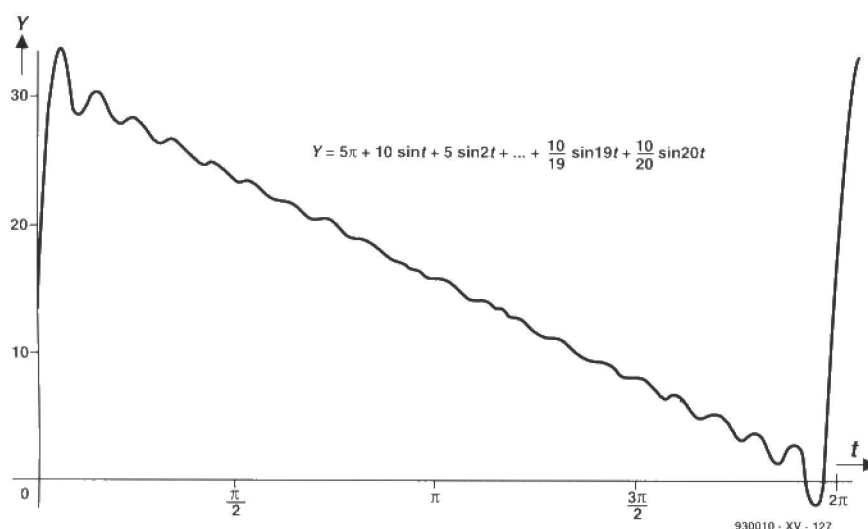


Fig. 127

Fourier series

The Fourier Series has this form:

$$y = A_0 + a_1 \cos t + a_2 \cos 2t + a_3 \cos 3t + \dots + a_n \cos nt + b_1 \sin t + b_2 \sin 2t + b_3 \sin 3t + \dots + b_n \sin nt.$$

[Eq. 122]

Although the equation is long and unwieldy, it breaks down into distinct parts as listed above. The constant term is A_0 . We represent the coefficients of the cosine terms by a_1, a_2, \dots, a_n , and the coefficients of the sine terms by b_1, b_2, \dots, b_n . The important prop-

erty of the Fourier Series is that, with some exceptions, any kind of periodic signal can be analysed as an equation of this form. Different signals have different sets of coefficients and our next task is to calculate these.

The first term is the mean

values of y over 1 cycle. This fits in with the idea of the first term being equivalent to the steady direct voltage on which the signal voltage is superimposed. In the case of Fig. 125, it is easy to evaluate the first term simply by looking at the graph. During 1 cycle, y ramps down linearly from 10π to zero. The first term is the mean of 10π and zero. In general:

$$A_0 = 5\pi$$

$$A_0 = \frac{1}{2\pi} \int_0^{2\pi} y \, dt \quad [\text{Eq. 123}]$$

This integral gives the area under the graph for a period of 1 cycle. The integral divided by the period (2π) is the mean value of y . In some cases, it may be easier

Integrating by parts

This technique is used to integrate the product of two expressions, both of which are functions of the same variable. We shall call the two parts u and dv/dt (these symbols do not necessarily have anything to do with voltages).

In the example in the text, for finding cosine terms:

$$u = y = 10\pi - 5t$$

$$dv/dt = \cos nt.$$

First, differentiate u :

$$du/dt = -5.$$

Next, integrate dv/dt to obtain v :

$$v = (\sin nt)/n.$$

The constant of integration is not required. The integral of the product is given by the formula

$$\int u \cdot dv/dt \, dt = uv - \int v \cdot du/dt \, dt$$

Substitute u , v and du/dt , and evaluate.

Applying this formula to the example:

$$a_n = \frac{1}{\pi} \int_0^{2\pi} (10\pi - 5t) \cos nt \, dt$$

$$= \frac{1}{\pi} \left[\left[(10\pi - 5t)(\sin nt)/n \right]_0^{2\pi} - \int_0^{2\pi} -5(\sin nt)/n \, dt \right]$$

The integration is continued in the text.

Box 1

to integrate from $-\pi$ to $+\pi$. It does not really matter where in the cycle we begin, as long as we finish 2π seconds later.

Cosine terms

The formula for the coefficients of the cosine term is:

$$a_n = \frac{1}{\pi n} \int_0^{2\pi} y \cos nt \, dt \quad [\text{Eq. 124}]$$

This is similar to Eq. 123, but here we have a **product** to integrate. The product is $y \times \cos nt$ and, since y is a function of t , we must integrate **by parts** (see Box 1). Using this technique, we find that:

$$a_n = \frac{1}{\pi n} \left[(10\pi - 5t) \sin nt \Big|_0^{2\pi} + 5 \int_0^{2\pi} \sin nt \, dt \right]$$

The second term on the right equals zero (see Box 2), leaving:

$$\begin{aligned} a_n &= \frac{1}{\pi n} \{ (10\pi - 10\pi) \sin 2n\pi \\ &\quad + (10\pi - 0) \sin 0 \} \\ &= \frac{1}{\pi n} \{ 0 + 10\pi \sin 0 \} \end{aligned}$$

But, $\sin 0 = 0$, so

$$a_n = 0.$$

As a result of this, there are no cosine terms in the series. This considerably simplifies matters.

Sine terms

The formula for the coefficients of the sine terms is:

$$b_n = \frac{1}{\pi n} \int_0^{2\pi} y \sin nt \, dt \quad [\text{Eq. 125}]$$

Integrating by parts:

$$\begin{aligned} b_n &= \frac{1}{\pi n} \left\{ [-(10\pi - t) \cos nt] \Big|_0^{2\pi} \right. \\ &\quad \left. + 5 \int_0^{2\pi} -\cos nt \, dt \right\} \end{aligned}$$

The second term on the right equals zero (see Box 2), leaving:

$$\begin{aligned} b_n &= \frac{-1}{\pi n} \left\{ [-(10\pi - t) \cos nt] \Big|_0^{2\pi} \right. \\ &\quad \left. + 5 \int_0^{2\pi} -\cos nt \, dt \right\} \end{aligned}$$

But $\cos 0 = 1$, so

$$b_n = 10\pi/\pi n = 10/n.$$

Thus, the sine terms have the form:

$$(10/n) \sin nt$$

for $n = 1, 2, 3, \dots$

How many terms?

We are now in a position to assemble the series from the initial term and the coefficients. In Eq. 126, we take the series as far as the third harmonic:

$$y = 5\pi + 10\sin t + 5\sin 2t + 3.333\sin 3t + 2.5\sin 4t$$

[Eq. 125]

This function is graphed for 1 cycle in **Fig. 126**. It shows undulating sine-like features, but is recognisably the triangular wave of **Fig. 125**. For such an un-sinusoidal waveform as a sharp-toothed triangular wave, we need

Useful integrals

Calculations are often made very much shorter when these integrals occur in an expression to be evaluated. Integration is with respect to t , over the limits 0 to 2π or $-\pi$ to $+\pi$, and n and m are positive integers.

Term to be integrated	Integral	Condition
$\sin nt$	0	
$\cos nt$	0	
$\sin^2 nt$	π	$n \neq 0$
$\cos^2 nt$	π	$n \neq 0$
$\sin nt \cos mt$	0	$n \neq m$
$\cos nt \cos mt$	0	$n \neq m$
or	π	$n = m$
$\sin nt \sin mt$	0	$n \neq m$
or	π	$n = m$

Example: $\int_0^{2\pi} \sin 3t \cos 4t \, dt = 0$

Box 2

more terms in the series to obtain a good representation. We extend the series until we obtain a waveform which we consider to be sufficiently close to the required waveform:

$$\begin{aligned} &\dots + 2\sin 5t + 1.667\sin 6t \\ &+ 1.429\sin 7t + \dots + 0.5\sin 20t. \end{aligned}$$

Figure 127 shows the result of extending the series up to $n = 20$, the 19th harmonic. It is clear that, as we take more and more terms, the resulting function approaches more and more closely to that of the original triangular wave. It is only where there is a dramatic change that appreciable oscillations are observed.

Calculating and summing the terms is fast on a programmable calculator. However, the program memory may not cope with as many as 20 terms. A computer program in BASIC (**Fig. 128**) is

easier to type and sums hundreds of terms, if required.

Circuit modelling


As an illustration of how the Fourier Series may be used in modelling, we will see what happens to the sawtoothed voltage wave of **Fig. 125** when it is applied to the circuit of **Fig. 129**, which is a passive high-pass filter. Remember that the period of the wave is 2π . Its frequency is $1/2\pi = 0.159$ Hz. To have any effect on the lower harmonics, we need a capacitor of relatively high value. With the values shown in **Fig. 129**, the -3 dB point is 2 Hz.

We now need to examine the terms of the Fourier Series for y and find what happens to them when fed into the filter. The first term, 5π , is a d.c. term and does not pass through. Recalling the technique used in Part 6 to calculate the attenuation and phase

```
10 FOR t = 0 TO 6.4 STEP 0.05
20 u = PI*5
30 FOR n = 1 TO 20
40 u = u + 10/n*SIN(n*t)
50 NEXT
60 PRINT "t="; t; " u="; ROUND(u,3)
70 NEXT
```


930010 - XV - 128

Fig. 128

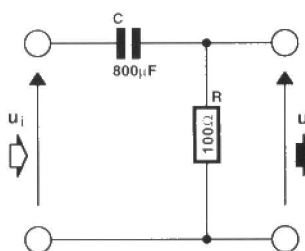

930010 - XV - 129

Fig. 129

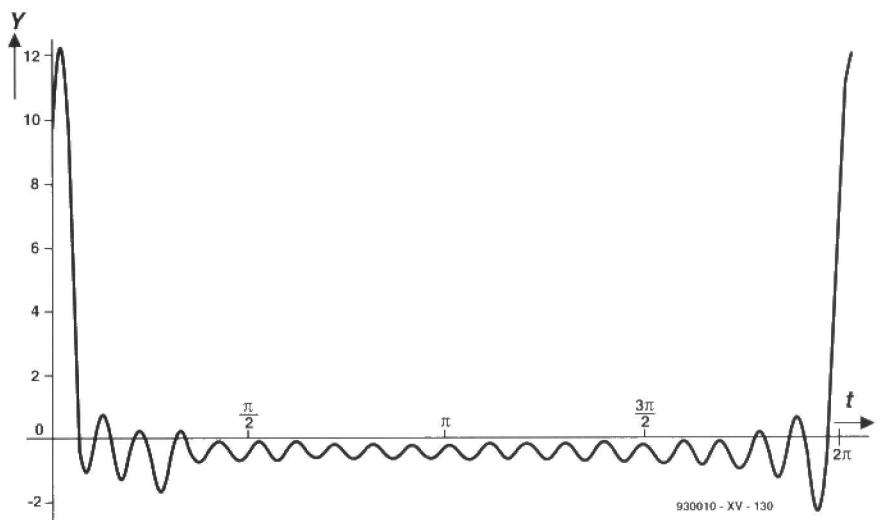

930010 - XV - 130

Fig. 130

Books from Elektor Electronics (Publishing)

The following books are currently available:

301 Circuits	£9-95	\$14.50
302 Circuits	£9-95	\$14.50
303 Circuits	£10-95	\$17.90
304 Circuits	£12-95	\$23.95
305 Circuits (published in April 1994)	£14-95	\$27.70
SMT Projects	£ 9-95	\$14.50
Microprocessor Data Book	£10-95	\$19.90
Data Sheet Book 2	£9-95	\$18.50
Data Book 3: Peripheral Chips	£10-95	\$19.95
Data Book 4: Peripheral Chips	£10-95	\$19.95

How to order:

UK and Overseas private customers (NOT in USA and Canada) from:

Elektor Electronics (Publishing)
PO Box 1414 Dorchester, England DT2 8YH
Telephone (0305) 250 995
Fax: (0305) 250 996

UK and Overseas bookshops, schools, colleges, universities and bulk orders (NOT in USA and Canada) from:

Gazelle Book Services Ltd
Falcon House, Queen Square, Lancaster,
England LA1 1RN
Telephone (0524) 68765
Fax: (0524) 63232

USA and Canada ONLY from:

Old Colony Sound – please see order form
on page 71 for details

VOUCHER

This voucher (original only; no photocopies accepted) entitles the holder to 7½% discount on the purchase price of any Elektor Electronics book listed in the adjacent box. Two vouchers qualify for 15% discount and three for 30%. More vouchers will be published in forthcoming issues of *Elektor Electronics*

04/94

lag of a low-pass filter (**Fig. 52**), we calculate the effect of the high-pass filter of **Fig. 128** on the fundamental component, $y = 10\sin t$. The total impedance of the filter is:

$$Z = R - j/\omega C,$$

where we express the impedance of the capacitor as a complex number (see Part 9). Given that $\omega = 1$, $R = 100$ and $C = 800 \times 10^{-6}$,

$$Z = 100 - j1250,$$

or, in polar form:

$$Z = 1254 \angle -1.49.$$

Angles are in radians. Considering the filter as a potential divider, its output is u_R , and:

$$u_{out} = u_{in} \cdot 100/Z.$$

For the fundamental, the peak values of u_{in} is 10 V (the coefficient of the $\sin t$ term of the series).

$$u_{out} = 1000/(1254 \angle -1.49) = 0.7974 \angle 1.49.$$

The output signal is attenuated to about 0.8 V peak and **leads** the input by 1.49 rad.

We can similarly find u_{out} for each of the harmonics, expressed

in polar form. The values of R and C remain the same, but ω becomes 2, 3, 4, ... for successive harmonics. The outputs are attenuated by different amounts and have different phase leads. These outputs can not be added in the usual way, as phasors, because they are all of different frequencies. We therefore express each of them as a sine wave of given amplitude and period with a given phase lead. In this form, the output from the fundamental is:

$$u_{out} = 0.7974 \sin(t + 1.49).$$

Summing the outputs for the fundamental and the first 19 harmonics, we have:

$$\begin{aligned} u_{out} = & 0.7974 \sin(t + 1.49) \\ & + 0.7900 \sin(2t + 1.41) \\ & + 0.7778 \sin(3t + 1.34) \\ & + \dots 0.5771 \sin(12t + 0.81) \\ & + \dots 0.4241 \sin(20t + 0.56). \end{aligned}$$

Note that the coefficients decrease, but much more slowly than in the original function. This reflects the fact that the higher frequencies are less attenuated than the lower frequencies. Also, the phase lead is less as frequency increases. When $\omega = 12$, $f = \omega/2\pi = 1.91$, which is approximately at the

-3 dB point of the filter. The input amplitude of this component is $10/12 = 0.8333$ and its output amplitude is 0.5771. The attenuation is $0.5771/0.8333 = 0.69$. This is roughly 0.7, the expected attenuation at the -3 dB level. The phase lead is 0.81 rad., equivalent to 46° , close to the lead of 45° expected at the -3 dB point.

A graph of u_{out} appears in **Fig. 129**. It shows that filtering has a dramatic effect on the sawtooth wave, reducing it to a series of spikes, where the voltage suddenly steps up at the beginning of each cycle. The circuit filters out the slow change of voltage as waveform ramps down. This graph has more pronounced undulations than **Fig. 127**; this is due to the fact that the high-pass filter makes the higher frequencies relatively prominent.

In the example above we have illustrated the use of the Fourier Series by modelling a simple waveform being passed through a circuit with a simple response. There are easier ways of doing this, as we shall see in Part 17. It is with more elaborate waveforms and more complicated circuits that the Fourier Series shows its power. With a computer to provide help with the calculations, this is a useful technique for

analysing circuit behaviour. Next month, we show how to tackle other types of wave and we look at ways of shortening the calculations.

Test yourself

A triangular waveform ramps up according to the equation $y = 2t$, repeating every 2π seconds. Express this as a Fourier Series, as far as the 3rd harmonic. This signal is applied to a low-pass filter having the same components as **Fig. 129**, but with R and C interchanged. Calculate a series for the waveform of the output signal as far as the 3rd harmonic.

Answers to

Test yourself (Part 14)

- $i = 0.3(e^{-t} - e^{-2t}) + 0.06923e^{-2t} - (9\cos 3t + 7\sin 3t)/130$.
- $i = 0.03316e^{-4t} - 0.02036e^{-246t} - 0.0128e^{-0.4545t}$. Current = 774 μ A.
- $d^2i/dt^2 + 10000 di/dt + 5000i = 4e^{0.5t}$
 $i = Ae^{-5t} + Be^{-9995t} + (7.27 \times 10^{-5})e^{0.5t}$
 $i = 0.0003277(e^{-5t} - e^{-9995t}) + (7.27 \times 10^{-5})(e^{0.5t} - e^{9995t})$
 Current = 0.275 mA.

DIRECT CONVERSION RECEIVERS

PART 2 (final)

SOME NOTES ON DESIGN AND CONSTRUCTION TECHNIQUES, AND THREE PRACTICAL EXAMPLES

By Joseph J. Carr, B.Sc., MSEE

In the previous instalment of this article we examined the theory behind direct conversion receivers (DCR). In this final instalment we will take a look at three simple projects that are based on the principles discussed in Part 1. Three different designs are selected for testing: the 40 and 75/80-meter bands 'Neophyte' design by John Dillon¹; a 40-meter band HF receiver based on the passive DBM designs of Lewallen and Campbell²; and a VLF design. All three designs were fabricated and tested on a common test chassis built especially for the purpose.

The common test chassis

Part of the decision to build and test several direct conversion receivers involved having a common chassis for all three designs. Although not very elegant, being made of scrap aluminum chassis and bottom plates from the 'junk box', it was at least low cost and effective. **Figure 1** shows the receiver test bed front panel. It is fitted with a Jackson Brothers calibrated dial with a 10:1 fast/slow vernier drive. The 6.35-mm (0.25-in.) shaft cou-

pling on the vernier drive is used to turn either a variable air dielectric capacitor or potentiometer, depending on whether the DCR being built is a mechanically tuned or voltage tuned version. For most of the experiments the voltage tuned variety was used. Two additional controls are also provided, and both are potentiometers. The pot to the right of the tuning knob is a volume control, while that to the left is the RF tuning control (for voltage tuned front-end circuits).

Three circuits are provided for the test bed: two d.c. power supplies and an LM386 audio power amplifier. One d.c. power supply (**Fig. 2**) is used to provide +12 V regulated to the circuits of the DCRs used on the test bed. It uses a 7812 three-terminal IC voltage regulator, and works from a 15 V d.c., or higher source. In the case of this project, raw power was provided by two 9-V dry-cell batteries connected in series. The second d.c. power supply (**Fig. 3**) consists of a 78L12 low-power, three-terminal voltage regulator and a potentiometer. The potentiometer is for main tuning, and is ganged to the main dial of the chassis. In

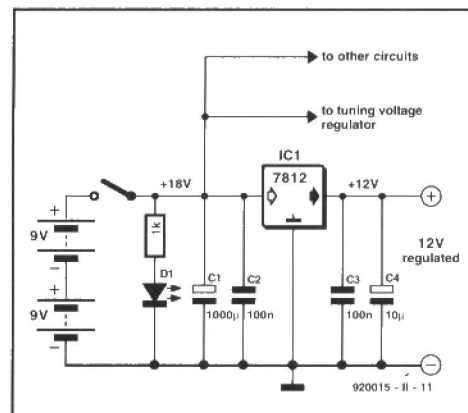


Fig. 2. DC power supply for the DCR test chassis. A pair of 9 volt batteries provides primary power, which is then regulated to 12 V by a 7812 IC voltage regulator.

normal use, this potentiometer is used to tune the local oscillator (LO) of the DCR.

The audio amplifier is the LM386 low-power 'audio system on a chip' device. The LM386 uses a minimum of external components, and includes both the audio preamplifiers and the power amplifiers to produce between 250 mW and 700 mW of audio power, depending on the particular device specified. The circuit for the audio section is shown in **Fig. 4**, while its location on the test bed chassis is shown in **Fig. 5**. Note that the audio section has its own +12-V regulator. This is an optional feature, but does serve to keep load variations in the audio amplifier from coupling to the rest of the circuitry. The audio section is the small circuit board on the left side of the chassis right by the audio volume control.

Figure 5 shows the rear view of the DCR test bed chassis. As mentioned, the audio amplifier section is shown on the left. The gray metal box contains either the variable air-dielectric capacitor, or potentiometer and power supply (**Fig. 3**),

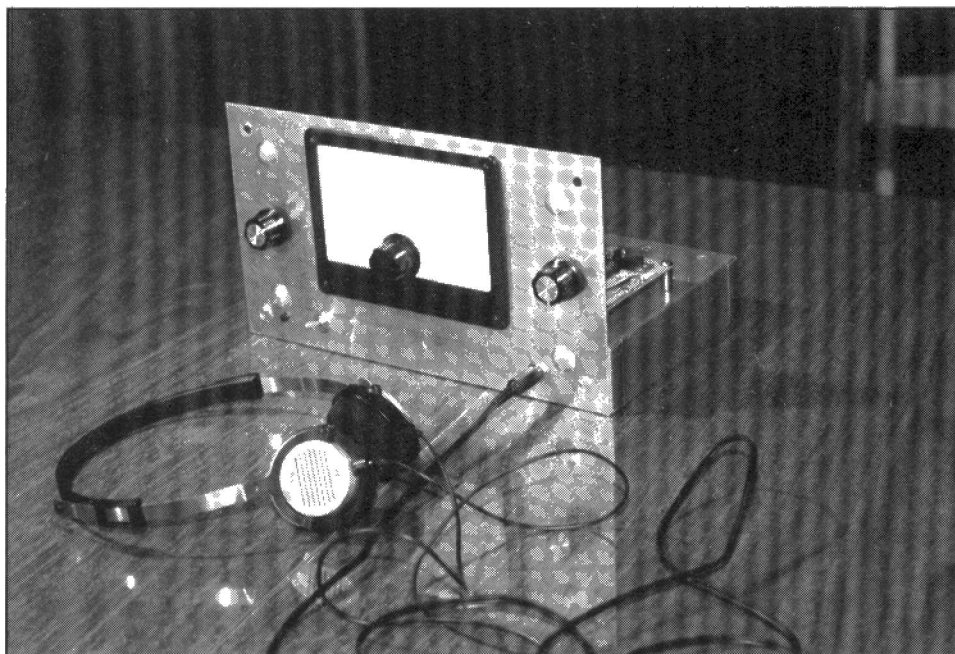


Fig. 1. Test chassis for direct conversion experiments. This chassis incorporates the DC power supplies, tuning voltages for RF and LO, and an LM386 audio amplifier stage.

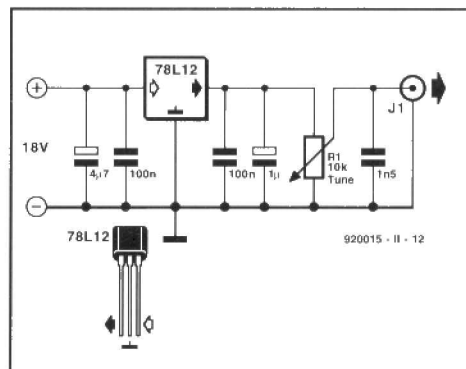


Fig. 3. Tuning voltage source. Potentiometer R1 is mechanically ganged to the main tuning dial and gear assembly.

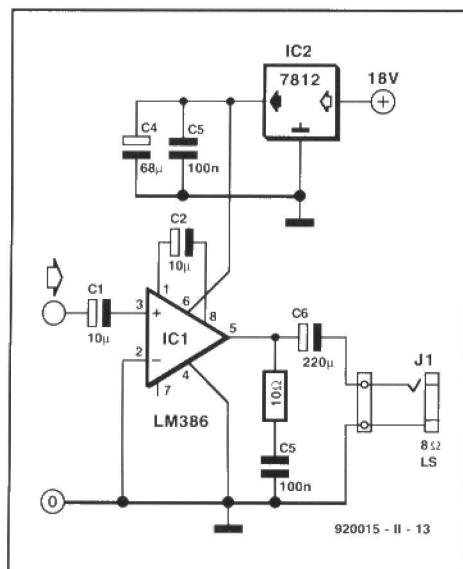


Fig. 4. Circuit for the LM386 audio amplifier stage on the DCR test chassis.

either of which may be used to tune the local oscillator of the DCRs being tested. The 12-V d.c. power supply is located on the small printed circuit board to the rear of the tuning box. Space is provided to the right of the tuning box for the circuitry of the DCR being tested. This board is changed from one project to the other.

Wiring board construction used two different methods. The audio amplifier, the tuning d.c. power supply and 12-V d.c. regulated power supply were built on Radio Shack (Tandy) 'universal' printed circuit boards. The DCRs, on the other hand, were wired using Vector perf-board with a hole grid on 0.1-inch centres, or an equivalent product.

Three different antennas were used for testing the DCRs in this article: a 5BTV Cushcraft $\frac{1}{2}$ -wavelength ham band vertical, an outdoor 30-m (100-ft) random length end-fed wire, and a 6-m (20-ft) wire strung across the ceiling of my basement workshop. Interestingly enough, on the HF bands there was not a large difference between the outdoor antennas' performance and only slightly more difference between the outdoor antennas and the indoor antenna. On the VLF band, however, the random length wire was clearly superior to the other two antennas.

75/80 and 40-m NE602 design

The first DCR tested is the John Dillon design, which was originally published in *QST*³ and discussed in Part 1 of this article. The Dillon design is based on the Signetics NE602 frequency converter chip available in the form of a parts kit from PennTek Electronics in the USA (14 Peace Drive, Lewistown, PA 17044, USA; Phone: 717-248-2507 — overseas callers note: normally a recording answers). The kit contains a printed circuit board and

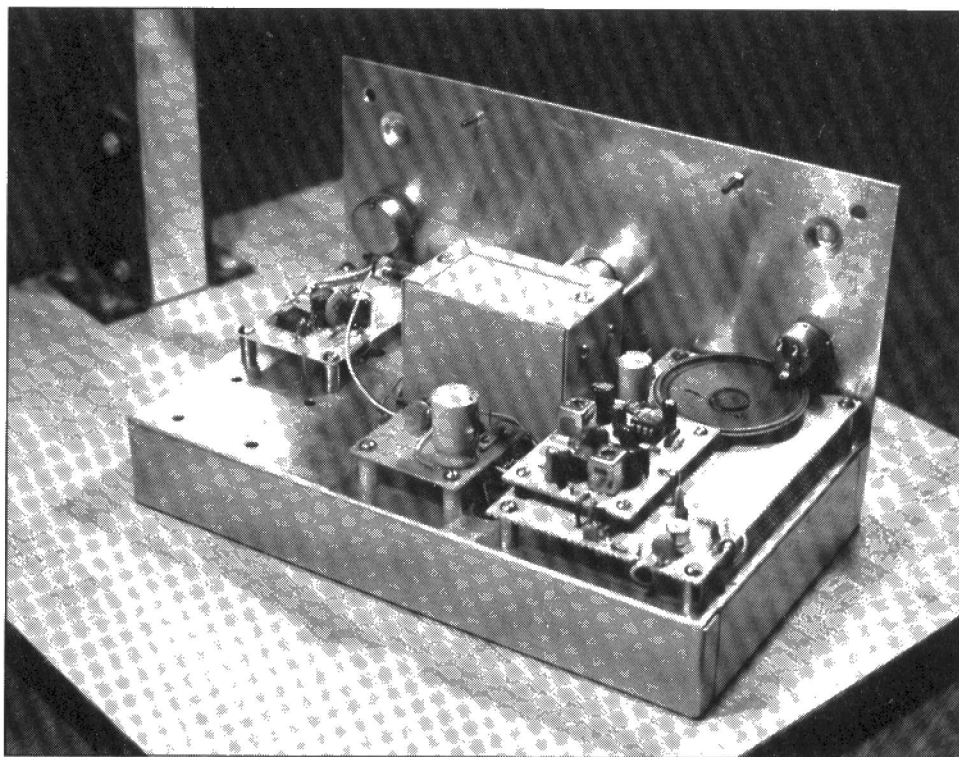


Fig. 5. Rear view of the DCR test chassis. Audio stage is on the left side, while the tuning voltage circuit is within the shielded metal enclosure. The main voltage regulator is behind the tuning voltage box (main batteries beneath chassis). Each test receiver was fabricated on a piece of perforated circuit board (shown here with the Dillon receiver mounted). In this example the audio stage was not needed because it was incorporated in the commercial printed circuit board mounted to the receiver board.

all of the electrical parts needed to build the receiver except for the variable capacitors. These capacitors are becoming difficult to obtain in the USA, but the Maplin (P.O. Box 777, Rayleigh, Essex, SS6 8LU, UK; phone 0702 554171) catalogue in UK offers several reasonable candidates for both RF and LO tuning capacitors.

The circuit for the Dillon design is shown in Fig. 6. The RF 'heart' of the circuit is the NE602 converter chip. The

NE602 contains the local oscillator (LO) and a transistor double-balanced mixer (DBM) in the form of a transconductance cell. This design provides about 20 dB of conversion gain, good sensitivity, and rejection of the LO and RF signal components in the output. However, the early design chip is a little lacking in dynamic range (a problem reputedly corrected in the updated NE612 chip). The Dillon DCR

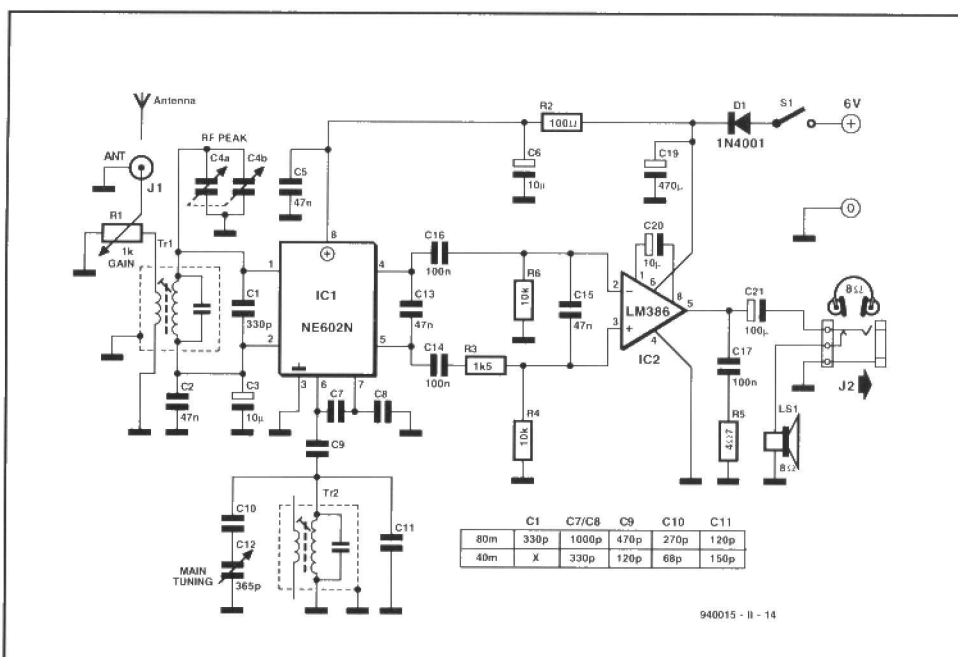


Fig. 6. Circuit for the Dillon H.F. DCR.

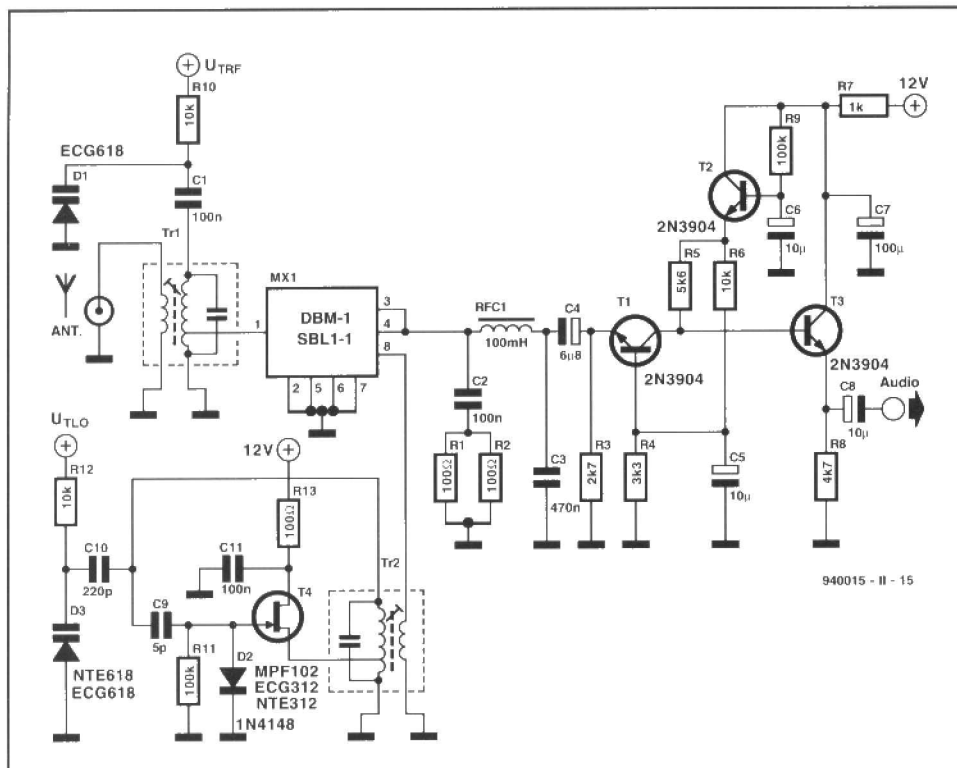


Fig. 7. DCR design based on a commercial passive double balanced mixer (DBM).

uses the balanced outputs of the NE602 (most designs are single-ended) in an effort to improve AM rejection. Likewise, to match the NE602 output scheme, the LM386 audio amplifier is wired in the differential input configuration.

Dillon's commercially produced printed circuit board was mounted on a piece of perf-board (see Fig. 5 again) that was cut to fit the space available on the test bed chassis. In addition to the Dillon board, the perf-board contained the circuitry for the RF and LO varactor circuits and a 7806 three-terminal voltage regulator to reduce the 12 V available on the test bed to the 6 V specified by Dillon.

The Dillon receiver can be used on either 75/80 meters, or 40 meters, depending on how the oscillator is configured. The performance is optimized for 75/80 meters, according to Dillon. In a telephone conversation John Dillon told the author that the 40-meter band was added later in accordance with the wishes of the original publisher of the project. However, despite Dillon's reservations, I found the 40-meter performance to be about the same as the 75/80 meter performance with the possible exception of overload problems due to the high power AM signals from international broadcasters found in the 40-meter band.

The Dillon design proved to be remarkably sensitive, much more so than I anticipated. Perhaps that is an advantage of the 20-dB conversion gain of the NE602.

Criticisms of the design include two things related to the audio amplifier.

First, there is no volume control. The level of the output signal is controlled by a

1000- Ω linear taper potentiometer that varies antenna signal to the RF front-end. I found the lack of a volume control disconcerting, but not overwhelmingly so.

Second, there is a general criticism of this design and all other designs I built where the LM386 is used alone for the audio stage without preamplification. The audio gain is insufficient to provide for really comfortable listening, especially when a loudspeaker was used instead of earphones. I believe that this could be relieved by adding a preamplifier stage ahead of the LM386. If the differential nature of the circuit is to be preserved, then an operational amplifier can be used for this purpose. Several candidate op-amps (or operational transconductance amplifiers) are available that work well on single polarity d.c. power supplies.

A crude test of this theory proved interesting. I attenuated the output of Dillon's receiver with a 1000- Ω potentiometer to make it compatible with the input of the LM386 audio amplifier that is used in the DCR test bed. The total gain of the two LM386s, even with some attenuation, was considerably higher than the gain of the receiver circuit alone. The result was loud and clear signals that would not tax a middle-aged, hard of hearing guy like me. Dillon confirmed the lack of audio gain⁵. He told me that he had designed a three-IC version that inserted a dual op-amp between the NE602 and LM386 (one section was a preamplifier and the other an audio filter). He stated that the present design was selected because of a goal of two-IC simplicity.

My general assessment of the Dillon design is that it makes a decent weekend

project for anyone who wishes to experiment with direct conversion radio receivers. The receiver can be used as designed, or easily modified if that is your preference. It is easy to modify for bands other than the amateur radio bands because both its circuitry and mechanical implementation are straight forward. It also provides a basis for experimenting with other variations of the basic design.

High-frequency DCR based on passive DBM

The next receiver that I built and tested was a high frequency design based on the MiniCircuits (P.O. Box 350166, Brooklyn, NY, 11235-0003, USA; phone 718-934-4500) SBL-1-1 passive double-balanced mixer (DBM). This mixer device provides frequency conversion up to 500 MHz, at LO power levels up to +7 dBm and RF levels up to +1 dBm. For higher dynamic range performance, there are variants that accept higher levels in both the LO and RF ports. The cost of those devices, however, is also higher than the SBL-1-1. If the SBL-1-1 is not easily available, then substitute the SRA-1 or SBL-1 designs. Alternatively, it is relatively easy to achieve reasonable performance using a homebrew passive DBM (see Part 1 of this series). Such circuits use toroidal coupling transformers and hot carrier RF diodes for mixing. The RF signal is applied to pin 1 of either SRA-1 or SBL-1 devices, while the LO is applied to pin no. 8; pins 2, 5, 7 and 8 are grounded. The IF output is found on pins 3 and 4, and these pins must be connected together for proper operation.

The circuit for this receiver is shown in Fig. 7. The circuit was built on a piece of perf-board cut to fit the space available on the test bed. The RF front-end of the receiver consists of a 10.7-MHz IF transformer intended for FM transistor radios; a Mouser Electronics (2401 Highway 287 N, Mansfield, TX, 76063, USA; phone 817-483-4422) type 42IF123 was used. FM IF transformers are a little broad banded (>200 KHz) for this application, but are convenient. A higher Q, narrower band transformer can be built if desired.

Another problem with the 10.7-MHz IF transformer is that the tap is not a good match to 50 Ω because the tap seems to be at a point where the impedance is apparently a couple of hundred ohms. However, the mismatch did not deteriorate the performance so much that it overcame the convenience of the easy-to-obtain transformer. Optimization of the circuit requires an RF transformer designed with a 50- Ω tap.

The internal capacitor of the IF transformer can be disconnected if desired, although I used it as part of the tuning capacitance for the circuit. At frequencies higher than 11 MHz, however, the

capacitor will have to be removed. This capacitor is found in a small external recess in the base of the IF transformer. It is not easy to 'disconnect' the capacitor without a lot of work and potential damage to the transformer. The best way to get rid of the capacitor is to crush it with a small probe or screwdriver tip. Be sure to remove the debris to keep it from shorting other circuits.

The circuit as shown will tune from about 5 MHz to greater than 9 MHz when the 440-pF varactor is used. The total capacitance seen by the transformer secondary consists of the internal capacitor (unless removed) plus the combined capacitance of C_1 and D_1 . This capacitance is:

$$C_{TRF} = (C_1 C_{D1}) / (C_1 + C_{D1}) \quad [2]$$

You can change the range of the tuning by using other values of capacitance than the 10 nF shown. When the 10-nF capacitor is used, the total capacitance is very nearly the capacitance of the diode. Other implementations of C_1 can include combinations of smaller valued fixed and variable (trimmer) capacitors.

The local oscillator for the receiver is a JFET Hartley oscillator that uses the same type of IF transformer as the RF input circuitry for main tuning. The secondary of the transformer is tuned to 10.7 MHz initially, but this frequency is modified by the external varactor circuit. The particular transformer used must be evaluated so that the tap is closer to the grounded end than the gate end of the winding. I found the correct configuration by simple comparison of the d.c. resistance of the segments of the winding (B-A and B-C) referenced to the tap (0.3 Ω and 0.8 Ω , respectively). This type of circuit was discussed in Part 1 of this article.

The tuning varactor has a maximum capacitance of 440 pF, but this value is a bit large for practical use. Therefore, a series capacitance, which is needed for d.c. blocking in any instance, is used to reduce the total capacitance. The same formula as above can be used for determining the value of series capacitance needed for making the circuit tune to any particular range.

The d.c. power supply was the same 12-V supply as used for the rest of the circuitry. An improved version might use a +9-V regulator to supply only the oscillator transistor. This design would prevent frequency pulling due to power supply noise or voltage variations caused by shifts in load current. If the receiver had used an incorporated audio power amplifier, rather than the outboard style used here (which has its own 12-V regulator), a separate regulator would have been indicated.

The output signal, when a 12-V d.c. power supply was used, was of the order of 800 mV_{pp}, so is within the drive range

permitted by the SBL-1-1.

The IF output of the DBM (pins 3 and 4) is terminated in two circuits. First is capacitor C_2 and resistors R_1 and R_2 . This network forms a 50- Ω match to the 50- Ω output of the DBM for high frequencies (a function of the capacitor). The $C_2/R_1/R_2$ network absorbs any residual LO and RF signal that makes it past the conversion process, while allowing the mixer to operate into its characteristic impedance. The second circuit terminating the DBM is an audio LC low-pass filter consisting of RFC₁ and C_3 . This circuit passes only those audio frequencies in the normal communications audio bandwidth below 3 KHz.

The audio preamplifier for the receiver is a two-stage amplifier based on common n-p-n bipolar transistors (2N3904 or equivalent). Transistor T_1 is a common base amplifier. It is used because its low input impedance is a reasonable match to the filter and DBM. Transistor T_3 forms an emitter follower output amplifier. An active decoupler (T_2) is used in the power supply line of the amplifier.

Like the other receivers, this design suffered from a lack of audio gain, although this defect was without practical effect when only headphones were used for reception. If you would like to try improving the circuit, then try using an IC audio preamplifier between the output of T_3 and the input of the audio power amplifier stage. Also, a higher power audio amplifier might prove useful.

VLF direct conversion receiver

The very low frequency (VLF) bands are


those frequencies below the medium wave AM broadcast band, i.e., below 540 KHz. A considerable amount of CW (morse code) and radio beacon activity is found in the VLF bands all over the world. In Europe, there is another broadcast band in the VLF region (145-280 KHz).

The circuit for the VLF DCR is shown in Fig. 8. This design is similar to Dillon, and also to one published in *The ARRL Handbook for Radio Amateurs (1993 Edition)*⁶, although a number of component values are changed because of the changed frequency range.

The front-end of the circuit is an NE602 integrated circuit. In the test circuit, the input circuit is untuned, although tuning can be accomplished by connecting a capacitor from point 'A' in Fig. 8 to ground. Most readers will probably wish to use a combination of a varactor diode and a parallel fixed capacitor, rather than an actual air variable capacitor, as shown in the inset to Fig. 8. The capacitor marked C_x can be used to ensure the tuning range of the varactor and T_1 .


The RF input transformer (Tr_1) and the local oscillator inductor (Tr_2) are 0.63-mH transformers intended for use as 455-KHz IF transformers. I used Toko RAN-10A6845EK, available in North America from Digi-Key (P.O. Box 677, Thief River Falls, MN 56701-0677; USA; Phone 1-800-344-4539 in USA and Canada) as part no. TK-1202.

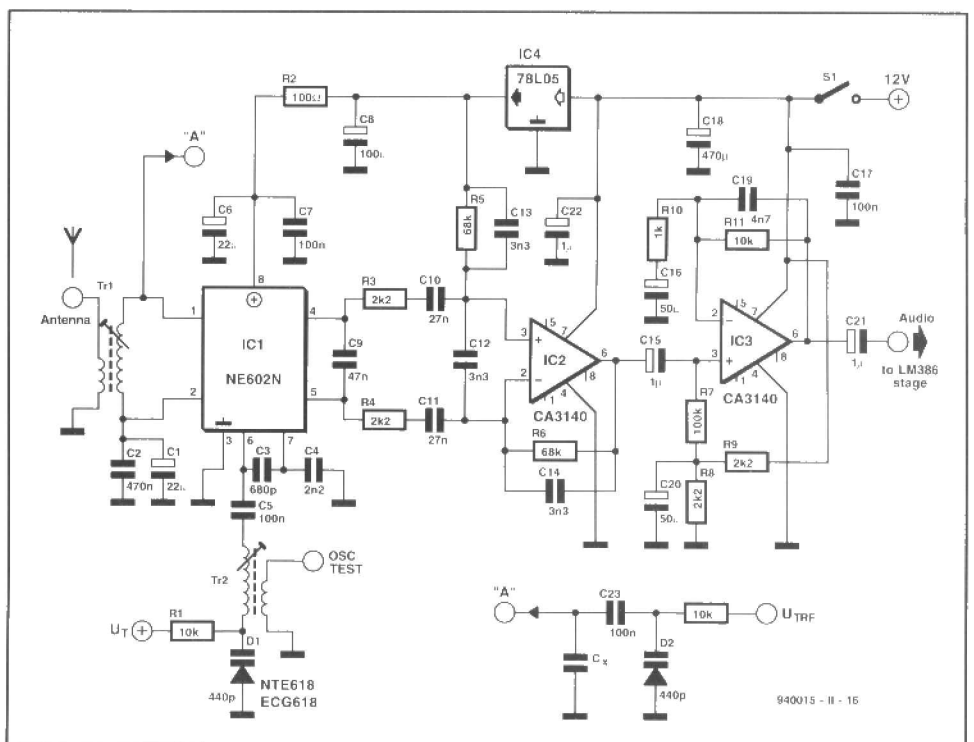The local oscillator circuit connected to pins 6 and 7 is a straightforward series-tuned Colpitts or Clapp design using the inductance of a 455-KHz IF transformer (see above) and a 440-pF voltage variable capacitance diode ('varactor'). I used the NTE618 or ECG618 service re-



PROGRAMMER & EMULATOR

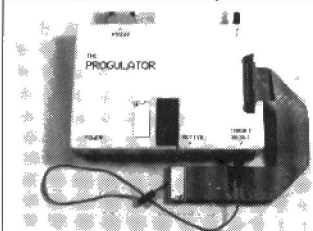The affordable and complete solution for microprocessor development work.



A combined EPROM programmer and emulator in a solid case for 8-bit development work with all EPROMs from 27(C)64 to 27(C)512. Features include: seven different programming algorithms, 38400 Baud serial comms for fast programming & emulation, auto reset of target at start of emulation, 5v. supply only required and PC hosted software which includes a hex editor & file format conversion utilities.

The PROGULATOR: £180 inc.

Further details and a DEMO DISK from:

White House Systems Tel: 091-373-4605

48 South Terrace, Esh Winning, Durham DH7 9PS



IF AN ADVERT IS WRONG, WHO PUTS IT RIGHT?

We do. The Advertising Standards Authority ensures advertisements meet with the strict Code of Advertising Practice. So if you question an advertiser, they have to answer to us.

To find out more about the ASA, please write to:
Advertising Standards Authority,
Department X, Brook House,
Torrington Place, London WC1E 7HN.



This space is donated in the interests of high standards in advertisements.

placement types for this receiver.

A feature of using an IF transformer for the LO tuning coil is that the secondary of the coil can be used as a test point ('OSC TEST') for measuring the oscillator frequency.

The output network of the NE602 is the differential form seen in Dillon earlier. A 47-nF capacitor is connected across output pins 4 and 5 for AM and LO/RF suppression. A differential operational amplifier (IC₂) is used as an audio preamplifier to boost the signal level about 30 dB. The output of this amplifier is coupled through C₁₅ to a non-inverting amplifier with a gain of 11. This stage was initially not used, but the audio output proved to be lower than I deemed comfortable when fed directly to the LM386 amplifier on the main chassis.

Both operational amplifiers are type CA3140 BiMOS devices, although it must be mentioned that the selection was based on supplies on-hand. There is no reason why any garden-grade op-amp would not work (the required audio bandwidth is only 3,000 Hz for SSB and even less for CW). A common 741 (which shares the pin-outs of the CA3140), or any other common op-amp will do nicely. Keep in mind, however, that the capacitors from pin no. 7 of both IC₂ and IC₃ are absolutely mandatory if CA3140 devices

are used, and they must be connected as close to the body of the amplifier as possible.

The d.c. power distribution in this circuit is simple and straightforward. The +12 V supply voltage is applied directly to IC₂ and IC₃, which are both wired in the 'single-supply' configuration. In the case of IC₂ the amplifier is differential, so one of the resistors goes to +5 V rather than to ground, as is usual in such amplifiers. In the case of IC₃ there is a resistor voltage divider (R₈/R₉) used to bias the non-inverting input. Because of this form of operation, there will be a potential of about +6 V at output pin 6, so as a result a coupling capacitor (C₂₁) is needed to prevent interaction with the following stages.

This circuit performed reasonably well, but I felt that it lacked some of the sensitivity seen in the high frequency versions. In addition, there was severe interference from AM broadcast band signals at 560 KHz, 630 KHz and 1220 KHz (which station is very close to my home). A VLF RF preamplifier and proper shielding of both circuits solved the problem. I still intend to experiment with low-pass filters set to attenuate signals above 520 KHz as a means for eliminating the AM signals.

Use your electronics know-how to create great sound!

Speaker Builder, the world's only loudspeaker magazine in English, can show you how to achieve excellence in sound from your stereo system. Whether you're modifying and improving your present speakers or building a new design from scratch, *Speaker Builder* contains the latest in loudspeaker technology. Within its pages, learn about Thiele-Small design software, build an inexpensive measurement mike good enough for the professionals, or simply indulge in reading about the experiences of others using their technical skills to improve the sound around them.



Since 1980, *Speaker Builder* has been exploring both the traditional and more unusual formats for loudspeakers. From pipes to corrugated boxes to transmission lines and electrostatics, every conceivable medium is discussed. An international forum for speaker enthusiasts the world over, sharing ideas and designs, *Speaker Builder* has made it possible for thousands to enjoy the highest quality sound without straining their budgets.

The publishers of *Speaker Builder* invite you to use your electronics know-how to discover the world of better sound. To subscribe, simply return the form below with your payment or FAX your credit card order and receive 8 issues of *Speaker Builder* for a low introductory rate of \$45 for a one-year subscription. That's a \$5 savings off the regular overseas airmailed rate. Or you may subscribe for two years at \$80 (\$10 off).

☐ One Year \$45 ☐ 2 Years \$80

Remittances in US funds drawn on a US bank only.

MC/ISA NUMBER

EXP. DATE

NAME

ADDRESS

CITY

ST

ZIP

Speaker Builder

PO Box 494, Peterborough, NH 03458-0494 USA
(603)924-9464 or FAX (603)924-9467 24 hours

Conclusion


In the two instalments of this article we have toured the world of direct conversion receivers, examined their weaknesses and strengths and provided some examples of both circuit elements and complete circuits. What is left is for you to design and build a version of your own.

References and notes:

1. John Dillon, WA3RNC, 'The Neophyte Receiver', *QST*, August 1988, pp. 14-19.
2. Roy W. Lewallen, W7EL, 'An optimized QRP Transceiver', *QST*, August 1980, pp. 14-19; Rick Campbell, KK7B, 'High-Performance Direct-Conversion Receivers', *QST*, August 1992, pp. 19-28.
3. Dillon (*op-cit.*)
4. 'NE602 Primer', Joseph J. Carr, *Elektor Electronics*, January 1992, pp. 20-25.
5. Telephone conversation between the author and Mr. Dillon (Oct. 19, 1992)
6. 'The QRP Three-Bander CW Transceiver for 18, 21 and 24 MHz', *The ARRL Handbook for Radio Amateurs (1993 edition)*, American Radio Relay League (Newington, CT, 1992), pp. 30-19 to 30-25.

RS232 INTERFACE FOR UNIVERSAL BUS

Design by A. Rietjens

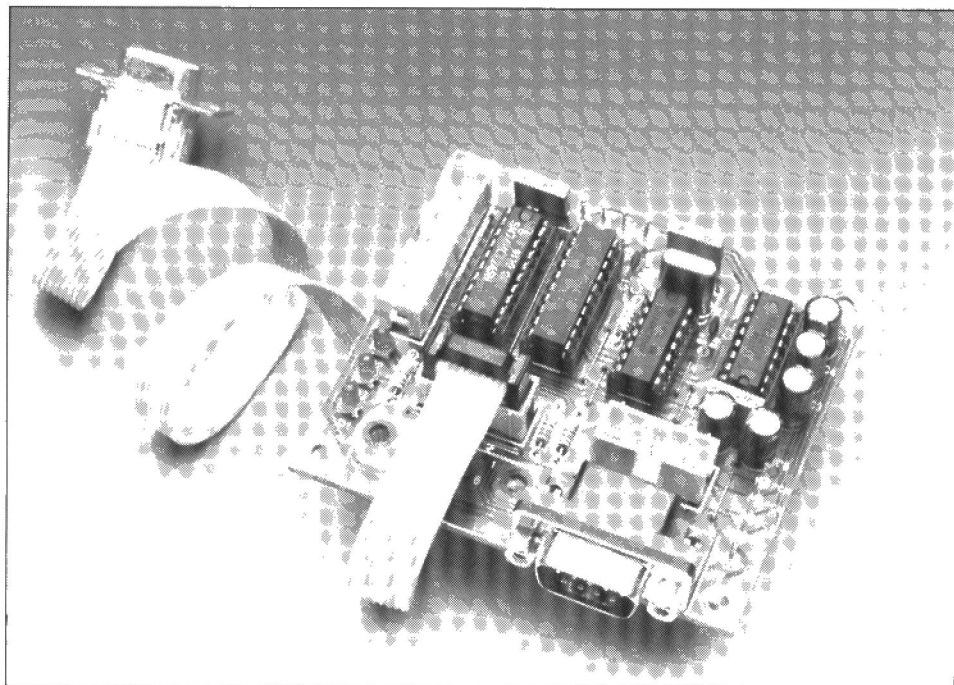

THIS is an RS232 extension card for the Universal I/O Interface for IBM PCs (Ref. 1). The circuit is based on the COM81C17 UART (universal asynchronous receiver/transmitter) from Standard Microsystem Corporation (SMC). This IC has an on-board programmable baud rate generator, which obtains its clock from a quartz crystal oscillator built around three gates in the 74HCT04 package.

The COM81C17 acts as an 8-bit read/write device on the bus. The RS232 handshaking is limited to the RTS-CTS (request to send - clear to send) pair, which will be adequate for most purposes. The status of these lines is indicated by two LEDs, D2 and D3. The INT (interrupt request) output of the IC is used as an activity indicator. The INT pin goes low when an 'enabled' condition has occurred in the status register, which can be read by the computer system via the bus.

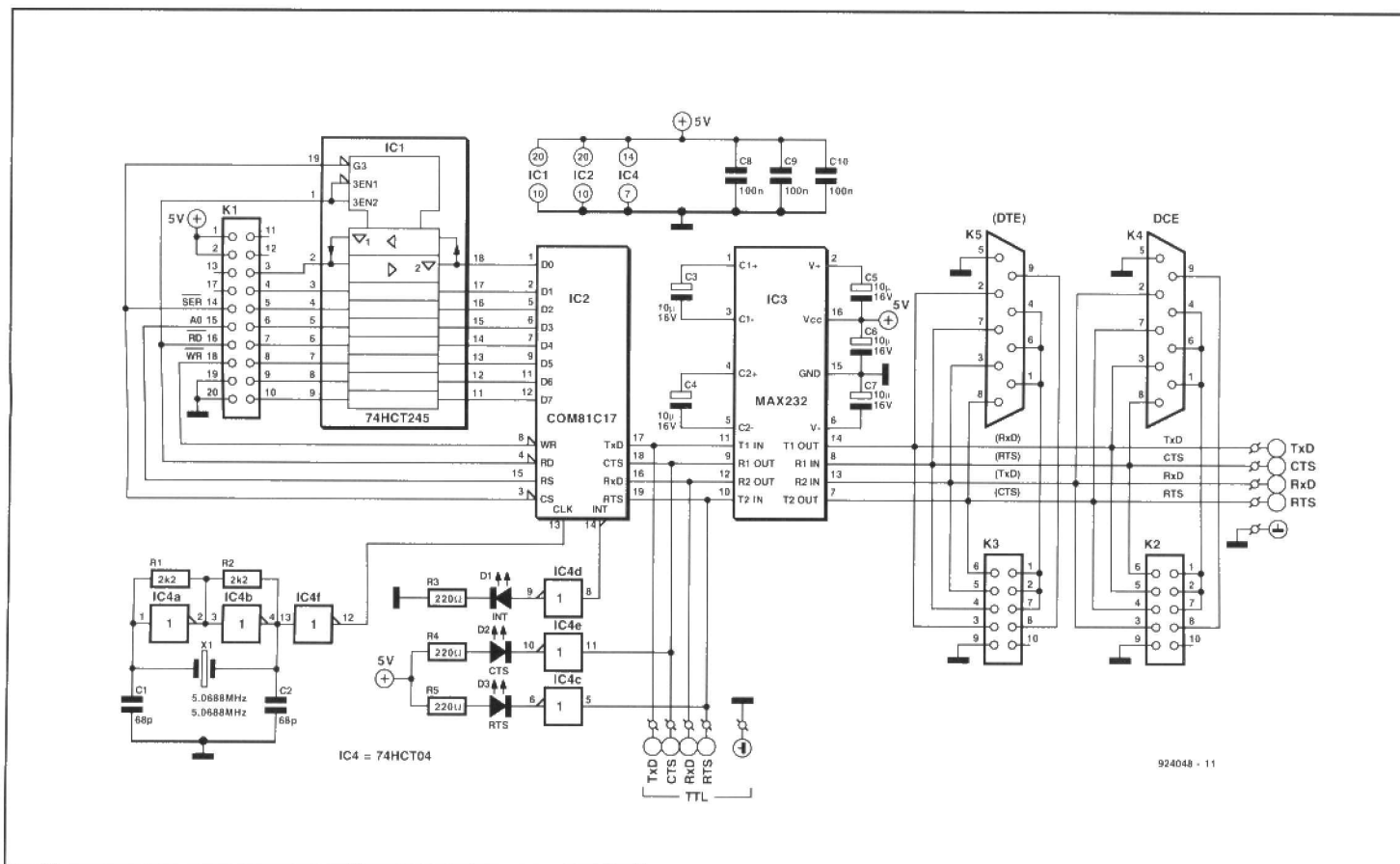


Fig. 1. Circuit diagram of the RS232 interface.

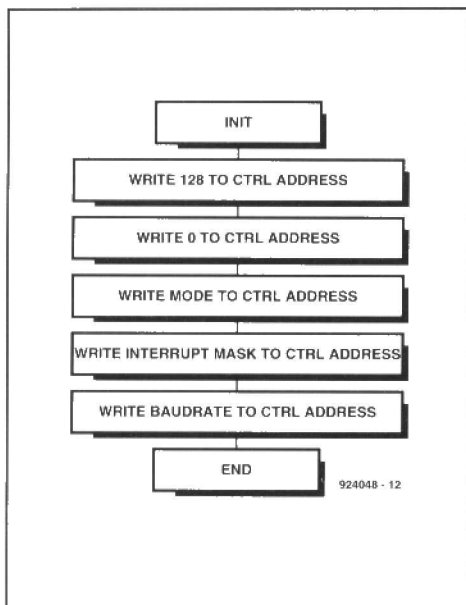


Fig. 2. UART initialization procedure flow-chart.

Remarkably, the COM81C17 is housed in a 20-pin DIL enclosure. The fact that it has 20 pins fewer than the well-known AY3-1015D (former 'industry standard') UART is mostly due to the fact that all status signals normally found on a UART are available as bits in a status register, rather than logic levels on IC pins. These status signals include Tx shift register empty, overrun error, parity error, Rx buffer full, and a host of others. The baud rate selection pins are also omitted and re-

Bit	Function	Description
D0	CP1	pin 18 (CP1): 0 = CTS (in); 1 = input
D1	I/O (CP2)	pin 19 (CP2): 0 = output; 1 = input
D2	CP2	pin 19 (CP2): 0 = RTS (output); 1 = input
D3	CLK	0 = internal divider; 1 = divide by 16
D4	PE	0 = no parity; 1 = parity enabled
D5	ODD	0 = even parity; 1 = odd parity
D6	# of data bits	0 = 7 databits; 1 = 8 databits
D7	# of stop bits	0 = 1 stop bit; 1 = 2 stop bits


924048-13

Fig. 3. UART MODE register programming.

Bit	Function	Description
D0	pin 18	input pin 18 (inverted)
D1	pin 19	input pin 19 (inverted); 0 if CP2 is output
D2	TX Shift Empty	1 if the transmit shift register is empty
D3	Parity Error	1 if parity error detected
D4	Overrun Error	1 if a character is overwritten before it has been fetched
D5	Frame Error	1 indicates wrong format received
D6	TX Buffer Empty	1 if the transmit buffer is empty
D7	RX buffer full	1 if the receive buffer is full

924048-14

Fig. 4. UART STATUS register programming.

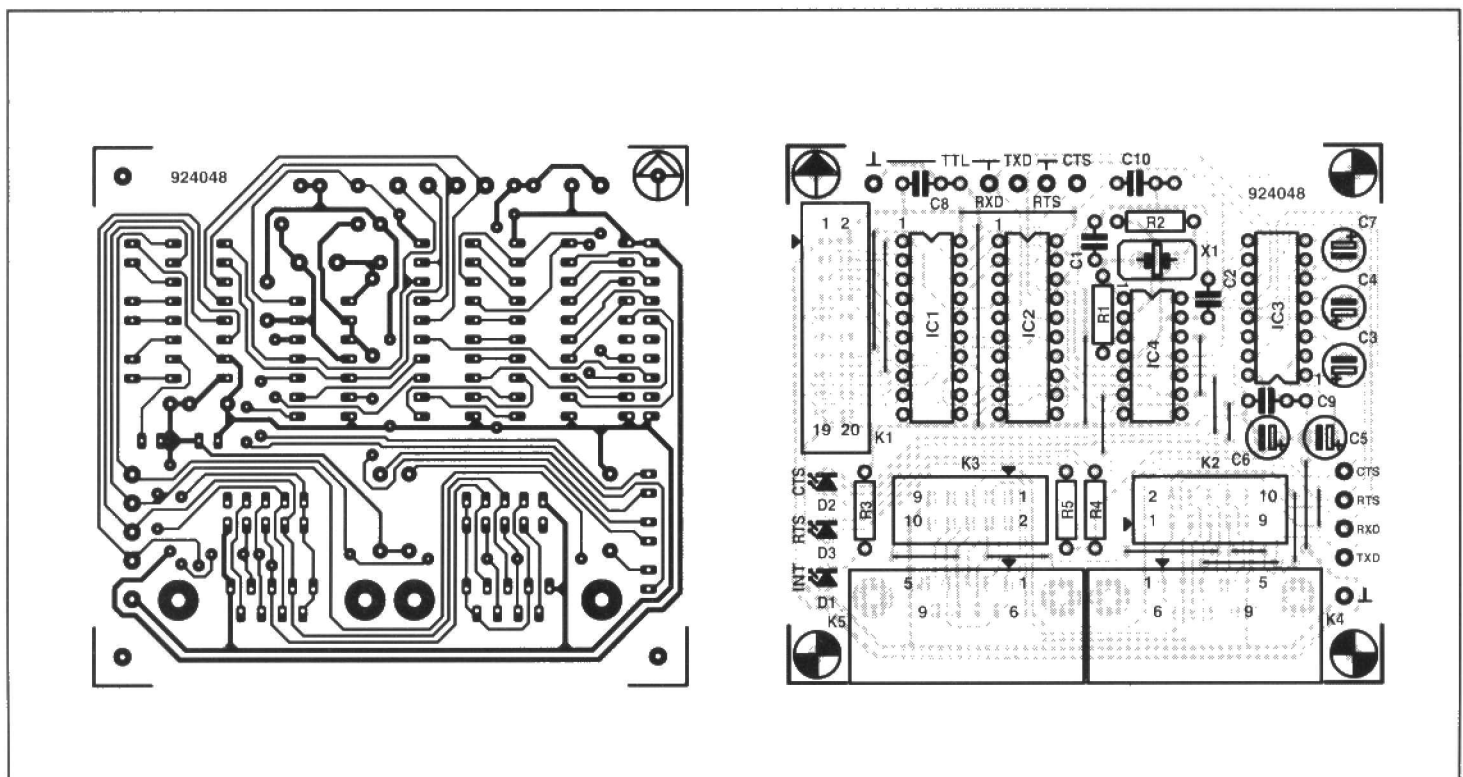

COMPONENTS LIST

Resistors:

R1;R2 = 2k Ω

R3;R4;R5 = 220 Ω

Capacitors:

C1;C2 = 68pF

C3-C7 = 10 μ F 16V radial

C8;C9;C10 = 100nF

Semiconductors:

D1;D2;D3 = LED, red, 3mm

IC1 = 74HCT245

IC2 = COM81C17 *

IC3 = MAX232

IC4 = 74HCT04

* SMC, head office: 35 Marcus Street,
Hauppauge, NY 11788, USA.

Telephone: (516) 273-3100.

UK distributors: Golden Gate,
Maidenhead, Telephone: (0628)

783631, Fax (0628) 71120, or
Manhattan Skyline, Maidenhead,
Telephone: (0628) 75851.

Miscellaneous:

K1 = 20-way boxheader.

K2;K3 = 10-way boxheader.

K4;K5 = 9-way angled PCB mount sub-
D connector.

X1 = quartz crystal 5.0688 MHz.

placed by a 'software' equivalent.

Unfortunately, it is beyond the scope of this article to cover all programming functions of the COM81C17. For full details, you are referred to the datasheets supplied by SMC, or to Ref. 3. Some information is, however, presented to get you started: an initialisation procedure flowchart (Fig. 2), mode and status register overviews, (Figs. 3 and 4), the baud rate selection table (Fig. 6), and a BASIC program (Fig. 7). The latter provides a useful test for the hardware by echoing transmitted characters. This requires K₃ or K₂ pins 3 and 5 (data) to be interconnected, and pins 4 and 6 (handshaking). Two jumpers are provided for this purpose. By the way, K₂ and K₃ are wired such that they can be connected directly to IDC-style D-connectors via lengths of flatcable (a straight pin1-to-pin 1 connection is used).

A MAX232 (with on-board negative voltage converter) is used in a standard configuration to interface the COM81C17 to the RS232 peripheral connected to K₄ or K₅. As shown in the circuit diagram, these two connectors allow the interface to behave like a DCE (data communication equipment) or a DTE (data terminal equipment). By

'tapping' the connections between the COM81C17 and the MAX232, a TTL-level serial interface is created, which may be used when RS232 levels are not required.

Finally, the addressing of cards connected to the universal bus, and the rules that apply to implementing read/write functions at one address, are discussed in Ref. 2. ■

References:

1. 'Universal I/O interface for IBM PCs and compatibles', *Elektor Electronics* May 1991.
2. 'Optocard for universal PC I/O interface', *Elektor Electronics* July/August 1992.
3. Databook 4: peripheral chips. *Elektor Electronics* publication.

D3 - D0	Baud rate
0000	50
0001	110
0010	134.5
0011	150
0100	300
0101	600
0110	1200
0111	1800
1000	2000
1001	2400
1010	3600
1011	4800
1100	7200
1101	9600
1110	19200
1111	38400

924048-15

Fig. 6. UART baud rate selection.

```

10 ADDRESS = $B3C0
20 TXADDRESS = ADDRESS+0      : REM write transmit buffer
30 RXADDRESS = ADDRESS+0      : REM read receive buffer
40 CTRLADDRESS = ADDRESS - 1  : REM write only
50 STATUSADDRESS = ADDRESS + 1 : REM read only
60 CTRLBYTE = 8*16+64
70                                REM reset tpuart
80 CTRLBYTE = CTRLBYTE OR 128
90 OUT (CTRLADDRESS),CTRLBYTE
100 CTRLBYTE = CTRLBYTE AND 127
110 OUT (CTRLADDRESS),CTRLBYTE
120 CTRLBYTE = CTRLBYTE OR 128
130 OUT (CTRLADDRESS),CTRLBYTE
140 CTRLBYTE = CTRLBYTE AND 127
150 OUT (CTRLADDRESS),CTRLBYTE
160                                REM set cts in rts out and internal clock
170 PARITY = 1 : REM 0: no parity
180 ODD = 0 : REM 0: even parity 1: odd parity
190 BITS = 1 : REM # bits per character 3: 7 bits 1: 8 bits
200 STOPBITS = 0 : REM # of stop bits 0:1 stop bit and 1: 2 stop bits
210 CP1 = 0 : REM cp1 as cts input
220 CP2IO = 0 : REM cp2 as output
230 CP2 = 0 : REM cp2 functions as rts output
240 CLK = 0 : REM internal clock
250 MODE = CP1 * 1 + CP2IO * 2 + CP2 * 4 + CLK * 8
260 MODE = MODE + PARITY * 16 + ODD * 32 + BITS * 64 + STOPBITS * 128
270 OUT (ADDRESS),MODE : REM define outputs and transmit format
280 OUT (ADDRESS),&HFF : REM interrupt on all status changes
290 OUT (ADDRESS),5 : REM set baudrate to 2400 Bd
300 OUT (CTRLADDRESS),CTRLBYTE
310 A = INP (STATUSADDRESS) : REM dummy read
320 CTRLBYTE = CTRLBYTE OR 64 : REM reset error bits
330 OUT (CTRLADDRESS),CTRLBYTE
340 CTRLBYTE = (CTRLBYTE AND (255-8-16)) OR 38 : REM enable communication
350 OUT (CTRLADDRESS),CTRLBYTE
360 A=INP (STATUSADDRESS) : IF (A AND 128) <>128 THEN 380
370 PRINT A; : A= INP (RXADDRESS) : PRINT A : GOTO 360
380 FOR I=0 TO 255
390 A = INP (STATUSADDRESS) : IF (A AND 64) <>64 THEN 390
400 OUT (TXADDRESS),I
410 A= INP (STATUSADDRESS) : IF (A AND 128) <>128 THEN 410
420 A= INP (RXADDRESS)
430 IF A=I THEN PRINT " ";A;" ";
440 IF A<>I THEN PRINT A;" ";I;" error ";
450 AS=INKEY$ : IF AS <> "" THEN END
460 NEXT
470 GOTO 380

```

924048 - 16

Fig. 7. BASIC program to demonstrate the operation of the RS232 interface.

STROBOSCOPE LIGHT

A flash tube control circuit is described which is suitable for playful as well as serious applications. The unit has a flash frequency of up to 100 Hz, and may also be triggered by an external source.

Design by T. Giesberts

STROBOSCOPE lights are very much in vogue these days, and can be seen in discotheques and shop windows, but also in the hands of the car mechanic (actually it is hard not to see them, the light of the more powerful units having an almost blinding and dazzling effect).

Where most stroboscope lights have a flash rate of between 1 Hz and 10 Hz, the present design reaches a maximum of about 100 Hz. Although such a high frequency is pretty exacting on the components used, it does give the stroboscope a much wider application area. Apart from creating exciting light effects, the circuit may also be used for mechanical adjustments (car ignition systems), or for advanced studies of human movement (particularly in 'professional' sports training and physiotherapy).

Block diagram


The block diagram in **Fig. 1** should enable you to get an understanding of the operation of the circuit without having to know the exact function of each and every component. The dashed block in the centre of the drawing is the flash circuit proper. The flash tube, La , is triggered in a conventional manner. When the tube is quenched, triac Tr acts as an opened switch, so that capacitor C_b is charged by the power supply via resistor R_b (and R_a). When the triac is triggered and starts to conduct, the right-hand side of C_b is effectively taken to ground, whereupon this capacitor discharges itself abruptly via transformer Tr . The result is a high voltage pulse which is stepped up even further by the ignition transformer. The pulse fires the flash tube, which remains lit until capacitor C_a is discharged. Next, the tube goes out, the capacitors are recharged, and the circuit waits for a new trigger pulse for the triac.

So far, it all looks pretty simple. However, there are a few snags which have given rise to a some interesting

circuit details. Since it was desired to have a controlled amount of energy per flash, the circuit operates in such a way that the flash tube must discharge a capacitor, the value of which allows the amount of energy to be controlled fairly accurately.

An unexpected problem is caused by the charging of capacitor C_a . If the circuit is to achieve a high flash rate whilst guaranteeing the maximum possible flash energy, the capacitor must be charged very rapidly. This, in turn, requires a fairly small value of resistor R_a . An obvious disadvantage of the low value of R_a is that a relatively high current flows through the tube once this has been fired. This is undesirable, and must be avoided since it can cause thermal overloading of the tube. The problem is solved by adding (semiconductor) switch S , which remains closed during the charging phase, and is opened as soon as a trigger pulse arrives. Consequently, the supply is disconnected from the flash tube during the actual flash.

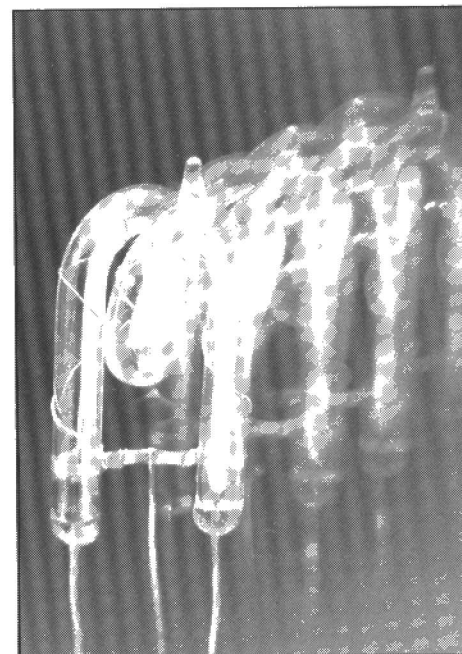Two monostable multivibrators are used to supply the trigger pulses, and control switch S . MMV_2 supplies the trigger pulses, while MMV_1 acts as a self-starting oscillator which deter-



mines the flash rate. First, a charge cycle is started for C_a , via switch S . This is immediately followed by an ignition pulse for the triac. Controls P_1 and P_2 allow the charging time and the flash repeat time to be adjusted respectively. In practice, things are a little more complicated than described here. A more detailed description will be given further on.

Finally, a switch is shown which enables the flashing to be stopped. Also, provision has been made to drive MMV_1 from an external oscillator. In that case, MMV_1 functions as a monostable multivibrator rather than an oscillator.

Practical design

The circuit diagram of the stroboscope light, **Fig. 2**, is a worked out version of the block diagram discussed above. Let us first do a quick tour around the various sub-circuits. The flash circuit proper is easily found because it is drawn in the direct vicinity of the flash

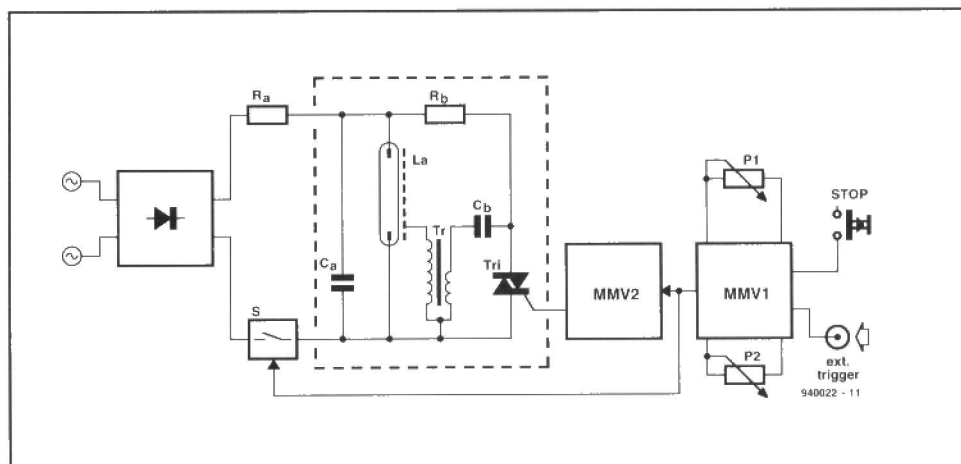


Fig. 1. Apart from a standard flash tube circuit (shown in dashed outline), the stroboscope also contains a power supply and a control circuit. When the tube flashes, the charge current which flows into C_a is interrupted by electronic switch S .

tube, La₁, transformer Tr₁ and triac Tr₁. The supply is roughly formed by the part around D₁-D₄ and C₁-C₂, while the drive circuit consists mainly of IC_{1a} and IC_{1b}. Switch S₁ functions as the 'stop' control; K₂ is the external oscillator input, and switch S shown in the block diagram is actually formed by a transistor, T₃.

The supply voltage is taken from the mains, and rectified. This causes a direct voltage of about 340 V across parallel connected high-voltage electrolytic capacitors C₁ and C₂. The flash capacitor, C₄-C₈, is charged via four parallel connected 10-watt resistors, R₅-R₈. Note that the flash capacitor consists of five parallel-connected low-loss solid capacitors for pulsed applications (Siemens MKP types) — an electrolytic type with an equivalent value (approx. 11 μ F) would be unsuitable considering the highest flash rate of about 100 Hz.

The flash tube, La₁, requires a firing voltage of between 4 and 6 kV. This voltage is supplied as a short pulse by

the secondary winding of transformer Tr₁ when C₉ discharges. The same pulse, however, also causes a considerable current surge through the primary winding of Tr₁. Consequently, a relatively high power triac is used — in this case, a TIC263M.

The drive signals for the triac (firing pulse) and the charging switch, T₃, are supplied by IC₁, a double MMV type 74HC221. This IC was chosen because it has some hysteresis on the positive trigger input. This affords a high degree of noise immunity, while the circuit is also capable of accepting extremely low-frequency trigger pulses. After the monotime of IC_{1a} has elapsed (adjustable with P₁), T₃ is switched off via pin 13. This causes the charging of C₄-C₈ to be stopped. At the same time, however, IC_{1b} is triggered. The MMV responds by supplying a pulse which is long enough to trigger the triac via T₁.

To prevent the flash tube from being overloaded while still achieving a reasonably high flash rate, the charging time control (P₂) and the flash rate con-

trol (P₁) are arranged to interact. This is achieved by adding the monotime set with P₂ to the time set with P₁. In this way, P₂ also determines the flash frequency. P₁ allows a maximum frequency of about 50 Hz to be set, which may be increased to 100 Hz by adjusting P₂. By virtue of the relatively short charging time, the energy fed to the flash tube remains more or less constant. At low frequencies, P₂ has a smaller effect on the frequency, and causes a small variation in brightness when the potentiometer is turned. If a flash tube is used which is different from the one stated in the components list, it may even happen that the trigger voltage drops below the firing threshold, and the tube starts to flash irregularly when P₂ is turned.

The 'stop' press-key is formed by S₁. If you use a push-to break switch in this position, the stroboscope flashes as long as you keep the key pressed. Alternatively, a normal on/off switch enables the circuit to be switched on and off permanently. Components D₈

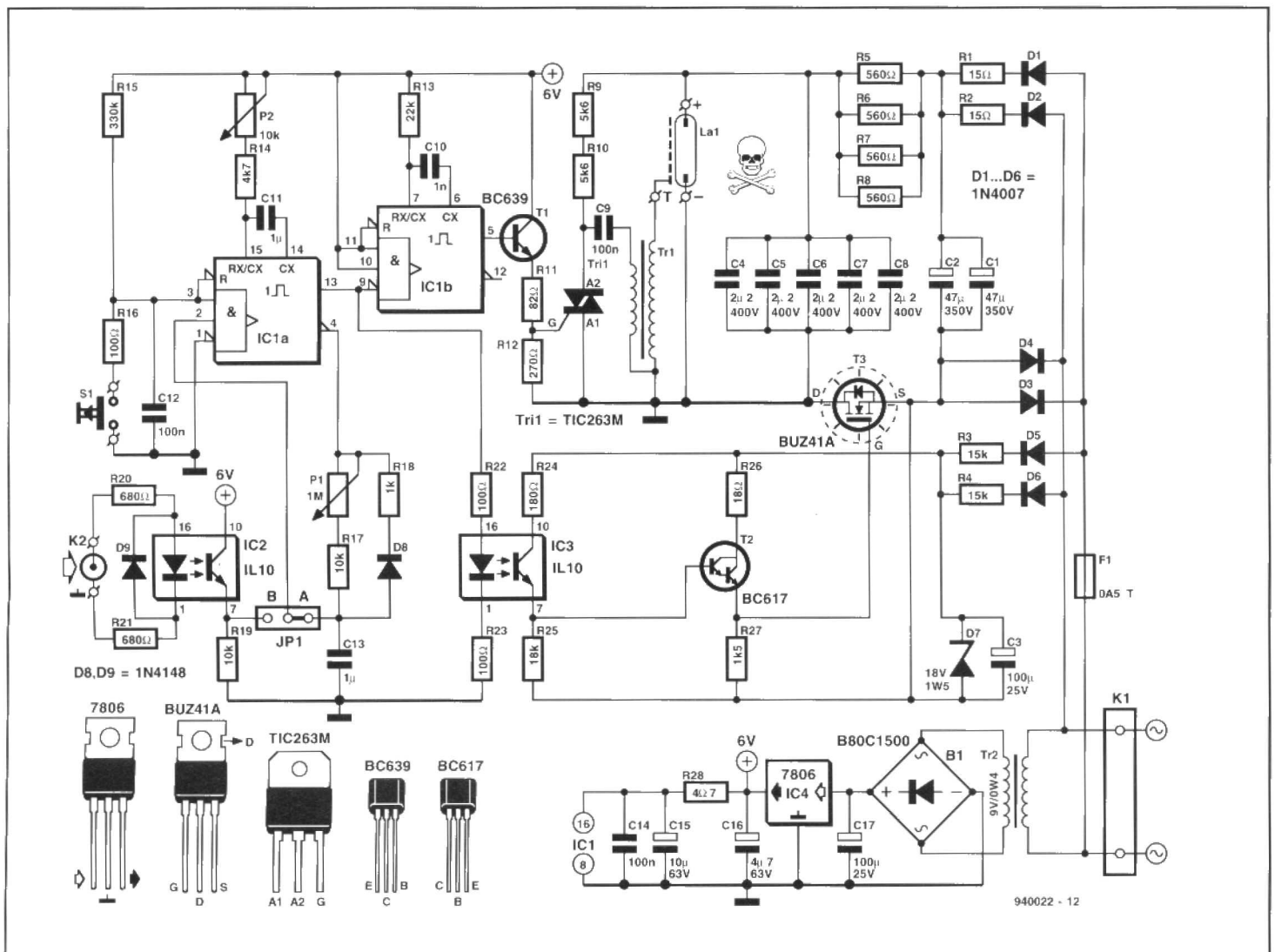


Fig. 2. The blocks shown in Fig. 1 are fairly easy to find back in this circuit diagram of the stroboscope light. In view of their dissipation, both the charging capacitor and the associated series resistor consist of a number of parallel connected components (capacitors C₄-C₈ and resistors R₅-R₈ respectively).

and R_{18} are added to enable C_{13} to be discharged during the period set with P_2 and R_{14} - C_{11} .

Opto-isolators

Apart from the electronics already discussed, **Fig. 2** also shows two opto-isolators, IC_2 and IC_3 . The first serves to afford electrical safety by creating isolation between the input of the external trigger oscillator (K_2) and the rest of the circuit. Jumper JP_1 allows you to select between internal and external triggering. If you select jumper position 'B', IC_{1a} operates as an MMV with P_1 effectively disabled. D_9 protects the LED in the opto-isolator, and limits the reverse voltage to about 0.7 V.

The second opto-isolator, IC_3 , has a quite different function. The controlling of power FET T_3 requires an additional circuit because a voltage difference of some 320 V occurs be-

tween C_4 - C_8 and the negative terminals of C_1 and C_2 . Consequently, the gate of T_3 would have to be driven (by IC_{1a}) with a potential which is 300 V higher! Obviously, that is a totally impractical requirement. Fortunately, the problem can be solved in a fairly simple way by adding an opto-isolator whose photo-transistor is fed from a separate supply line. This voltage is derived from the mains by rectifier D_5 - D_6 , current limiters R_3 - R_4 , smoothing capacitor C_3 , and stabilizer D_7 . Darlington transistor T_2 acts as a buffer between the photo-transistor in IC_3 and the gate of T_3 .

Still on the subject of supply lines, IC_1 and the triac drive circuit obviously require a suitable supply voltage also. Since the current consumption of the relevant components is too high to enable it to be supplied directly by the mains at reasonable efficiency, a miniature (0.35-VA) transformer is used (Tr_2). A couple of electrolytic ca-

pacitors and a 7806 (IC_4) are added to give a small 6-V d.c. power supply.

Construction

Before you start building the present project, seriously consider the following point regarding electrical safety. **Most parts in the circuit are at mains potential, and are, therefore, extremely dangerous to touch. Never touch any part while the circuit is connected to the mains. Always disconnect the circuit from the mains before doing any measurement or adjustment.** Also note that the high-voltage capacitors retain their charge for quite a while after the circuit is disconnected from the mains, so be extremely careful.

The artwork of the printed circuit board designed for the stroboscope light is shown in **Fig. 3**. Unfortunately, this PCB is not available ready-made

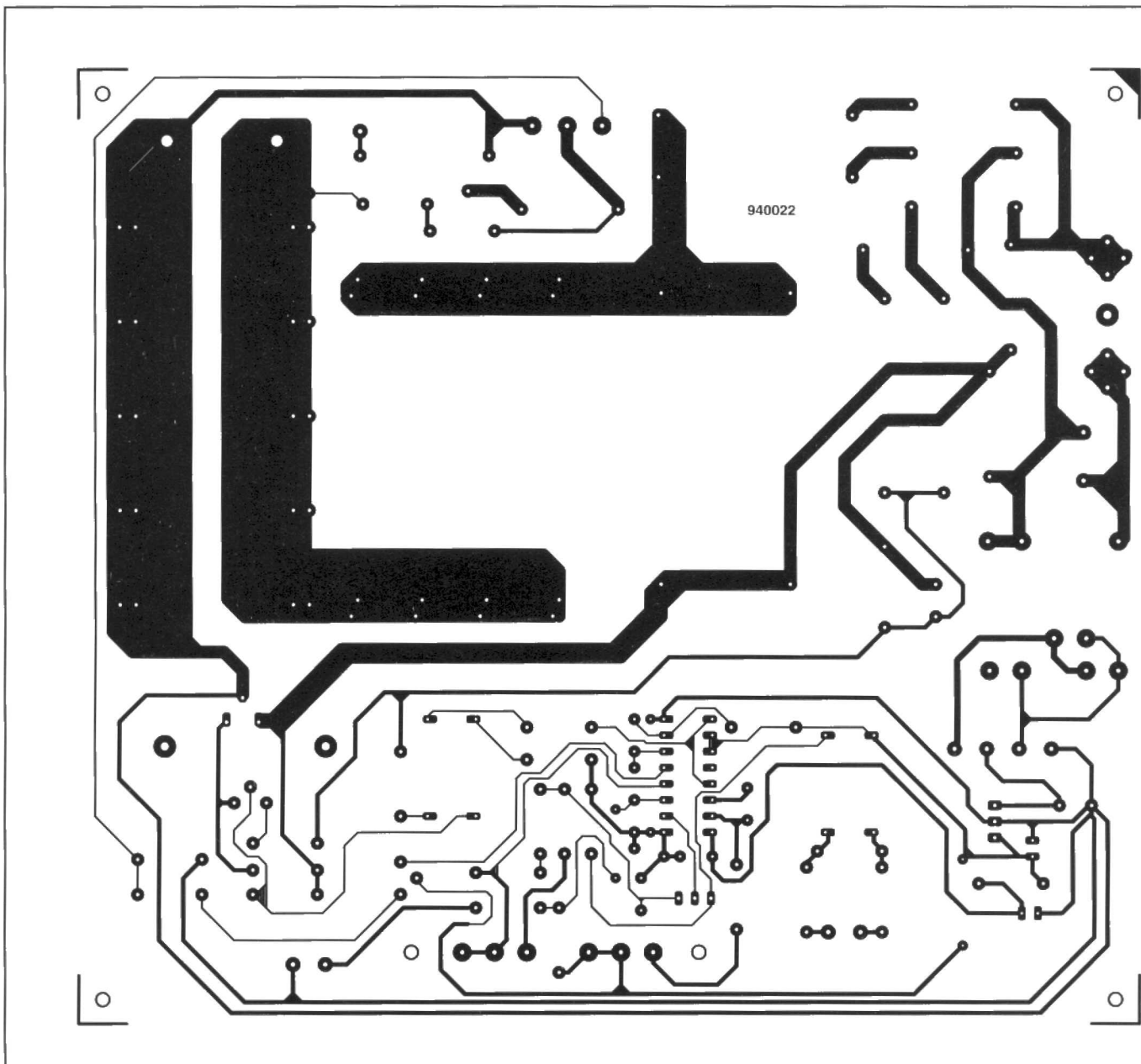


Fig. 3. The PCB is marked by its spacious track pattern between $C1$ - $C2$ and $La1$. Always keep in mind that most tracks on the board are

through our Readers Services, so you have to etch and drill it yourself (alternatively, you may want to have it made for you). The track layout is fairly 'spacious'. The copper tracks in the section roughly between C_1 and Tr_1 are very wide because of the high currents they carry. The connections for potentiometers P_1 and P_2 , socket K_2 , switch S_1 and the jumper are located at the front edge of the board. The rear edge has the connections for the flash tube, while the fuseholder for F_1 , and the PCB terminal block for connecting the mains cable (K_1), are found at the left-hand side edge.

A few notes must be made regarding the construction of the unit. Resistors R_5 through R_8 must be mounted at a height of about 1 cm above the board to allow for their dissipation. Transistor T_3 must be mounted on a fairly large heat-sink using an insulating washer and a bush. Given the cur-

rent through the flash tube, and its heat dissipation, the connection to the contacts provided on the board must be solid. For the prototype, spade terminals were used of the type found in cars. If it is desired to fit the tube at some distance from the board, mains rated cable should be used with good insulation properties and a minimum cross-sectional area of 2.5 mm^2 .

The potentiometers must be types with a plastic spindle. They are fitted direct on to the board using small brackets. The PCB layout is such that various types of mains transformer can be used. Voltage regulator IC_4 is only lightly loaded. Consequently it dissipates little heat, and can make do without a heat-sink.


Once all components are fitted on to the board, run a very careful inspection on your solder work. Also check the polarity of the high voltage electrolytics, C_1 and C_2 , and diodes D_1 - D_4 .

The photograph in **Fig. 4** shows the prototype of the PCB after completing the solder work and the visual inspection.

A case for a case

The choice of a suitable enclosure for the circuit will depend greatly on the nature of the application. One option is to fit the flash tube behind a window, in the same case as the control circuit. Alternatively, you may want to mount the tube in a separate, duly insulated, case, and connect it to the control circuit via a length of insulated cable. For the sake of safety, the control circuit must be mounted in a metal case which is connected to the mains earth line via a good quality mains socket.

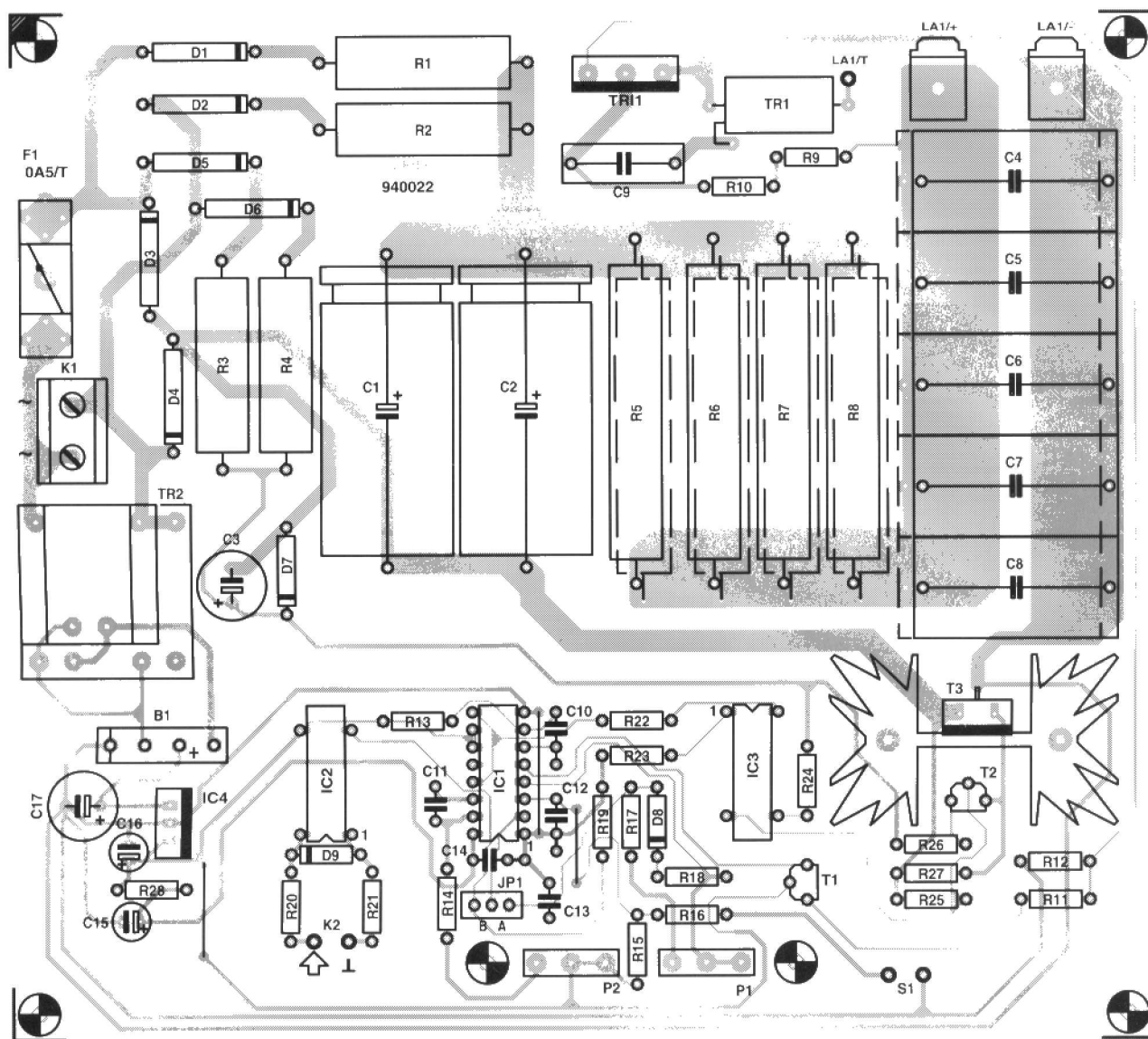Another point that deserves your attention is the heat developed by some parts of the circuit, notably R_5 - R_8 , T_3 and the flash tube. Keep in mind that



extremely dangerous to touch since they are at mains potential or even higher.

COMPONENTS LIST

Resistors:

R1;R2 = 15Ω 5W
 R3;R4 = 15kΩ 5W
 R5-R8 = 560Ω 10W
 R9;R10 = 5kΩ26
 R11 = 82Ω
 R12 = 270Ω
 R13 = 22kΩ
 R14 = 4kΩ7
 R15 = 330kΩ
 R16;R22;R23 = 100Ω
 R17;R19 = 10kΩ
 R18 = 1kΩ
 R20;R21 = 680Ω
 R24 = 180Ω
 R25 = 18kΩ
 R26 = 18Ω
 R27 = 1kΩ5
 R28 = 4Ω7
 P1 = 1MΩ log. (all ABS)
 P2 = 10kΩ lin. (all ABS)

Capacitors:

C1;C2 = 47μF 350V (Siemens B43050-C4476-T)¹
 C3;C17 = 100μF 25V radial
 C4-C8 = 2μF2 400V MKP (Siemens B32650-K4225-J)¹
 C9 = 100nF 400V MKP (Siemens B32650-K4104-J)¹
 C10 = 1nF
 C11;C13 = 1μF, pitch 5mm

C12,C14 = 100nF

C15 = 10μF 63V

C16 = 4μF7 63V

Semiconductors:

B1 = B80C1500
 D1-D6 = 1N4007
 D7 = 18V 1W5 zener diode
 D8,D9 = 1N4148
 T1 = BC639
 T2 = BC617
 T3 = BUZ41A
 IC1 = 74HC221
 IC2,IC3 = IL10 (Siemens)¹ or CNY65 (Telefunken)
 IC4 = 7806
 Tri1 = TIC263M

Miscellaneous:

JP1 = 3 PCB pins.
 K1 = 2-way PCB terminal block, pitch 7.5mm.
 K2 = BNC socket.
 S1 = Press-key w. make contact, mains rated.
 F1 = Glass fuse 0.5A slow, w. PCB holder.
 La1 = Xenon flash tube, e.g., FT-152G (Display Elektronika)².
 Tr1 = 6-kV trigger transformer, e.g. 58 16 15 (Conrad)³.
 Tr2 = Mains transformer 2x9V, e.g.

196-757 (Electromail)⁴. For 220V mains: BV 20 0009 (Hahn), 1090007M (Velleman) or EE20-0.35VA (Conrad).

Heat-sink for T3.

Two spade terminals, screw-mount.

¹ ElectroValue, Unit 3, Central Trading Estate, Staines TW18 4UX. Te. (0784) 442253, fax (0784) 460320.

² Display Elektronika, Coloradodreef 18, NL-3665 BT, Utrecht, Holland, Tel. (+31) 30 611855, fax (+31) 30 622024.

³ Conrad Electronic Nederland BV, P.O. Box 12, NL-7500 AA Enschede, Holland. Tel. (+31) 53 282000, fax (+31) 53 283075.

⁴ Electromail, P.O. Box 33, Corby, Northants NN17 9EL, England. Tel. (0536) 204555, fax (0536) 405555.

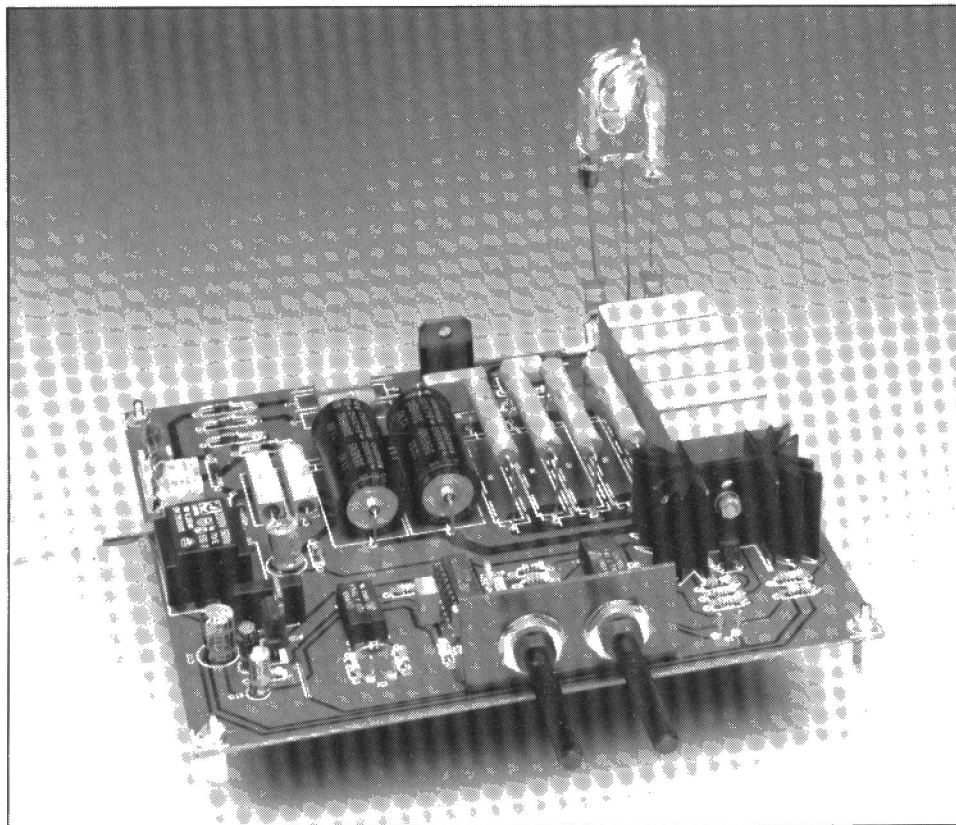


Fig. 4. Finished printed circuit board with components loaded, ready for mounting into a metal enclosure.

the heat dissipation increases with the flash rate. Some means of ventilation must, therefore, be provided in the case. If the flash tube and the control board are fitted in a single case, a small fan is probably no luxury.

Finally, a word about the flash tube. These devices come in many sizes and specifications. Many of these are suitable for use in the present circuit, and there is no need to insist on using the one mentioned in the parts list (FT-152G), although this has been tested by us, and is known to give good results even at the highest flash rate. The temperature of the tube rises with the repeat rate set with the potentiometers. This on its own causes thermal problems with some tubes. Unfortunately, a related problem then arises; the ignition voltage increases with the device temperature, so that the tube does not light at every discharge. In particular as regards too small tubes, be warned that the highest frequency that can be generated by the circuit may result in too much energy being fed to the tube. This may cause the lifetime of the tube to be reduced considerably. ■

READERS' CORNER

CORRECTIONS

Liquid crystal displays (February 1994 - p. 46)

Some pin numbers of IC₁ in Fig. 1 are shown incorrectly: pins 1 and 3, and pins 4 and 6, should be interchanged.

Telephone-controlled switch (January 1994 - p. 58)

The address of Chesilvale Ltd. in the Components List on p. 60 should read: Unit 3, Maes Glas Industrial Estate, Newport, Gwent NP9 2NN; Telephone +44 (0)633 223 552; Fax +44 (0)603 223 948.

PRODUCT NEWS

Parallel port data acquisition offers high performance at low cost

New from Computer Instrumentation Ltd is the 'Parallel Pad' Data Acquisition System. Connected to a PC or Notebook computer parallel port, the 'Parallel Pad' achieves data acquisition at up to 100 kHz using a 12 bit converter with programmable ranges from ± 10 mV to ± 10 V.

An additional screw terminal block assembly may be plugged in providing 8x4 wire inputs suitable for a range of sensors including thermocouples, PRTs, accelerometers, mV signals and mA signals. Also provided are 32 programmable logic input/output channels and two counter/timers for frequency measurements, and so on.

Powered from the mains, or its own internal batteries, the unit is suitable for lab-

oratory, factory or field use. A stand-alone (wake/sleep) data logging mode then allows the notebook to be taken home, leaving the 'Parallel Pad' to collect data under battery power.

At £445.00, the basic cost includes a range of software drivers for BASIC, Pascal, C, and Visual BASIC for Windows, together with versions of Computer Instrumentation's SoftScope and Data Logging software. Computer Instrumentation Ltd, Bld. no. 3 Woods Way, Goring, Worthing, England BN12 4QY; Telephone +44 (0)903 700 755; Fax +44 (0)903 700 788.

Let Maplin Electronics help beat the fuel VATman

With the imposition of VAT on fuel to come into operation this month, it is not too soon to be planning ways and means of reducing the household and office fuel bills. One sure fire way is the implementation of fuel saving devices and controllers and it is here that Maplin Electronics can help everyone to save money. The new Maplin catalogue (see back cover) features many cost effective, value for money products designed with energy saving in mind.

New from Maplin is the **24-hour Programmable Timer** which has many security and energy saving uses. Lights and radio can be timed to switch on and off throughout the day and night for security purposes, and a random program mode allows lights to be switched at random for even higher protection.

Also from Maplin is the **Digital Time-switch** comprising a battery powered clock with LC display which controls power throughout to a mains outlet. The unit plugs into a standard wall socket in which position the display and controls are

easily seen.

Also new is the **7-day Immersion Heater Controller**, a wall mounted unit that provides economical and convenient control of electric immersion heater systems. Easily programmable, the controller allows up to seven on/off switching programmes with automatic everyday allocation, providing up to 49 on/off settings per week. An optional 'boost' facility enables instant override for one or two hour periods.

Also available is a **Room Thermostat** which features easy-to-use controls for all kinds of heating system. Mounted on the wall, this thermostat, once set to the required temperature, will automatically trigger the heating system to come on and go off in order to maintain that temperature. This unit can be linked to any pump to control gas, solid fuel or oil fired central heating, warm air and electric underfloor or ceiling systems. The unit includes an 'accelerator' which reacts quickly to changes in room temperature so as to maintain an even level.

All items available from Maplin shops (including the new Northampton, Milton Keynes and Slough stores) or by mail order. (Please note: there is a £1.40 charge levied on every mail order to go towards the cost of handling and packing. On large, fragile or heavy items, an additional charge is made to contribute towards the cost of carriage, up to a maximum of £5.70 per order).

The Maplin 1994 Catalogue is available at £2.95 from W H Smith, R S McColl (Scotland) and local Maplin shops. Mail order price UK: £3.45.

Maplin Electronics, PO Box 3, Rayleigh, England SS6 8LR; Telephone: Sales +44 (0)702 554 161; Enquiries +44 (0)702 552 911; Fax +44 (0)702 553 935.

COMPONENT RATINGS

In resistor and capacitor values, decimal points and large numbers of zeros are avoided wherever possible. Small and large values are usually abbreviated as follows:

p (pico-)	= 10^{-12}
n (nano-)	= 10^{-9}
μ (micro-)	= 10^{-6}
m (milli-)	= 10^{-3}
k (kilo-)	= 10^3
M (mega-)	= 10^6
G (giga-)	= 10^9

Note that nano-farad (nF) is the international way of writing 1000 pF or 0.001 μ F. Resistors are $1/3$ watt, 5% metal film types un-

less otherwise specified.

The direct working voltage of capacitors (other than electrolytic or tantalum types) is assumed to be ≥ 60 V. As a rule of thumb, a safe value is about $2\times$ direct supply voltage.

Direct test voltages are measured with a 20 k Ω /V meter unless otherwise specified.

Mains (power line) voltages are not listed in the articles. It is assumed that our readers know what voltage is standard in their part of the world.

Readers in countries that use 60 Hz supplies, should note that our circuits are usually designed for 50 Hz. This will not normally cause problems, although if the mains frequency is used

for synchronization, some modification may be required.

The international letter symbol 'U' is used for voltage instead of the ambiguous 'V'. The letter V is reserved for 'volts'.

The size of a metric bolt or screw is defined by the letter M followed by a number corresponding to the overall diameter of the thread in mm, the \times sign and the length of the bolt or screw, also in mm. For instance, an M4x6 bolt has a thread diameter of 4 mm and a length of 6 mm. The overall diameter of the thread in the BA sizes is: 0 BA = 6.12 mm; 2 BA = 4.78 mm; 4 BA = 3.68 mm; 6 BA = 2.85 mm; 8 BA = 2.25 mm.

High sensitivity frequency counter/finder

Quantek Electronics have introduced a high sensitivity pocket size frequency counter/finder, Model FC2000, capable of measuring frequencies from 1 MHz to 2.4 GHz.

Conventional frequency counters typically have a specified sensitivity of 10 mV, whereas that of the FC2000 is <1 mV between 10 MHz and 850 MHz and is typically 225 µV at 150 MHz. This enables the FC2000 to be used for measuring transmitted radio frequency signals as well as for laboratory bench measurements.

The compact and rugged design of the FC2000 makes it ideally suited for use by field service engineers, radio amateurs, scanning receiver owners for frequency finding, and counter surveillance operators.

The FC2000 has a bright 8-digit LED display, two gate times, hold function, charge and gate LEDs, 50-Ω BNC input, internal 700 mAh NiCd batteries, and is supplied complete with a.c. mains adaptor/charger and telescopic BNC antenna.

The FC2000 costs £119 + £5 p&p and is available direct from Quantek Electronics, 3 Houldey Road, Birmingham, England B31 3HL. Telephone +44 (0)21 411 1821; Fax +44 (0)21 411 2355.

Mitsubishi 38000 Series of 8-bit microcontrollers from Highland Technology

Available from Highland Technology is the Mitsubishi 38000 Series of 8-bit microcontroller, which includes general-purpose types as well as devices designed specifically for controlling vacuum fluo-

rescent and liquid crystal displays.

The controllers are designed for ease of use and versatility, with ROM, RAM, I/O and control registers all within the same address space to allow data transfer and operation to be performed by common instructions.

The devices can operate in either single-chip mode, accessing only internal memory, or in expanded and external memory modes in which I/O ports become address, data and control lines, mapping external memory and peripherals.

Further details from Highland Technology, Albert Drive, Burgess Hill, England RH15 9TN. Telephone +44 (0) 444 236 000; fax +44(0)444 236 641.

TOR 1502 Digital Multimeter

The TOR 1502 Digital Multimeter is an easy-to-use, hand-held, high-accuracy meter, all range and functions of which are selected by rotary switch and displayed on a large 23 mm 3½ digit liquid crystal display. Among its features are: frequency testing up to 1 MHz, capacitance testing in five ranges up to 99.9 µF; when used in conjunction with any of the optional K-type thermocouples, it has a wide temperature testing range of -20 °C to 1300 °C. With automatic positive and negative indication, diode test, over-range indication, overload protection, low battery indication, continuity beeper and current testing up to 10 A, it is particularly useful for all kinds of service engineering, test management and laboratory applications. The TOR 1502 is supplied complete with test leads and instruction manual.

Full details from TOR Technologies,

TOR House, Earl Shilton, Leicester, England LE9 7DG; Telephone +44 (0)455 844 114; Fax +44 (0)455 844 116.

GENERAL NEWS

Piracy on the high CDs

Recent IFPI (International Federation of the Phonographic Industry) figures show that the number of pirated CDs illegally printed or imported into the UK reached 700,000 in 1992. In 1991 there were hardly any.

CD piracy is increasing dramatically throughout Europe – IFPI research suggests there were 13 million illegal discs in 1991 and nearly 19 million in 1992 – and whilst the number of illegal discs sold in the UK last year amounted to only 1% of total sales, that figure is expected to increase greatly this year both here and in Europe.

With the growth of the domestic and commercial multimedia and CD-ROM markets, it can not be long before they, too, become noticeably affected by illegal counterfeiting – with resultant revenue loss to publishers, game-ware producers, film companies, and others.

Disctronics, Europe's leading independent CD manufacturer, have sailed to the rescue with the introduction of a low-cost and effective counter measure which identifies the CD as being genuine and also prevents a disc from being copied. They have announced their ability to print holograms in colour on CDs. This not only provides security – it is virtually impossible to copy a hologram

Produced and published by **ELEKTOR ELECTRONICS (Publishing)**

Editor/publisher: Len Seymour
Technical Editor: J. Buiting

Editorial & Administrative Offices:
P.O. Box 1414
DORCHESTER DT2 8YH
England
Telephone: (0305) 250 995 (National)
or +44 305 250 995 (International)
Fax: (0305) 250 996 (National)
or +44 305 250 996 (International)

U.K. Advertising Office:
3 Crescent Terrace
CHELTENHAM GL50 3PE
Telephone: (0242) 510 760
Fax: (0242) 226 626

International Advertising Office:
Elektuur BV
P.O. Box 75
6190 AB BEEK
The Netherlands
Telephone: +31 46 38 94 44
Fax: +31 46 37 01 61

Subscriptions:
World Wide Subscription Service Ltd.

Unit 4, Gibbs Reed Farm
Pashley Road
TICEHURST TN5 7HE
Telephone: (0580) 200 657 (National)
or +44 580 200 657 (International)
Fax: (0580) 200 616 (National)
or +44 580 200 616 (International)

Head Office:
P.O. Box 75
6190 AB BEEK
The Netherlands
Telephone: +31 46 38 94 44
Telex: 56617 (elekt nl)
Fax: +31 46 37 01 61
Managing Director: M.M.J. Landman

Distribution:
SEYMOUR
1270 London Road
LONDON SW16 4DH

Printed in the Netherlands by NDB,
Zoeterwoude

Overseas editions:
FRANCE
Elektor sarl
Les Trois Tilleuls
B.P. 59; 59850 NIEPPE
Editor: G.C.P. Raedersdorf

GERMANY
Elektor Verlag GmbH
Süsterfeld Straße 25
5100 AACHEN
Editor: E.J.A. Krempelsauer

GREECE
Elektor EPE
Kariskaki 14
16673 Voula—ATHENA
Editor: E. Xanthoulis

HUNGARY
Elektor Elektronikai folyóirat
1015 Budapest
Batthyány u. 13
Editor: Lakatos András

INDIA
Elektor Electronics PVT Ltd
Chhotani Building
52C, Proctor Road, Grant Road (E)
BOMBAY 400 007
Editor: C.R. Chandarana

ISRAEL
Elektorcal
P.O. Box 41096
TEL AVIV 61410
Publisher: M. Avraham

NETHERLANDS
Elektuur BV
Peter Treckpoelstraat 2-4
6191 VK BEEK
Editor: P.E.L. Kersemakers

POLAND
Elektor Elektronik
02-777 Warszawa 130
Skrytka Poczтовая 271
Editor: W. Marciniak

PORTUGAL
Ferreira & Bento Lda.
R.D. Estefani, 32-1°
1000 LISBOA
Editor: F. Ferreira de Almeida

SPAIN
Resistor Electronica Aplicada
Calle Maudes 15 Entlo C.
28003 MADRID
Editor: Agustin Gonzales Buelta

SWEDEN
Electronic Press AB
Box 5505
14105 HUDDINGE
Editor: Bill Cedrum

ble to copy a hologram without extremely sophisticated (and expensive) equipment – but the discs also look highly attractive. More importantly, it allows the customer to identify the genuine product and avoid buying a sub-standard imitation.

Integrating this hologram into the CD has been developed by Discronics by placing the optical security information on the same side as the sound/data track. It will also include hidden optical information for the independent evaluation requirements of the trading standards authorities.

Discretics is one of the pioneers of the CD-ROM and multimedia revolution. Last December, they became the first company in the world to produce Video-CD (the use of digital compact discs with film footage) to the agreed White Book Standard. This allows CDs to be played on all platforms, including Commodore Amiga CD32, CDi and Multimedia PC.

For consumers, this will mean that they can buy any Video-CD player in the knowledge that it will play not only their music CDs, but also open up the huge range of Video-CDs which will be coming on to the market in the next few months – including films, games-ware and music videos.

Further information from Disctronics
UK CD-ROM Division, Southwater
Business Park, Worthing Road, Southwater,
England RH13 7YT. Telephone +44 (0)403
732 302; fax +44 (0)403 732 313.

SWITCHBOARD

Switchboard allows all PRIVATE READERS of *Elektor Electronics* one FREE advertisement of up to 108 characters, including spaces, commas, numerals, etc., per month.

Write the advertisement, which **MUST** relate to electronics, in the coupon on this page; it **MUST INCLUDE** a private telephone number or name and address; post office boxes are **NOT** acceptable.

Elektor Electronics (Publishing) can not accept responsibility for any correspondence or transaction as a result of a free advertisement or of any inaccuracy in the text of such an advertisement.

Advertisements will be placed in the order in which they are received.

Elektor Electronics (Publishing) reserve the right to refuse advertisements without giving reasons or without returning them.

FOR SALE. Data base disk of *Elektor Electronics* 1983–1993, DB3 based; includes search program; £ 9.95. Call Gary on 081-861-2216.

!HELP! Can anyone suggest a source of $\geq 10\text{ kV } \geq 20\text{ mA}$ fast diodes for my home-brew switch-mode PSU? Phone Alan on 081 800 0982.

WANTED. 27128 EPROMs 21 V. Please phone (0222) 566 413.

WANTED. Information on PCB and schematic programs used in *Elektor Electronics*. Please

Increase your electronics know-how and skills

The speed and intensity with which electronics penetrates our daily lives at home, at work, or in our car, tends to make us forget that we **can use electronics creatively** by building designs with a practical application and having the satisfaction of a successfully finished project. *Elektor Electronics*, which is distributed all over the world, can help you achieve these goals. Throughout the year, the magazine features original construction projects, informative articles and news on the gamut of electronics, science & technology, book reviews and information on new products. The past 11 issues contained 80 major and 97 minor construction articles, 21 articles of an educative or instructional nature, and 10 articles dealing with Science & Technology.

If you wish to increase your electronics know-how and skills, take out an annual subscription to *Elektor Electronics* by writing or faxing to

World Wide Subscription Service Ltd

Unit 4, Gibbs Reed Farm

Pashley Road, Ticehurst

East Sussex TN5 7HE, England

Telephone (0580) 200 657; Fax (0580) 200 616

You will then have the convenience of having the magazine delivered to your home, and the peace of mind that you will not miss any issue. The 1994 worldwide rates for an annual subscription (11 issues) are shown on page 72.

write to William Wallace, 934 Sharon Drive,
Lebanon, Ohio 45036, USA., or phone (513)
932-1277.

FOR SALE. Z80-based computer, keyboard, monitor, disk drive, documentation, software, £ 150 o.n.o. Call after 6 p.m. (0905) 353 531.

WANTED. Acorn Atom with disk drive, any condition. Please ring (0729) 860 224.

WANTED. Epsom FX800 circuit. Please write to R. Click, 12 Avon Grove, Cheadle, Stoke on Trent, Staffs ST10 1QR.

FOR SALE. Philips scope PM3217, 50 MHz, calibrated will October 1994, with leads and pouch. £250 o.n.o. Please ring 091 372 0923.

HELP! I need some information about the Orcad program. I need the file 'LIB EDIT' for 3.21 version. Thanks in anticipation. Please write to Luis M. Pinto, C. de Vila-Nespereira, 4620 Lousada, Portugal.

FOR SALE. PDP 11/23 main frame, 3 RL02 disk, 2 VT320 terms, 12 hard drive disks, working. £250 o.n.o. Please phone (0642) 711 368.

WANTED. Information/manual W.H.Y. for S.E. Labs 2001A frequency response analyser. Please ring (0602) 372 109.

FOR SALE. Z8 microcontroller-based single board computer system EPROM monitor, RS232, non-volatile RAM from £32. Call (0642) 480 620.

Send this coupon to
Elektor Electronics (Publishing)
P.O. Box 1414
Dorchester DT2 8YH
England

Block capitals please – one character to each box

A large rectangular grid consisting of 10 columns and 10 rows of squares, intended for drawing a picture.

ELEKTOR ELECTRONICS 03/94

Name and address MUST be given

READERS SERVICES

Except in the USA and Canada, all orders, except for subscriptions and past issues (for which see below), must be sent BY POST to our Dorchester office using the appropriate form opposite. Please note that we can not deal with PERSONAL CALLERS, as no stock is carried at the editorial and administrative office.

Readers in the USA and Canada should send orders, except for subscriptions (for which see below), to Old Colony Sound Lab, Peterborough, whose full address is given on the order form opposite. Please include shipping cost according to total order value. For surface delivery in the USA, if order is less than \$50, include \$3: \$50+, \$4. For Canada surface, if less than US\$50, include US\$5; US\$50+, US\$7.50. For air or other deliveries, please inquire. Please allow 4-6 weeks for delivery.

All other customers must add postage and packing charges for orders up to £25.00 as follows: UK and Eire £1.95; surface mail outside UK £2.45; Europe (airmail) £2.95; outside Europe (airmail) £3.70. For orders over £25.00, but not exceeding £100.00, these p&p charges should be doubled. For orders over £100.00 in value, p&p charges will be advised.

SUBSCRIPTIONS & PAST ISSUES

Subscriptions and past issues, if available, should be ordered from **Worldwide Subscription Service Ltd, Unit 4, Gibbs Reed Farm, Pashley Road, TICEHURST TN5 7HE, England**. For subscriptions, use the order form on the opposite page. Prices of past issues (except July/August and December), including postage for single copies, are £2.70 (UK and Eire); £3.00 (surface mail outside UK); £3.20 (air mail Europe); £3.95 (airmail outside Europe). Prices of past July/August and December issues, including postage for single copies, are £3.75 (UK); £4.00 (surface mail outside UK); £4.25 (airmail Europe); and £5.00 (airmail outside Europe).

PAST ARTICLES

Photocopies of articles from January 1978 onwards can be provided, postage paid, at £1.95 (UK and Eire), £2.10 (surface mail outside UK), £2.45 (airmail Europe), or £2.70 (airmail outside Europe). In case an article is split into instalments, these prices are applicable **per instalment**. Photocopies may be ordered from our editorial and administrative offices.

COMPONENTS

Components for projects appearing in *Elektor Electronics* are usually available from appropriate advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. It should be noted that the source(s) given is (are) not exclusive — other suppliers may also be able to help.

BOOKS

For book availability, see advertisement on page 51.

SHELF BOX

Elektor Electronics shelf box£2.95.....\$6.00

FRONT PANEL FOILS

PROJECT	No.	Price (£)	Price (US\$)
Timecode interface	910055-F	8.80	17.60
Digital function generator	910077-F	10.60	21.20
4-Megabyte printer buffer	910110-F	11.45	22.90
FM tuner	920005-F	13.20	26.40
4MB printer buffer card	920009-F	8.25	16.50
LC meter	920012-F	11.45	22.90
Guitar tuner	920033-F	8.80	17.60
NICAM decoder	920035-F	8.25	16.50
12VDC to 240VAC inverter	920038-F	16.15	32.30
Audio DAC	920063-F	10.00	20.00
Dig. audio/visual system	920022-F1	10.00	20.00
	920022-F2	19.40	38.80
	920022-F3	28.80	57.60
1.2 GHz multifunction frequency meter	920095-F	13.80	27.60
U2400B NiCd battery charger	920098-F	8.75	17.50

PROJECT	No.	Price (£)	Price (US\$)
Workbench PSU	930033-F	17.00	34.00
Inexpensive phase meter	930046-F	17.25	34.50
Mini preamplifier	930106-F	Not available	
AF rms voltmeter	930108-F	17.25	34.50

EPROMS / PALS / MICROCONTROLLERS

Amiga mouse/joystick switch (1 x GAL 16V8)	6001	8.25	16.50
4-Megabyte printer buffer (1 x 2764)	6041	15.30	30.60
8751 emulator			
incl. system disk (MSDOS)	6051	29.40	58.80
Connect 4 (1 x 27C64)	6081	15.30	30.60
EMON51 (8051 assembler course) (1 x 27256+disk 1661)	6061	20.00	40.00
EMON51 (8051 assembler course) (1 x 27256+disk 1681)	6091	20.00	40.00
FM tuner (1 x 27C256)	6101	15.30	30.60
Multi-purpose Z80 card: GAL set (2 x GAL 16V8)	6111	11.15	22.30
Multi-purpose Z80 card: BIOS (1 x EPROM 27128)	6121	15.30	30.60
1.2 GHz multifunction frequency meter (1 x 27C256)	6141	11.45	22.90
Digital audio/visual system (1 x 27C256)	6171	10.30	20.60
TV test pattern generator (1 x 27256)	6151	13.00	26.00
DiAV system. Package: 1 x 27512; 2 x GAL; 1 x floppy disk (MSDOS)	6181	30.50	61.00
PAL test pattern generator (1 x GAL 20V8-25)	6211	9.40	18.60
80C535 assembler course (1 x EMON52 EPROM and 1 x disk 1811)	6221	17.05	34.10
Watt-hour meter (1 x 27256)	6241	10.00	20.00
Four fold DAC (1 x GAL)	6251	10.75	21.50
Multipurpose display decoder (1 x 2764)	6261	11.50	23.00
Telephone-controlled switch (1 x 2764)	6271	14.50	29.00
Relative humidity meter (1 x 2764)	6301	14.50	29.00
535 card w. EPROM emulator (1 x PAL; 1 x GAL)	6311	26.00	52.00
Copybit eliminator (1 x GAL 16V8 and 1 x MACH110)	6321	42.25	84.50
RDS decoder (1 x 27C64)	6331	14.50	29.00
I ² C tester (1 x GAL 6001)	6341	30.75	61.50
8751 programmer (1 x 8751)	7061	46.40	92.80
Microcontroller NiCd charger (1 x ST62E15)	7071	10.00	20.00
Maxi micro clock (clock)	7081	11.50	23.00
Maxi micro clock (darkroom timer)	7091	11.50	23.00
Maxi micro clock (cooking timer)	7101	11.50	23.00
Mini micro clock (clock)	7111	11.50	23.00
Mini micro clock (darkroom timer)	7121	11.50	23.00
Mini micro clock (cooking timer)	7131	11.50	23.00
VHF/UHF TV tuner (1 x 87C51)	7141	25.75	51.50
Microcontroller-driven UART (1 x ST62T10)	7151	17.25	34.50
PIC programmer (1 x PIC17C42 and 1 x disk)	7161	50.00	100.00

DISKETTES

Plotter driver (D. Sijsma)	1541	11.15	22.30
I/O interface for Atari	1571	7.65	15.30
Tek/Intel file converter	1581	7.65	15.30
B/W video digitizer	1591	11.15	22.30
Timecode interface	1611	7.65	15.30
RTC for Atari ST	1621	7.65	15.30
24-bit colour extension for video digitizer	1631	11.15	22.30
PC controlled weather station - 3 (supercedes disks 1551 and 1561)	1641	7.65	15.30
8051/8032 Assembler course (IBM version)	1661	7.65	15.30
8051/8032 Assembler course (Atari version) (3.5")	1681	7.65	15.30
AD232 converter	1691	7.65	15.30
GAL programmer (3 disks; upgrade: June 1993)	1701	11.15	22.30

PROJECT	No.	Price (£)	Price (US\$)
Multi-purpose Z80 card	1711	7.65	15.30
Fuzzy Control One	1721	7.75	15.50
Pascal library for MMC	1751	9.70	19.40
Speech/sound memory	1771	7.65	15.30
PC-aided transistor tester	1781	7.50	15.00
IR receiver and DTMF decoder for 80C32 SBC	1791	9.00	18.00
80C535 assembler course	1811	8.80	17.60
I ² C opto/relay card	1821	7.65	15.30
Video digitizer for PCs	1831	14.50	29.00
GAL programmer for Amiga	1841	11.00	22.00
I ² C alphanumeric display	1851	8.50	17.00
Philips preamplifier	1861	8.50	17.00
GAL programmer (excl. Opal Jr. disks)	1881	10.75	21.50
Precision clock for PCs	1871	8.50	17.00
X2404-to-8751 interfacing	1891	8.50	17.00
Mini I/O card for Casio			
FX850/880P	1921	10.75	21.50
SIM — an 8051 simulator	1931	34.25	68.50

PRINTED CIRCUIT BOARDS

Printed circuit boards whose number is followed by a + sign are only available in combination with the associated software item, and can **not** be supplied separately. The indicated price includes the software.

DECEMBER 1993

535 card w. EPROM emulator incl. GAL and PAL (6311)	930103+	47.50	95.00
AF rms voltmeter	930108	12.25	24.50
I ² C power switch	930091	6.25	12.50
Medium power HEXFET amplifier	930102	12.75	25.50
Microcontroller driven UART	930073	4.75	9.50
SCART switching box	930122	14.25	28.50
Low-power NBFM transmitter	914114	Not available	
Photographic workshop light	930116	Not available	
Stereo PWM output amplifier	934076	Not available	

JANUARY 1994

Digital dial	920161	12.75	25.50
RDS decoder			
incl. EPROM (6331)	930121+	23.75	51.50
I ² C tester			
incl. GAL (6341)	930128+	36.25	72.50
Telephone-controlled switch			
incl. EPROM (6271)	934054+	37.25	74.50

FEBRUARY 1994

80C535 single-board computer	924046	14.10	28.20
Copybit eliminator			
incl. MACH and GAL	930098+	46.25	92.50
Mini preamplifier	930106	29.25	58.50
Bidirectional RS232-to-Centronics converter	930134	14.00	28.00
24 cm FM ATV transmitter			PCB available from author

MARCH 1994

PIC programmer			
incl. software set 7161	940048+	64.75	129.50
100W AF amplifier			
- adaptor board	930039	8.25	16.50
- amplifier board	920135-1	19.40	38.80
- protection board	920135-2	7.95	15.90
Mini I/O card for Casio			
FX850/880P	930090	Not available	
AF signal tracer	940006	Not available	
Electronic fuse	936071	Not available	

APRIL 1994

Mains transmission system (receiver)	940021-1	10.25	20.50
68HC11 processor board	930123	7.75	15.50
RS232 speedometer	930119	Not available	
Stroboscope light	940022	Not available	
Headphones amplifier	940016	18.75	37.50
Halogen light dimmer	940034	Not available	

A list of all PCBs, software products and front panels available through the Readers Services is published in the March, June, September and December issues of *Elektor Electronics*.

NEW


FULL COLOUR GUIDE TO ELECTRONIC PRODUCTS

Maplin



BS 5750
Part 2 1987

Level B:
Quality Assurance
RS12750

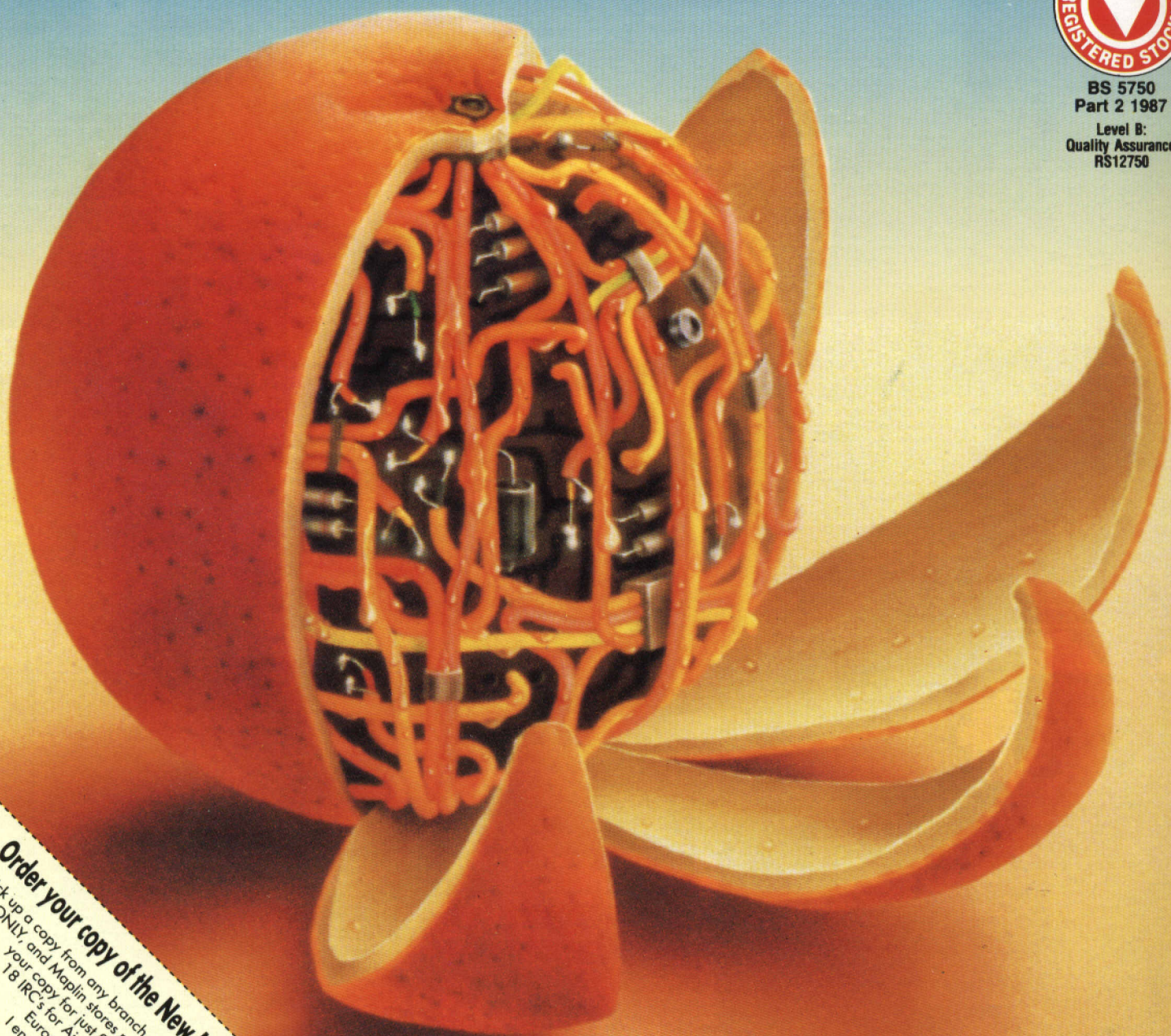

Order your copy of the New MAPLIN Catalogue on sale NOW!

Pick up a copy from any branch of WHSMITH, selected branches of RSM^{Mc}COLL in Scotland ONLY, and Maplin stores nationwide for just £2.95 or post this coupon now to receive your copy for just £3.45 inc. p&p. If you live outside the U.K. send £6.80 or 18 IRC's for Airmail in Europe/£5.20 or 13 IRC's for surface mail outside Europe; or £11.50 or 30 IRC's for Airmail outside Europe. I enclose £3.45/£6.80/£5.20/£11.50 (delete as applicable).

Name.....
Address.....
Post Code.....
Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex, England
SS6 8LR.
EK94

Over 700 colour packed pages with hundreds of brand New Products at Super Low Prices, on sale now, **only £2.95.**

Available from all branches of WHSMITH, selected branches of RSM^{Mc}COLL in Scotland ONLY, and Maplin stores nationwide. The Maplin Electronics 1994 Catalogue – **UNIQUELY DIFFERENT!**

Africa customers please contact MAPLIN (SOUTHAFRICA) Tel: (024) 51-5124